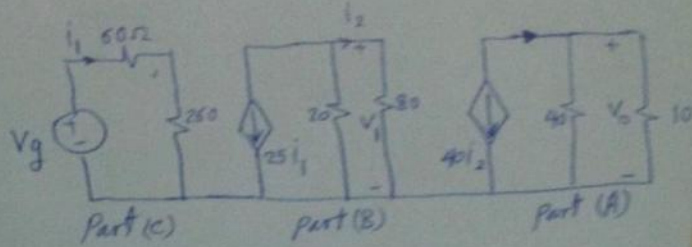


Question(1):

Given: $V_o = 5V$
 Required: V_g & V_1



Solution:

* Part (A)

$\therefore V_o = 5V$

$\therefore i_{10\Omega} = 5/10 = 0.5A$

$\therefore i_{40\Omega} = 5/40 = 0.125A$

$\therefore 40i_2 = -(i_{10\Omega} + i_{40\Omega}) = -0.625 \rightarrow i_2 = -0.015625A = -15.625mA$

* Part (B)

$\therefore i_2 = -15.625mA$

$\therefore V_1 = i_2 * 80 = -1.25V$

$\therefore i_{20\Omega} = V_1/20 = -1.25/20 = -62.5mA$

$\therefore 25i_1 = -(i_2 + i_{20\Omega}) = -(-15.625m - 62.5m) = 78.125m \rightarrow i_1 = 3.125mA$

* Part (C)


$\therefore i_1 = 3.125mA$


$\therefore V_g = i_1(60 + 260) = 3.125m * 320 = 1000mV = 1V$

$\therefore V_g = 1V \quad \& \quad V_1 = -1.25V \quad \dots \dots \text{Req} \neq$

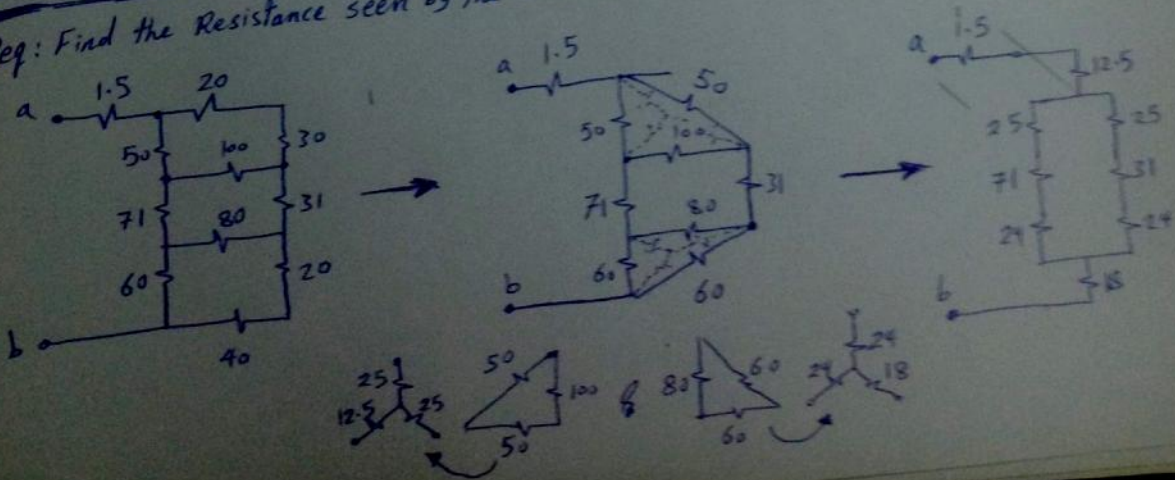Question(2):

Req: Find the Resistance seen by the Source



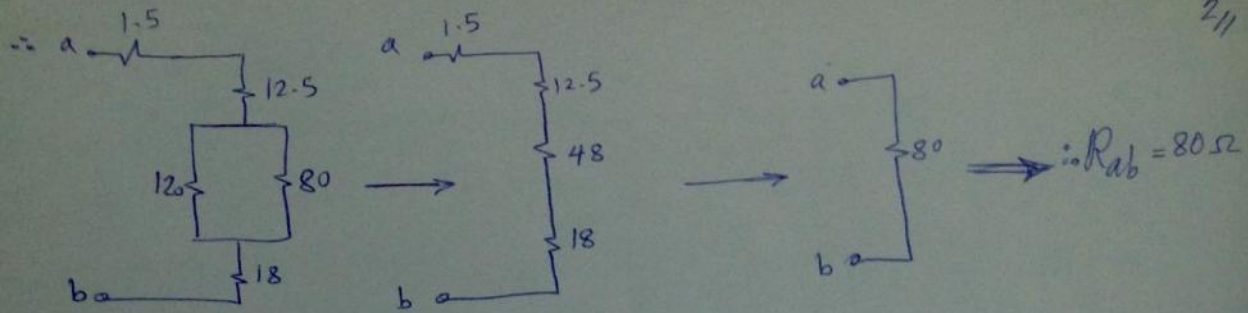


Question (3):

Using Node-Voltage to find V_o :

Solution:

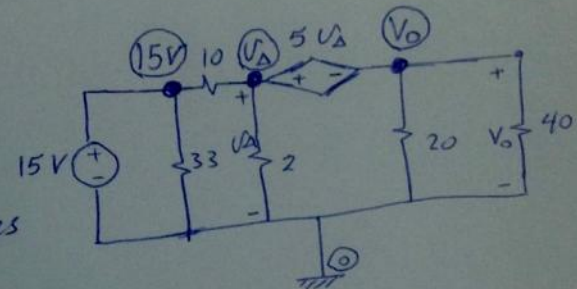Firstly: If there is Voltage Source between two unknown node voltages then (Super Node) is used



① $V_{\Delta} - V_o = 5V_{\Delta}$ ----- ①

② Apply KCL at the superNode:

$$\frac{V_{\Delta}}{2} + \frac{V_{\Delta} - 15}{10} + \frac{V_o}{20} + \frac{V_o}{40} = 0 \quad * (40)$$

$$\therefore 20V_{\Delta} + 4V_{\Delta} - 60 + 2V_o + V_o = 0$$


$$\therefore 24V_{\Delta} + 3V_o = 60 \quad \text{----- ②}$$

From ①, ② :

$$24V_{\Delta} + 3(-4V_{\Delta}) = 60$$

$$\therefore V_{\Delta} = 5V$$


$$V_o = -20V \quad \text{Req. \#}$$

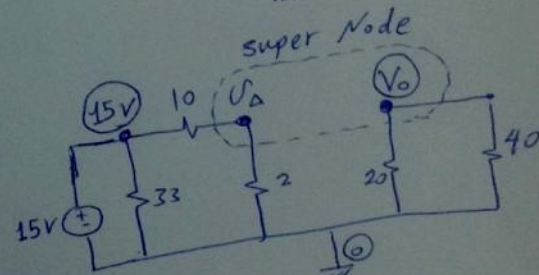

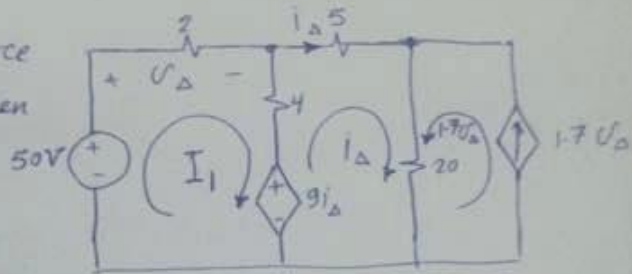Question (4):

Using Mesh current

Firstly: If there is current source between two unknown meshes then (super mesh) is used.



Ans: None

① Apply KVL at I_1 :

$$-50 + 2I_1 + 4(I_1 - i_\Delta) + 9i_\Delta = 0$$

$$6I_1 + 5i_\Delta = 50 \dots\dots ①$$

② Apply KVL at i_Δ :

$$-9i_\Delta + 4(i_\Delta - I_1) + 5i_\Delta + 20(i_\Delta + 1.7V_\Delta) = 0$$

$$-4I_1 + 20i_\Delta + 34V_\Delta = 0 \dots\dots ②$$

③ $V_\Delta = 2I_1 \dots\dots ③$

From ②, ③: $-4I_1 + 20i_\Delta + 34 * 2I_1 = 0$

$$64I_1 + 20i_\Delta = 0 \dots\dots ④$$

From ①, ④: $24I_1 + 20i_\Delta = 200$ ①

$$-64I_1 + 20i_\Delta = 0$$
 ④

$$-40I_1 = 200$$

$$\therefore I_1 = -5A \quad \& \quad i_\Delta = 16A$$

$$\therefore P_{50V} = \ominus 50 * I_1 = +250W \dots \text{absorbing}$$

$$P_{9A} = \oplus 9i_\Delta * (I_1 - i_\Delta) = -3024W \dots \text{generating}$$

$$P_{1.7V_\Delta} = \ominus 1.7V_\Delta * (20(I_1 + 1.7V_\Delta)) = -(-17) * (-20) = -340W \dots \text{generating}$$

∴ The sources that generating power are the dependent sources $g_{i\Delta}$ & $1.7 \mu\Delta$ ----- Req. (1) #

$$P_{\text{dissipated}} = P_{2\Omega} + P_{4\Omega} + P_{5\Omega} + P_{20\Omega} + P_{50V}$$

$$= (I_1^2 * 2) + [(I_1 - i_{\Delta})^2 * 4] + (i_{\Delta}^2 * 5) + [(i_{\Delta} + 1.7 \mu\Delta)^2 * 20]$$

$$+ P_{50V}$$


$$= 50 + 1764 + 1280 + 20 + 250 =$$

$$P_{\text{dissipated}} = 3364 \text{ W} \text{ ----- Req. (2) #}$$

$$P_{\text{generating}} = -3024 - 340 = -3364 \text{ W} \text{ ----- For check}$$

Question (5):

Find Thevenin eq.

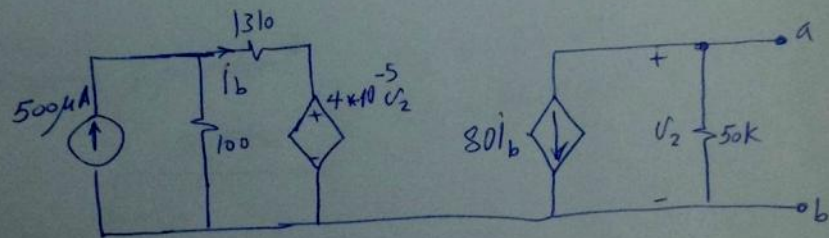

Solution: (Dependent + Independent)

① $V_{th} = V_{o.c}|_{ab}$

Part (A)

$$V_{th} = V_2 = -(80 i_b * 50k) \text{ ----- ①}$$

Part (B)


*Using Mesh current method:

*Apply KVL at i_b :

$$100 (i_b - 500\mu) + 1310 i_b + 4 * 10^{-5} V_2 = 0 \text{ ----- ②}$$

Apply ① in ②: $100 i_b - 0.05 + 1310 i_b + (4 * 10^{-5} * -80 i_b * 50k)$
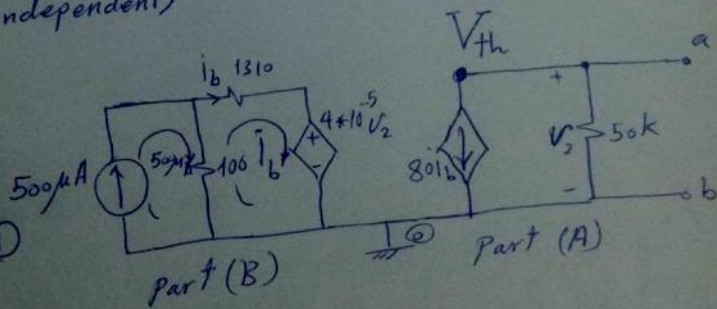
$$\therefore 1250 i_b = 0.05 \quad \therefore i_b = 40 \mu A \quad \therefore V_{th} = -160 \text{ V}$$



② $I_N = I_{s.c} |_{ab}$

Part (A):

$I_N = -80 i_b$


$V_2 = 0$

Part (B):

$\therefore V_2 = 0 \quad \therefore \text{Source } (4 \times 10^{-5} V_2) = 0$

$\therefore i_b = 500 \mu \times \frac{100}{100 + 1310} = 35.461 \mu A$

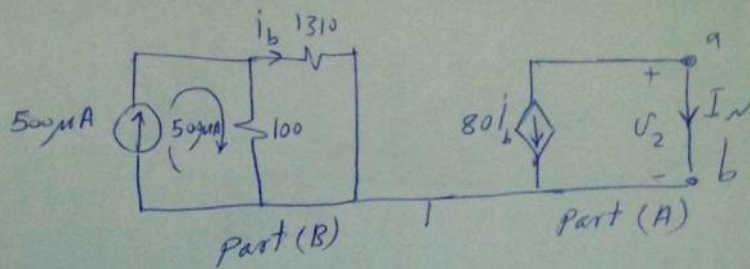
$\therefore I_N = \underline{\underline{-2.8369 \text{ mA}}}$



③ $R_{th} = V_{th} / I_N = \underline{\underline{56.4 \text{ k}\Omega}}$

\therefore Thevenin Equivalent

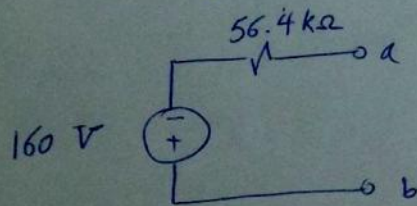$V_{th} = -160 \text{ V}$
 $R_{th} = 56.4 \text{ k}\Omega$




Question (6):

using superposition find i_o :


① Using 6A source and cancel the other ones

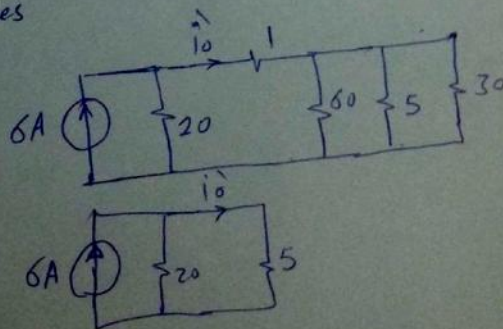$\therefore i_o = 6 \times \frac{20}{20+5} = 4.8 \text{ A}$



② Using 10 A Source
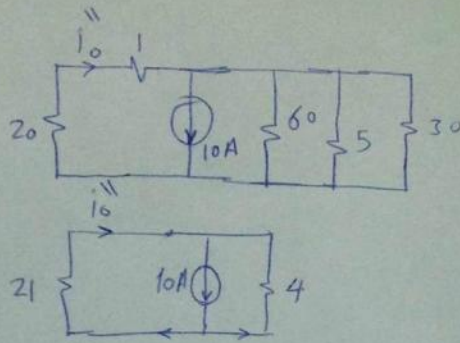
$$\therefore i_o''' = 10 * \frac{4}{4+21} = 1.6 A$$



③ Using 75V Source

using Node Voltage!

$$\frac{V_1}{20} + \frac{V_1}{21} + \frac{V_1 - 75}{30} = 0$$

$$\therefore \frac{3}{2} V_1 + \frac{10}{7} V_1 + V_1 - 75 = 0$$

$$\therefore \frac{55}{14} V_1 = 75 \quad \therefore V_1 = 19.091 V$$

$$\therefore i_o''' = \frac{-V_1}{21} = -0.9091 A$$

$$\therefore \text{From } \textcircled{1}, \textcircled{2}, \textcircled{3} : i_o = i_o' + i_o'' + i_o'''$$


$$\therefore i_o = 5.491 A \quad \dots \text{Req} \neq$$

Question (7):

Saturation occurs when:

$$10 \leq V_o \leq -10$$

$$V_o = \pm V_{CC} = \pm 10 V$$

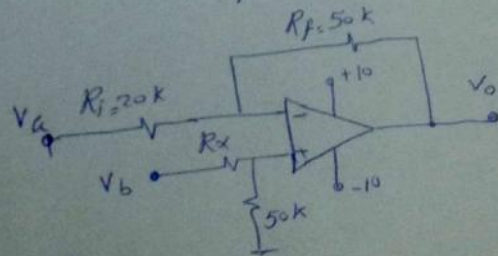

$$V_o = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{50k}{R_x + 50k}\right) V_b - \frac{R_f}{R_i} V_a$$

$$V_o = (1 + 2.5) \left(\frac{50k}{R_x + 50k}\right) V_b - 2.5 V_a$$

$$V_o = \left(\frac{175k}{R_x + 50k}\right) V_b - 2.5 V_a$$

$$\therefore (R_x + 50k) = \frac{175k * V_b}{V_o + 2.5 V_a}$$

$$\therefore R_x = \frac{175k * V_b}{\pm 10 + 2.5 V_a} - 50k$$