




Electronics 1

BSC 113

Summer 2021-2022

Lecture 11

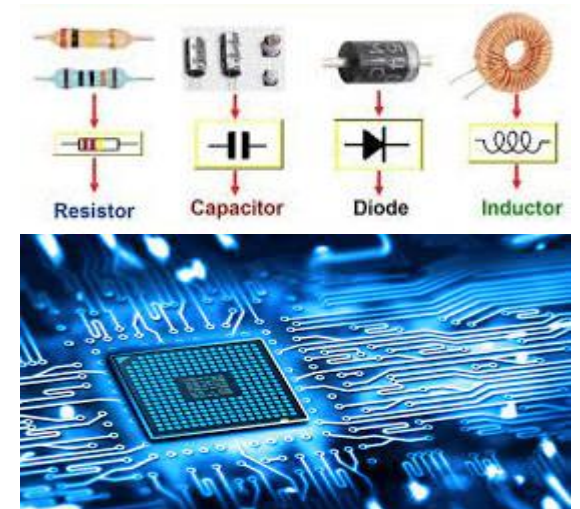

NATURAL AND STEP RESPONSE FOR RL, RC AND RLC CIRCUIT

INSTRUCTOR

DR / AYMAN SOLIMAN

➤ Contents

- 1) Inductors
- 2) Capacitors
- 3) Important characteristics of basic elements
- 4) First order transient circuit
- 5) Second order transient circuit
- 6) SINUSOIDAL STEADY STATE ANALY
- 7) Phasors and sin wave
- 8) Electrical circuit analysis
- 9) Average and RMS




Inductors

- An inductor is a passive element designed to store energy in its magnetic field. Inductors find numerous applications in electronic and power systems.
- They are used in power supplies, transformers, radios, TVs, radars, and electric motors.
- Any conductor of electric current has inductive properties and may be regarded as an inductor. But in order to enhance the inductive effect, a practical inductor is usually formed into a cylindrical coil with many turns of conducting wire



Inductors

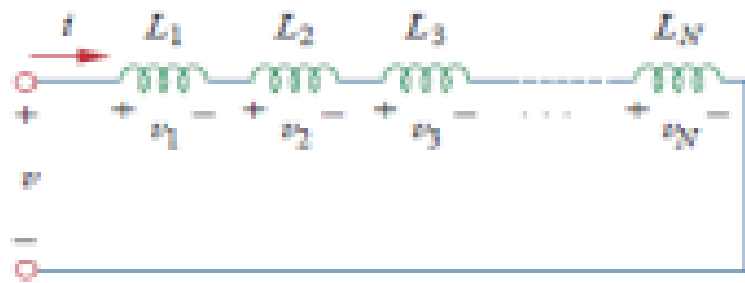



$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt}$$

$$= \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$
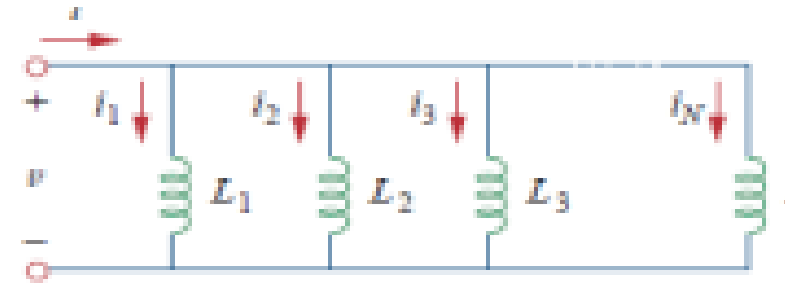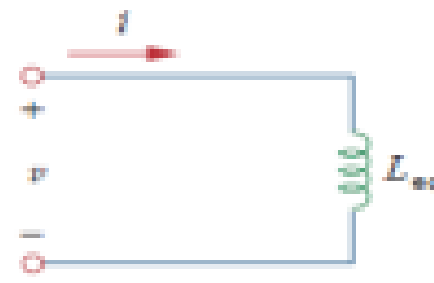
$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



$$i = i_1 + i_2 + i_3 + \dots + i_N$$


$$i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$

$$= \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

Capacitors

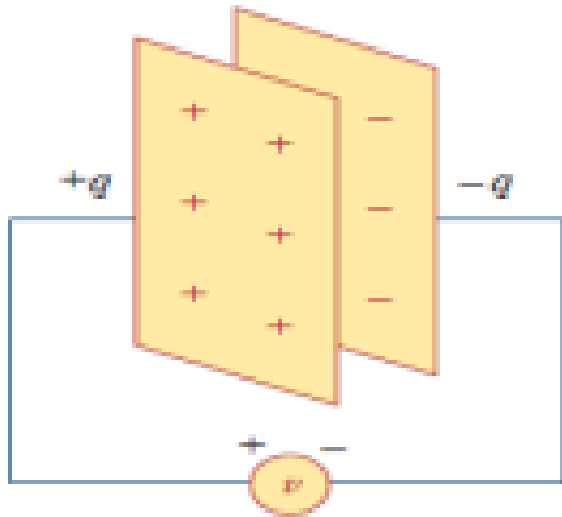
- A capacitor is a passive element designed to store energy in its electric field. Besides resistors, capacitors are the most common electrical components. Capacitors are used extensively in electronics, communications, computers, and power systems.



$$IF= 1C/IV$$

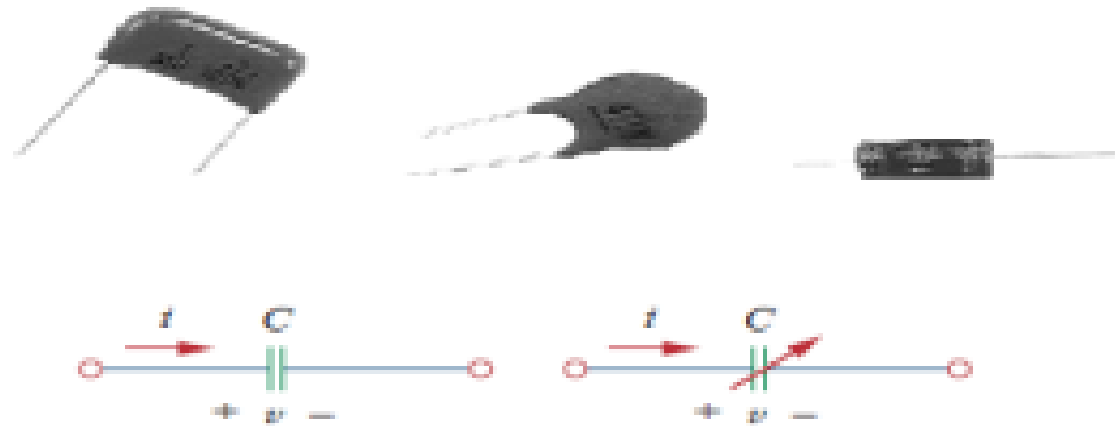

Capacitors

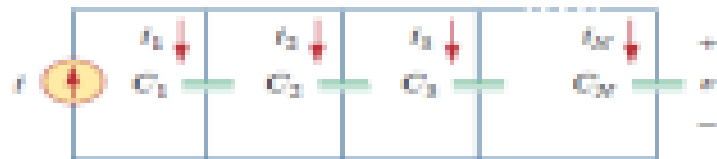


$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$
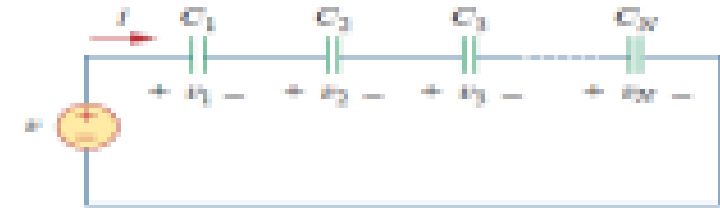
$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$



$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = \frac{1}{C_1} \int_{t_0}^t i(t) dt + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(t) dt + v_2(t_0)$$

$$+ \dots + \frac{1}{C_N} \int_{t_0}^t i(t) dt + v_N(t_0)$$

$$= \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(t) dt + v_1(t_0) + v_2(t_0)$$

$$+ \dots + v_N(t_0)$$

$$= \frac{1}{C_{eq}} \int_{t_0}^t i(t) dt + v(t_0)$$


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

Important characteristics of basic elements

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
$v-i$:	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit

First order transient circuit

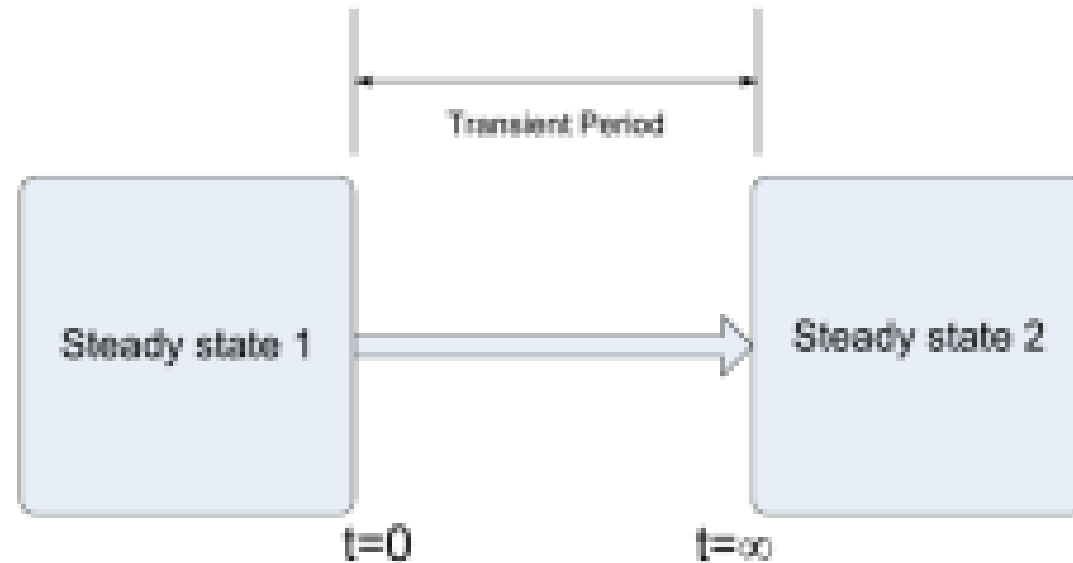
- In this chapter, we shall examine two types of simple circuits: a circuit comprising a **resistor and capacitor** and a circuit comprising a **resistor and an inductor**.
- These are called **RC** and **RL** circuits, respectively.
- A first-order circuit is characterized by a first-order differential equation.



1- Source free R-C circuit

- A source-free RC circuit occurs when its **dc source is suddenly disconnected**.
- The energy already stored in the capacitor is released to the resistors (sometimes called free response).
- This shows that the voltage response of the RC circuit is an exponential decay of the initial voltage.
- Since the response is due to the **initial energy** stored and the **physical characteristics** of the circuit and not due to some external voltage or current source, it is called the **natural response** of the circuit.

1- Source free R-C circuit

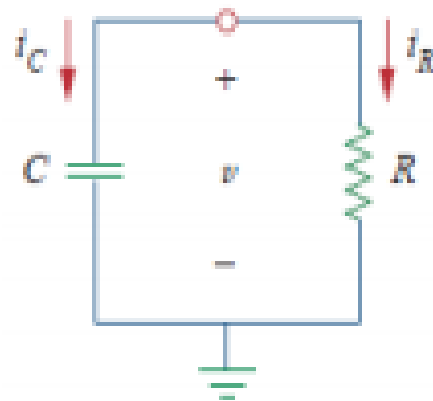

$$v(0) = V_0$$

$$w(0) = \frac{1}{2} CV_0^2$$

$$i_C + i_R = 0$$

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = 0$$

$$\frac{dv}{v} = -\frac{1}{RC} dt$$


$$\ln \frac{v}{A} = -\frac{t}{RC}$$

$$v(t) = Ae^{-t/RC}$$

$$v(t) = V_0 e^{-t/RC}$$


$$\int_0^t \frac{v}{RC} dt = \int_0^t p dt = \int_0^t \frac{V_0^2}{R} e^{-2t/RC} dt$$
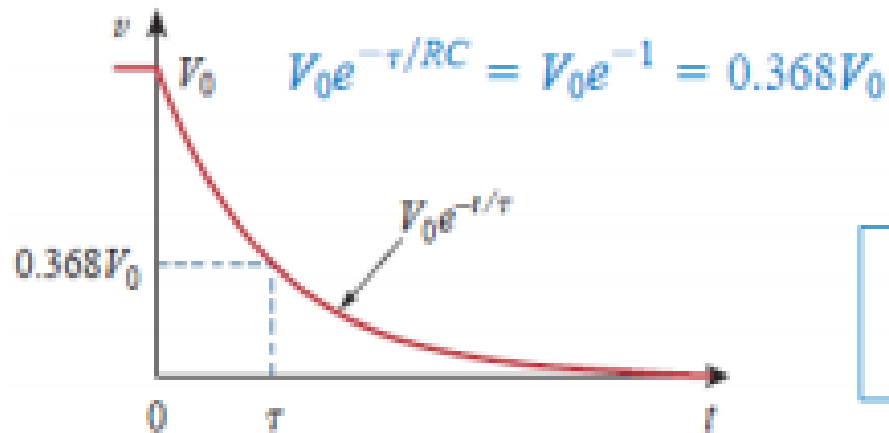
$$-\frac{RC}{2R} e^{-2t/RC} \left[-\frac{1}{2} CV_0^2 (1 - e^{-2t/RC}) \right]$$



$$\tau = RC$$

$$v(t) = V_0 e^{-t/\tau}$$

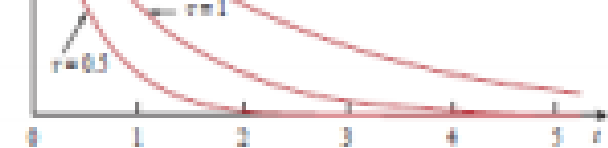

Example

➤ let $V_c(0)=15$, find V_c , V_x and i_x for $t > 0$


$$R_{\text{eq}} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

$$\tau = R_{\text{eq}}C = 4(0.1) = 0.4 \text{ s}$$

$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V}, \quad v_C = v = 15e^{-2.5t} \text{ V}$$


$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$$
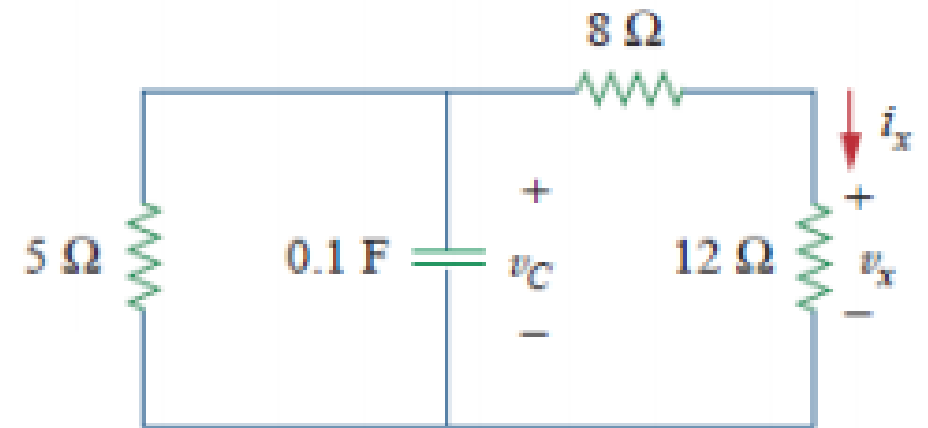
$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$$



2- Forced R-C circuit

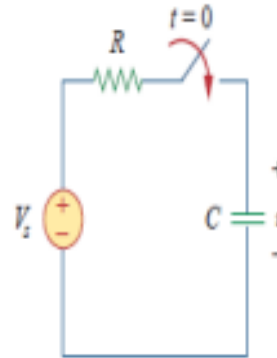- The steady-state response is the behavior of the circuit a long time after an **external excitation** is applied.
- The forced R-C circuit is shown in figure. with **$v(\infty)$** is the **final value of capacitor voltage**.



$$v(0^-) = v(0^+) = V_0$$

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t)$$

$$\frac{dv}{dt} = -\frac{v - V_s}{RC}$$

$$\frac{dv}{v - V_s} = -\frac{dt}{RC}$$

$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = -\frac{t}{RC} \Big|_0^t$$

$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = -\frac{t}{RC} + 0$$

$$\ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC}$$



$$\frac{v - V_s}{V_0 - V_s} = e^{-t/\tau}, \quad \tau = RC$$

$$v - V_s = (V_0 - V_s)e^{-t/\tau}$$

$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$


$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$
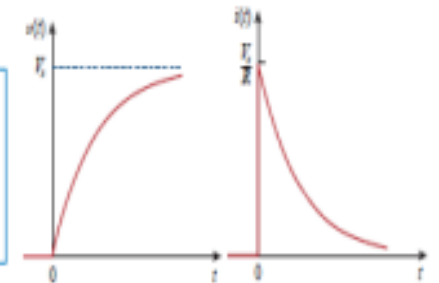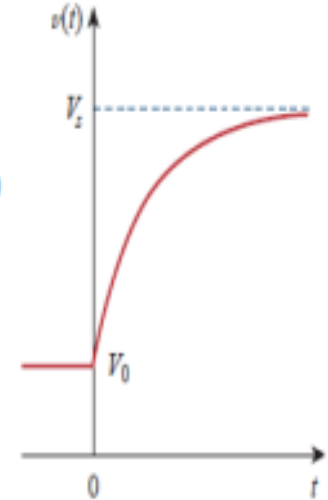
$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$




3- Source free R-L circuit

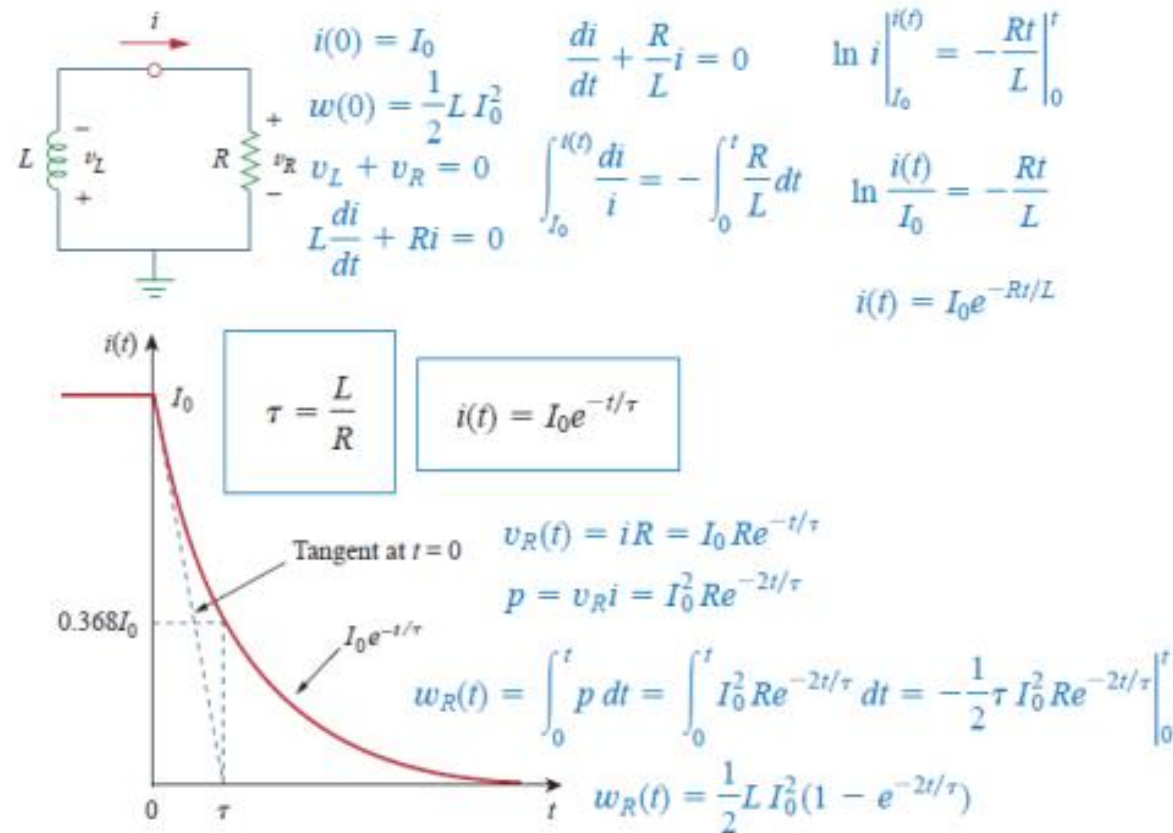- Consider the **series** connection of a **resistor and an inductor**, as shown in Fig.
- Our goal is to determine the circuit response.



4 Forced R-L circuit

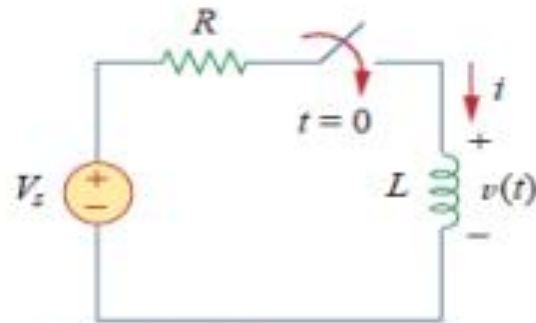- The steady-state response is the behavior of the circuit a long time after an **external excitation** is applied. The forced R-L circuit is shown in figure with $i(\infty)$ is the final value of inductor current.



$$i = i_t + i_{ss}$$

$$i_t = Ae^{-t/\tau}, \quad \tau = \frac{L}{R}$$

$$i_{ss} = \frac{V_s}{R}$$

$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$


$$i(0^+) = i(0^-) = I_0$$

$$I_0 = A + \frac{V_s}{R}$$

$$A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$
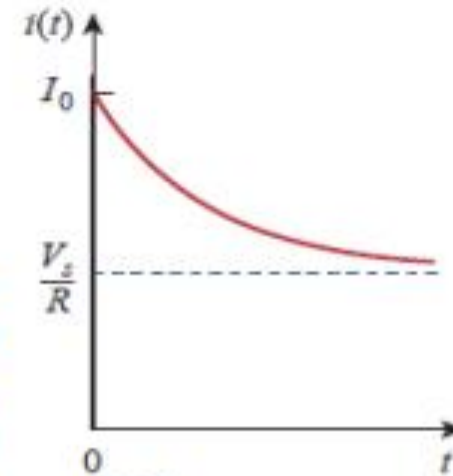
$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$



Example

- Find $i(t)$ in the circuit in the following Fig. for $t > 0$. Assume that the switch has been closed for a long time.

Answer: When $t < 0$ the 3-ohm resistor is short-circuited, and the inductor acts like a short circuit. The current through the inductor is

$$i(0) = \frac{10}{2} = 5A$$

When $t > 0$ the switch is open.


$$i(\infty) = \frac{10}{2 + 3} = 2A$$

The Thevenin resistance across the inductor terminals is

$$R_{Th} = 2 + 3 = 5$$

Thus,

$$i(t) = 2 + 3e^{-15t}A$$

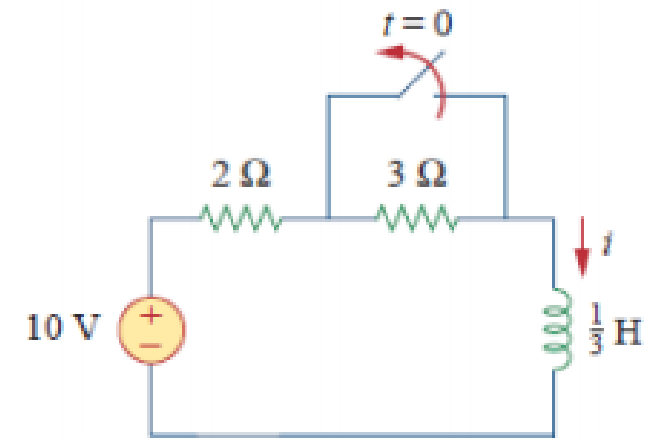


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

Second order transient circuit

- In this chapter we will consider circuits containing **two storage elements**. These are known as **second-order** circuits because their responses are described by differential equations that contain **second derivatives**.
- Typical examples of second-order circuits are **RLC** circuits, in which the three kinds of passive elements are present.
- Examples of such circuits are shown in figure. A second-order circuit is characterized by a second-order differential equation.
- It consists of resistors and the equivalent of two energy storage elements.

Second order transient circuit

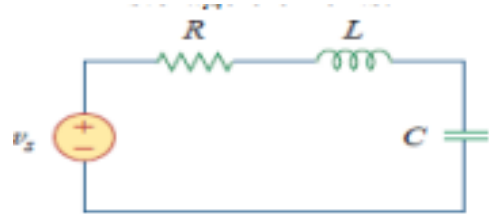

$$v(0) = \frac{1}{C} \int_{-\infty}^0 i dt = V_0$$

$$i(0) = I_0$$

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i dt = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$Ri(0) + L \frac{di(0)}{dt} + V_0 = 0$$

$$\frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0)$$



$$i = Ae^{st}$$

$$As^2 e^{st} + \frac{AR}{L} s e^{st} + \frac{A}{LC} e^{st} = 0$$

$$Ae^{st} \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

SINUSOIDAL STEADY STATE ANALYSIS


1- Phasors and sin wave

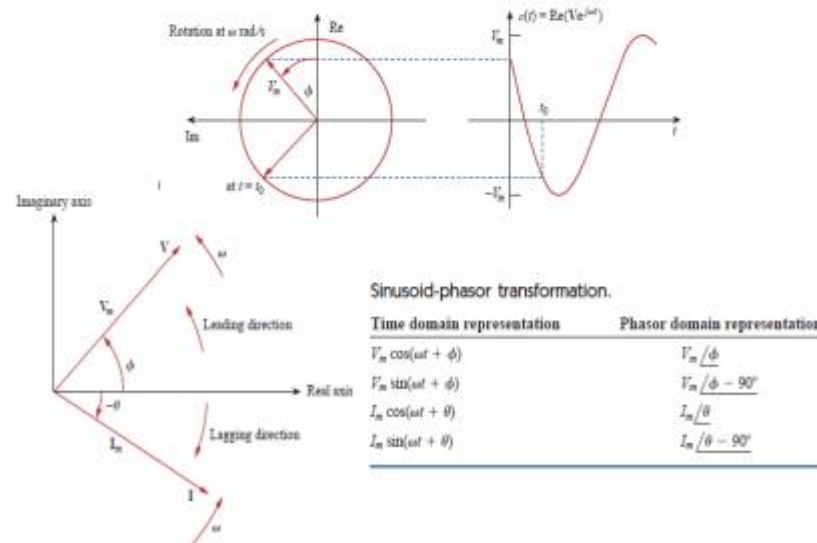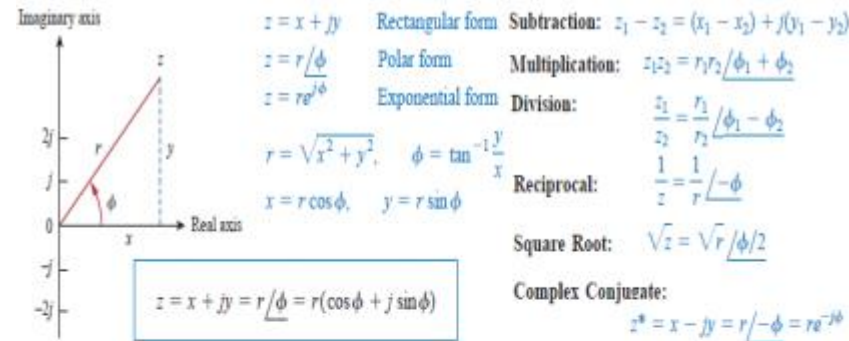- A phasor is a complex number that represents the amplitude and phase of a sinusoid.



2- Electrical circuit analysis

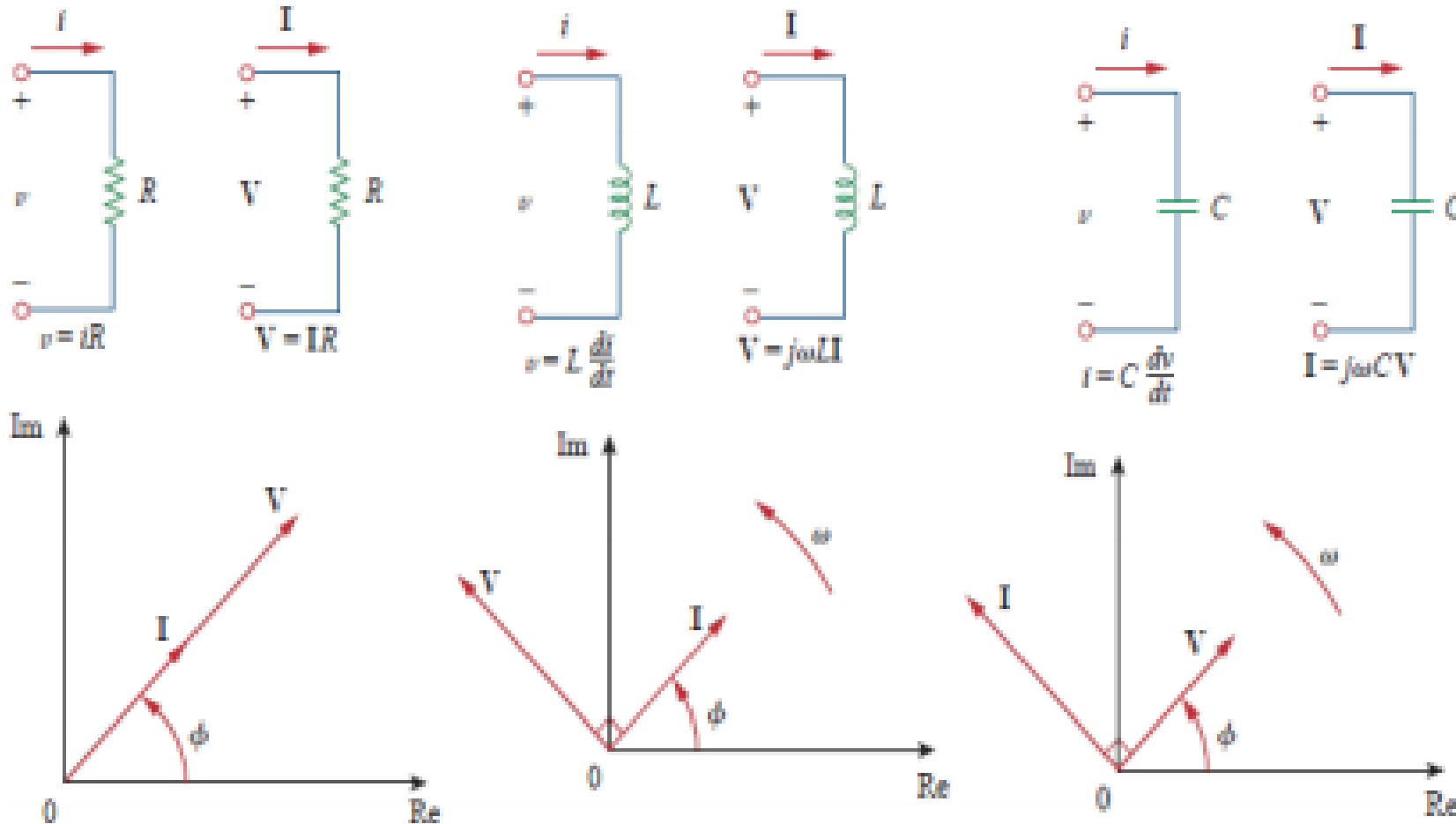➤ Phasor relationships of circuit elements



2- Electrical circuit analysis

- Summary of voltage-current relationships

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

3- Average and RMS


- The two important parameter in electronics calculations is average and root mean square value which are discussed here.

$$v_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

- Given a periodic function , its rms value (or the effective value) is given by

$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Example

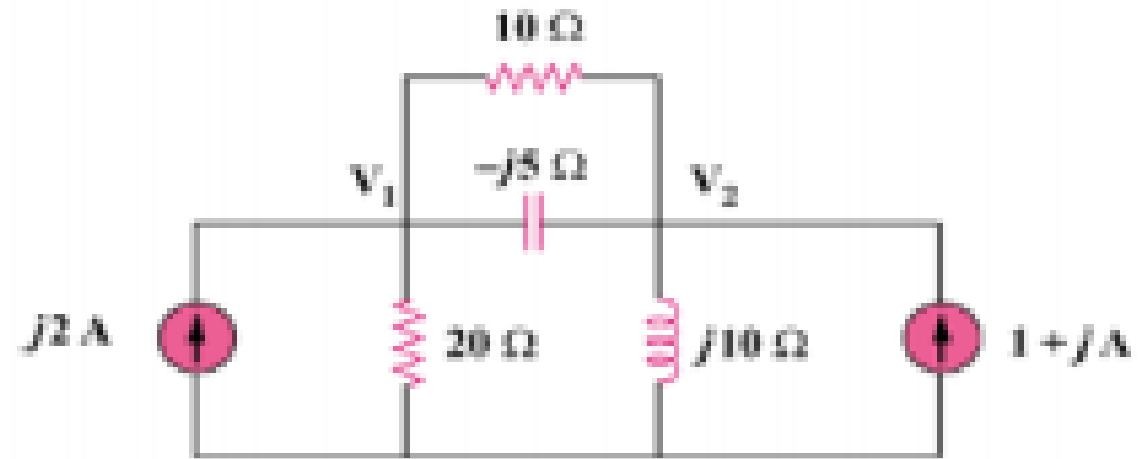

At node 1,


$$j2 = \frac{V_1}{20} + \frac{V_1 - V_2}{10} + \frac{V_1 - V_2}{-j5}$$

$$j40 = (3 + j4)V_1 - (2 + j4)V_2$$

At node 2,

$$\frac{V_1 - V_2}{10} + \frac{V_1 - V_2}{-j5} + 1 + j = \frac{V_2}{j10}$$

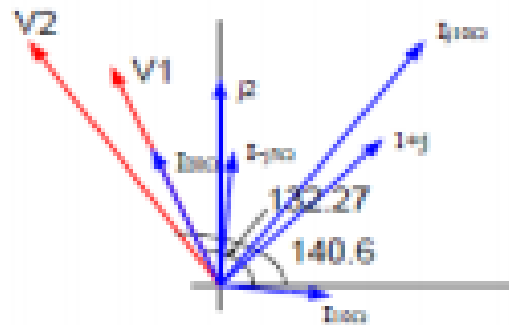
$$10(1 + j) = -(1 + j2)V_1 + (1 + j)V_2$$



$$V_1 = 22.87 \angle 132.27^\circ \text{ V}$$

$$V_2 = 27.87 \angle 140.6^\circ \text{ V}$$

Example

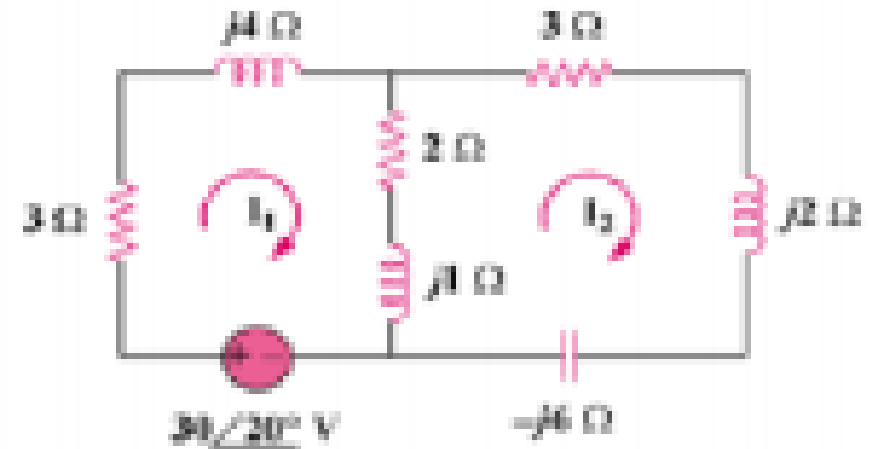

For mesh 1,

$$(5 + j5)I_1 - (2 + j)I_2 - 30\angle 20^\circ = 0$$

$$30\angle 20^\circ = (5 + j5)I_1 - (2 + j)I_2$$


(1)

For mesh 2,

$$(5 + j3 - j6)I_2 - (2 + j)I_1 = 0$$

$$0 = -(2 + j)I_1 + (5 - j3)I_2$$

(2)

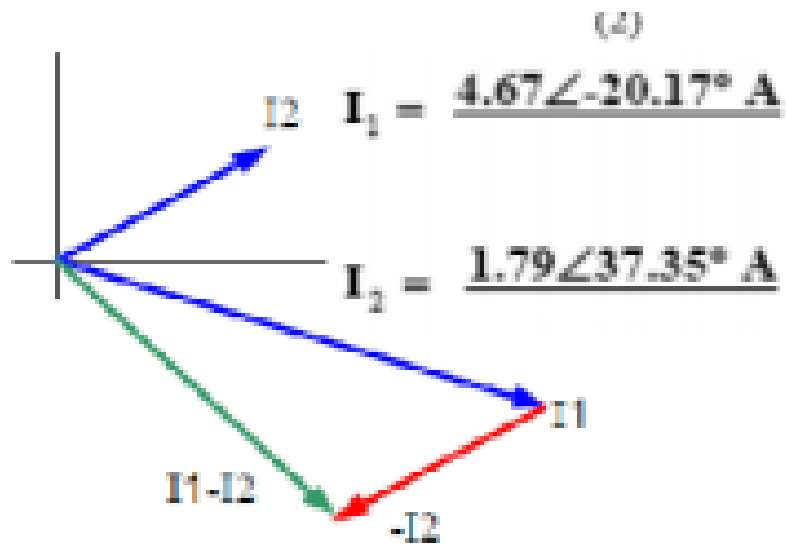

Thank
you

