



Benha University - Benha Faculty of Engineering.
Electro-Mechanical Engineering Program. (Credit Hours System)



Subject: Electronic Devices and Circuits
Subject Code: EME306
Lecturer: *Dr. Ayman Soliman*
TA: *Eng. Ahmed Nasr*

Summer Semester 2022
Sheet No: 1
Date: 16/07/2022

REVIEW QUESTIONS

1. Write short notes about the following items with the aid of formulas and sketches:
 - a. Series and parallel resistor arrangements
 - b. Voltage and current dividers
 - c. Voltage and current sources
 - d. Delivered and consumed power
 - e. Materials used in electronics.
 - f. Semiconductors construction blocks (hint: P-type and n-type)
 - g. PN Junction
 - h. Forward and reverse biasing of a diode

Problems

1.1 Ohm's law relates V, I, and R for a resistor. For each of the situations following, find the missing item:

(a) $R = 1 \text{ k}\Omega$, $V = 10 \text{ V}$ (b) $V = 10 \text{ V}$, $I = 1 \text{ mA}$ (c) $R = 10 \text{ k}\Omega$, $I = 10 \text{ mA}$ (d) $R = 100 \Omega$, $V = 10 \text{ V}$

1.2 Ohm's law and the power law for a resistor relate V, I, R, and P, making only two variables independent. For each pair identified below, find the other two:

	V	I	R	P
a		10m	1k	
b	10	1m		
c	10			1
d		10m		.01
e			1k	1

1.3 If the original resistor is $10 \text{ k}\Omega$, what is the value of the shunting resistor needed to reduce the combined value by 1%, 5%, 10%, and 50%? What is the result of shunting a $10\text{-k}\Omega$ resistor by $1 \text{ M}\Omega$? By $100 \text{ k}\Omega$? By $10 \text{ k}\Omega$?

1.4 You are given three resistors, each of $10\text{ k}\Omega$, and a 9-V battery whose negative terminal is connected to ground. With a voltage divider using some or all of your resistors, how many positive-voltage sources of magnitude less than 9 V can you design? List them in order, smallest first.

1.5 Design a simple current divider that will reduce the current provided to a $1\text{-k}\Omega$ load to 20% of that available from the source.