



Electronic Devices and Circuits

EME306

(Summer 2021-2022)

Lecture 10



Bipolar Junction Transistors (BJTs)


INSTRUCTOR

Dr / Ayman Soliman


➤ Contents

- 1) BJT Simplified Structure
- 2) Transistors Types & symbols
- 3) Modes of Operation
- 4) Applications of regions of operations
- 5) Operation of the NPN Transistor in the Active Mode
- 6) The Emitter Current
- 7) Small signal models



Simplified Structure

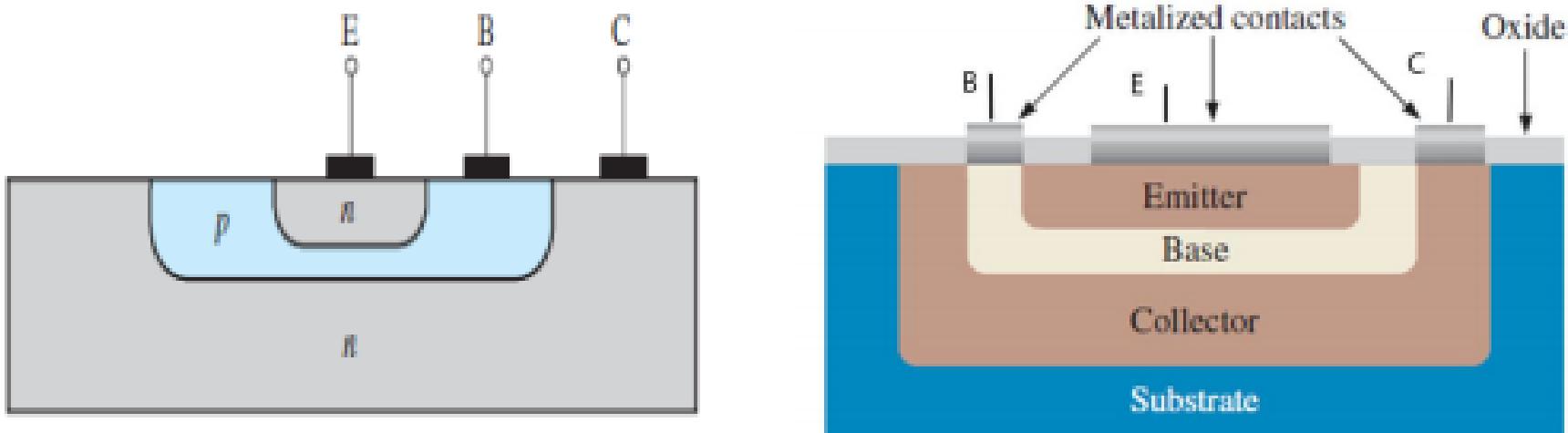

Cross section of an npn BJT.



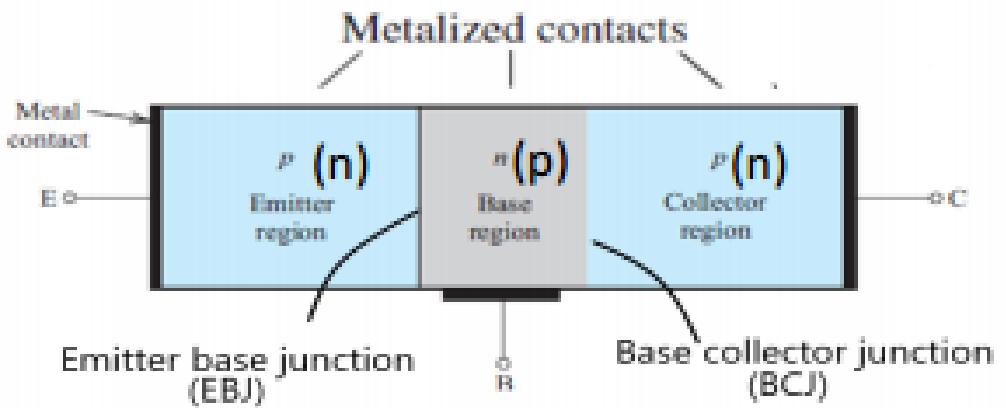


Transistors Types & symbols

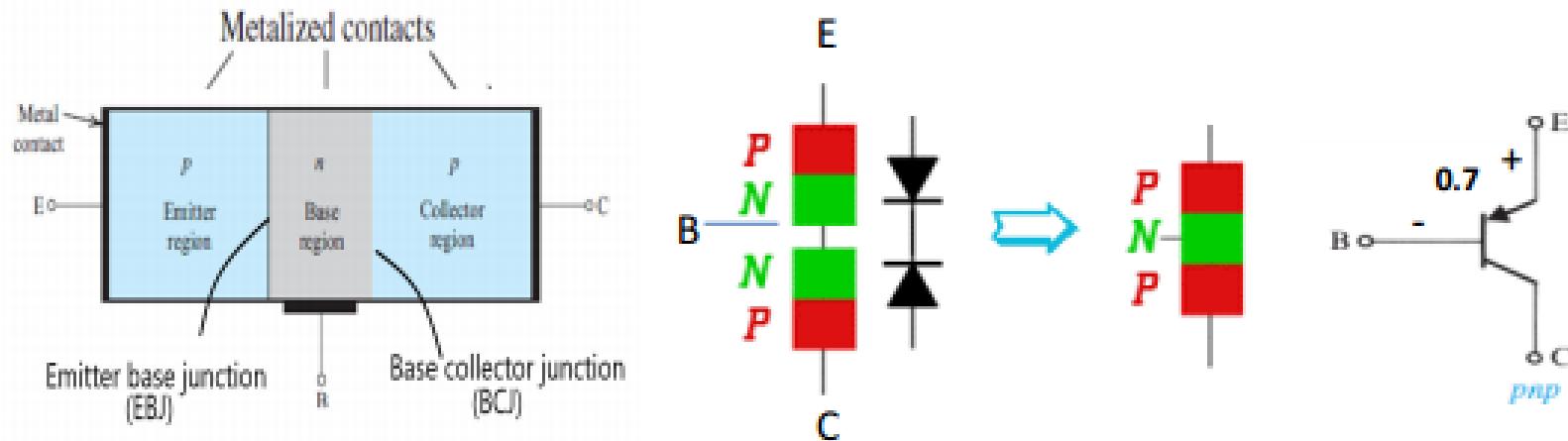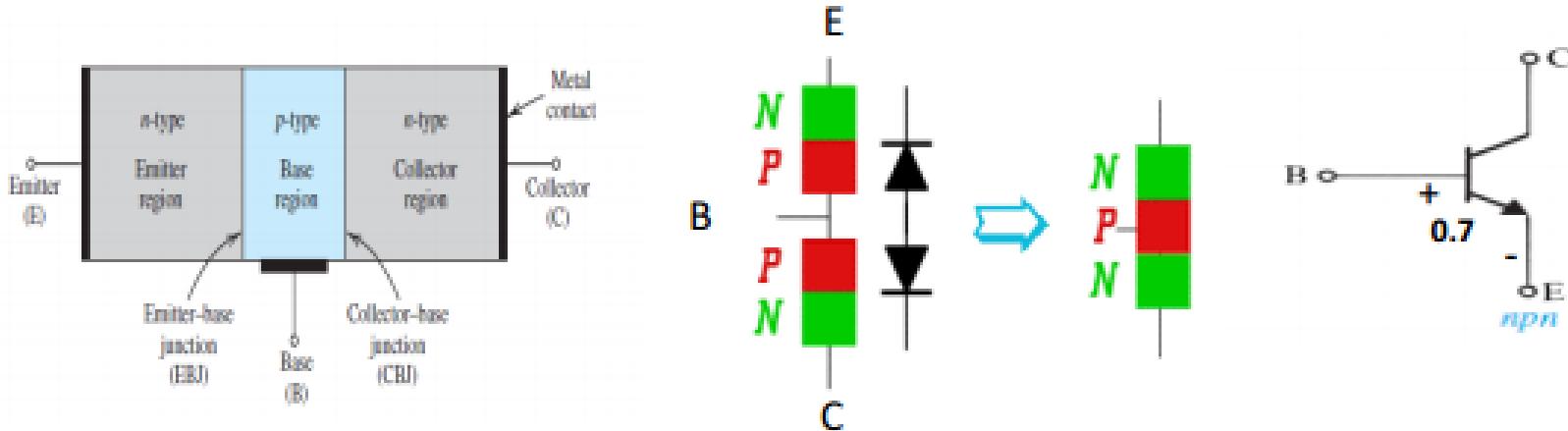

Modes of Operation



For NPN Transistor

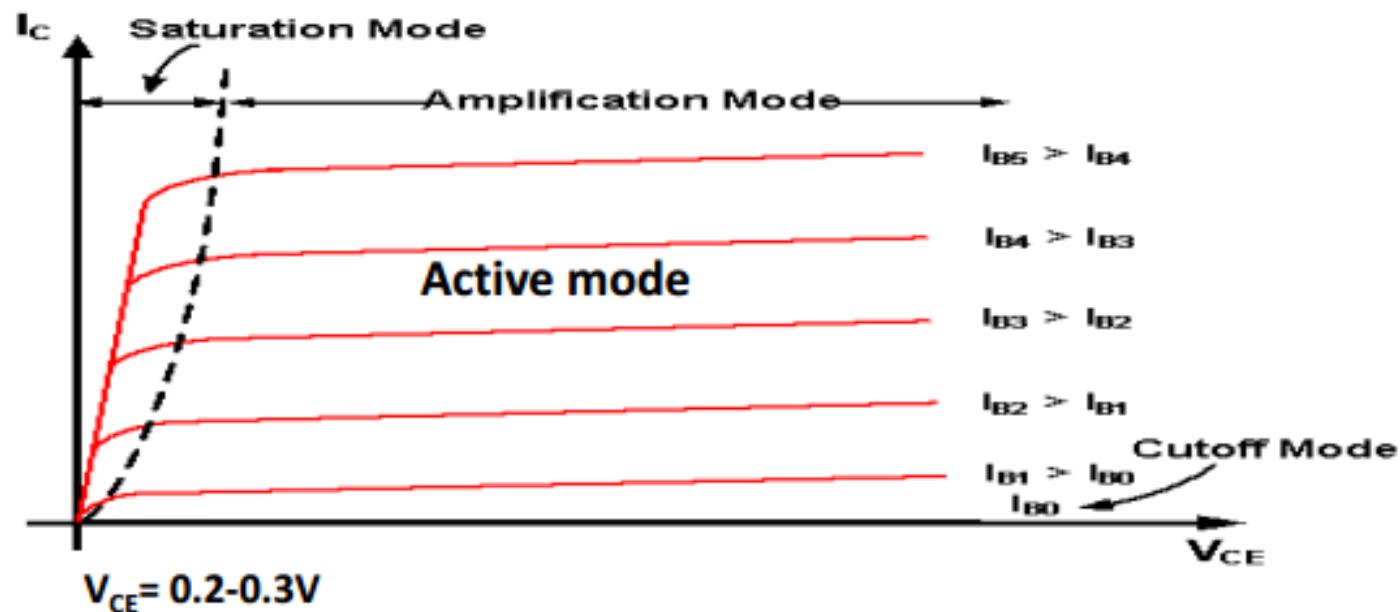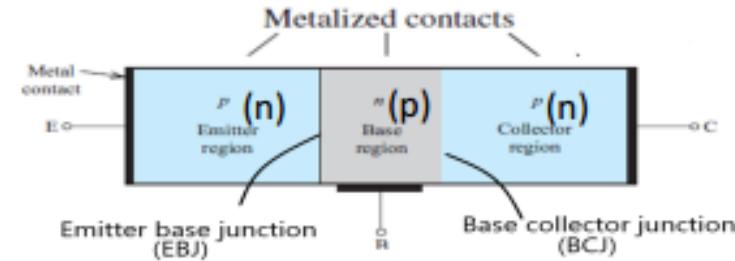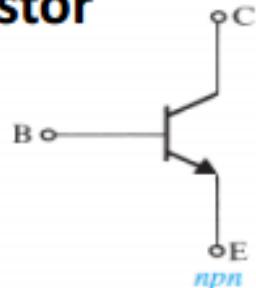

Modes of Operation


BJT Modes of Operation		
Mode	EBJ	CBJ
Active	Forward	Reverse
Saturation	Forward	Forward
Cutoff	Reverse	Reverse

Amplifier
Switch

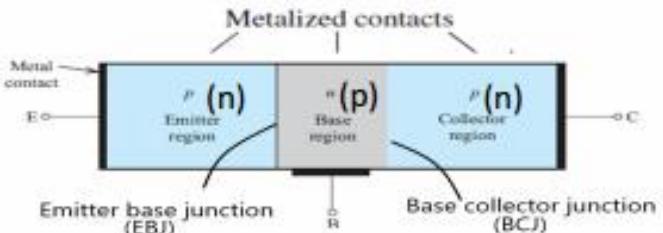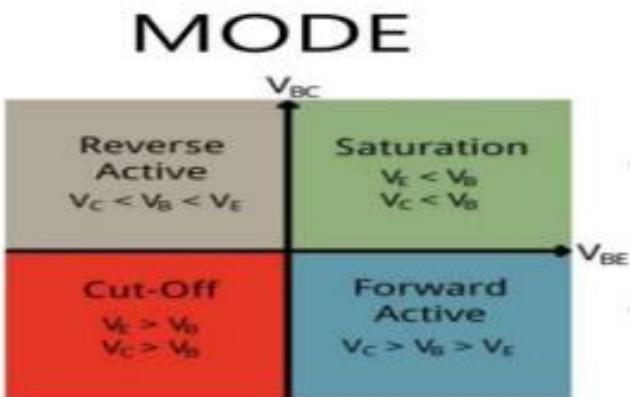


Applications of regions of operations


Amplifier

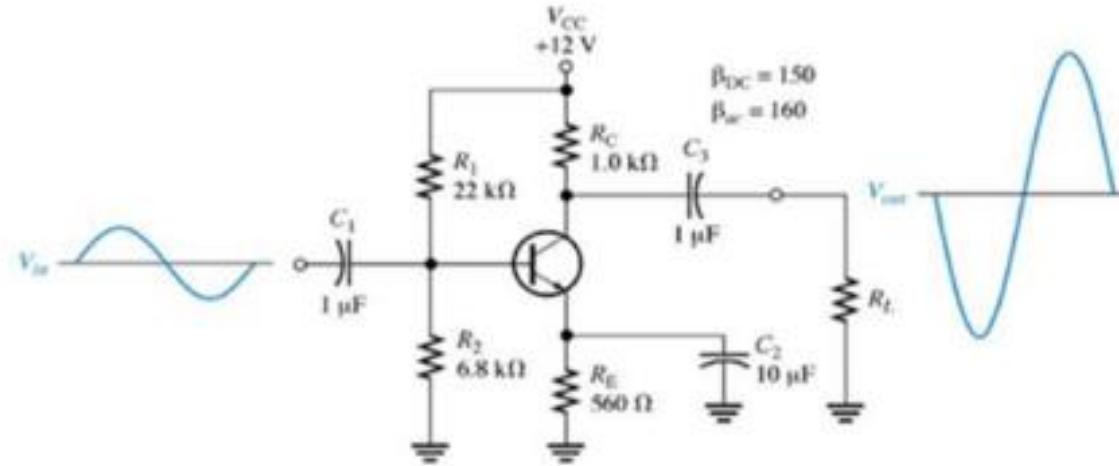

Switch

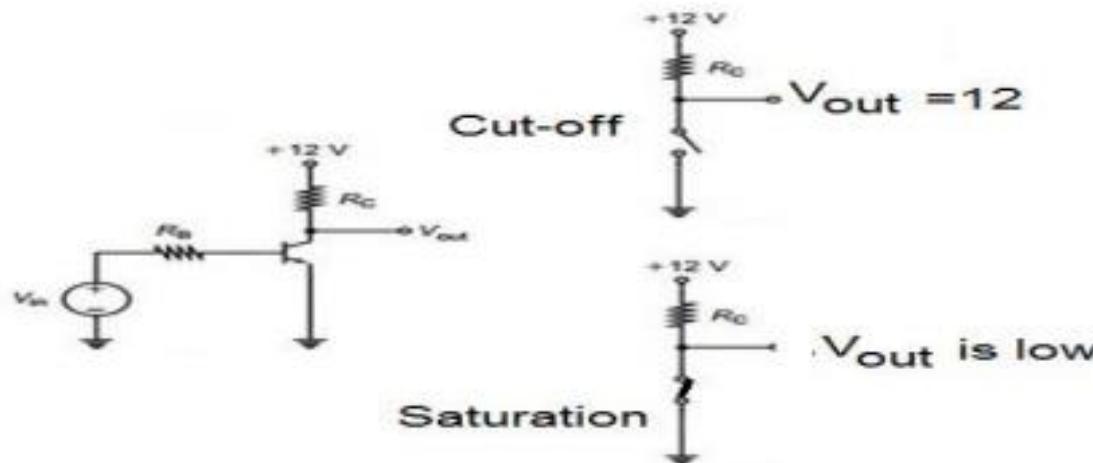

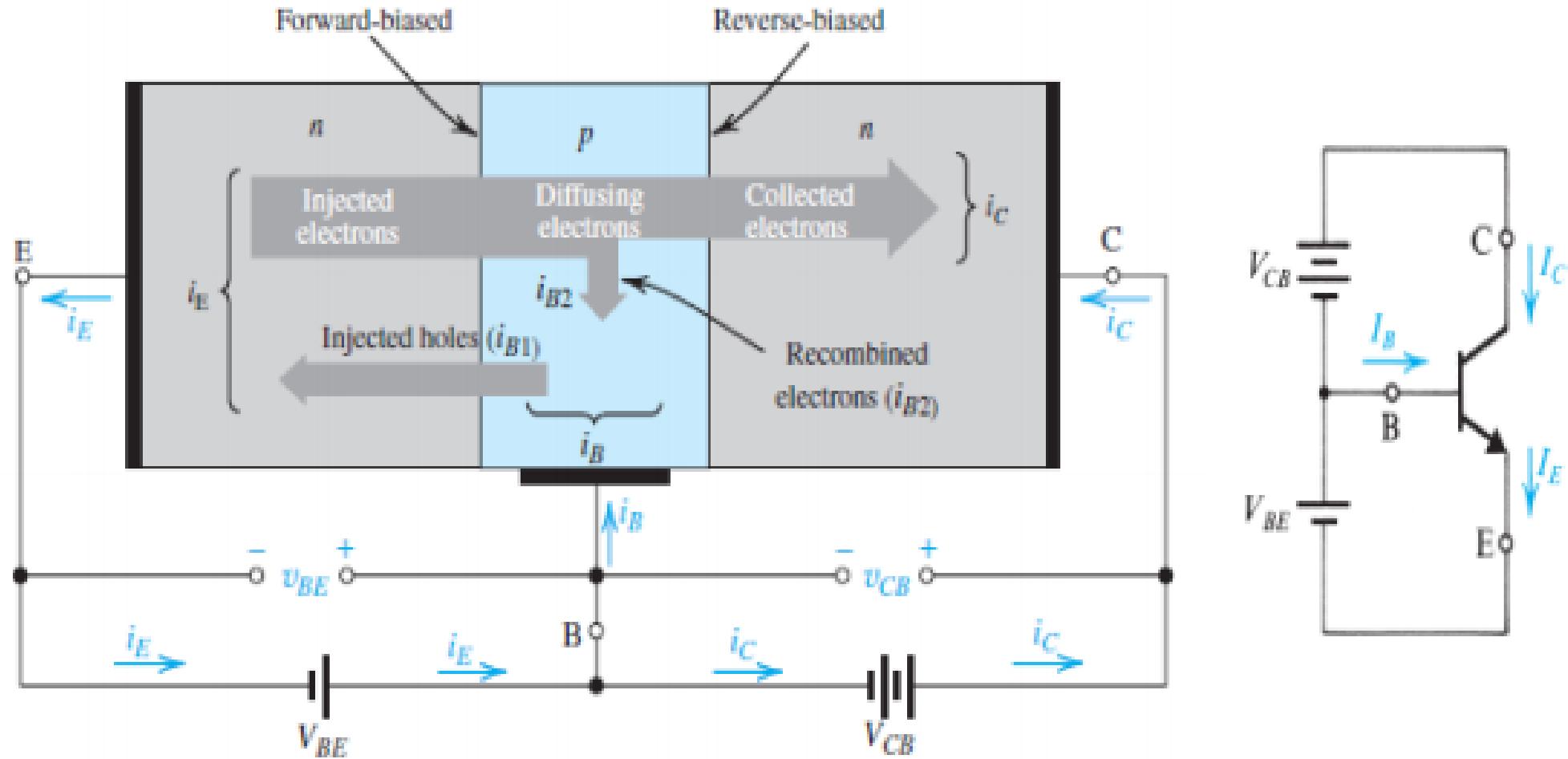Operation of the NPN Transistor in the Active Mode



The Emitter Current

- the emitter current I_E is equal to the sum of the collector current I_C and the base current I_B

$$i_E = i_B + i_C = i_B + \beta i_B = (1 + \beta) i_B = i_C / \alpha$$

$$i_E = \frac{i_C}{\alpha} = \frac{I_s}{\alpha} e^{V_{BE}/V_T}$$

$$I_E > I_C > I_B$$

$$I_C = \beta I_B$$

$$I_E = I_B + I_C = (1 + \beta) I_B$$



$$I_C = \alpha I_E$$

$$\beta = \frac{\alpha}{1 - \alpha}, \quad \beta \gg 1$$

$$\alpha = \frac{\beta}{1 + \beta}, \quad \alpha \ll 1$$

α, β are current gain

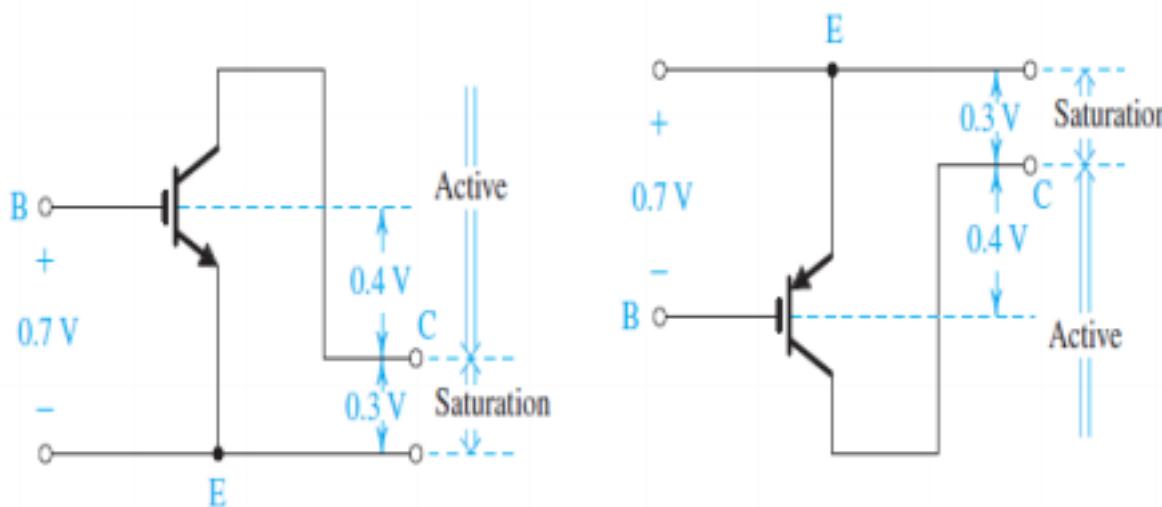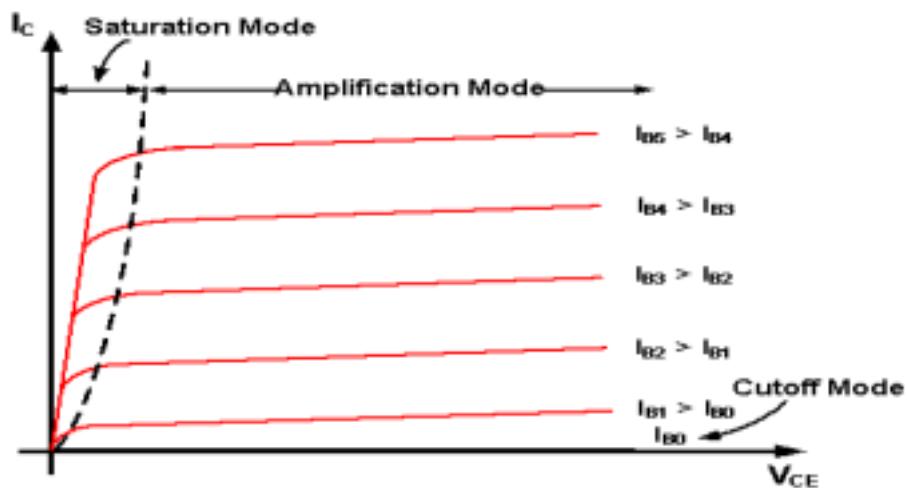V_{EB} and V_{CE} for Active and saturation



Active Region	Saturation Region	Cut off Region
EB junction is forward bias BC Junction is reverse bias	EB junction is forward bias BC Junction is forward bias	EB junction is reverse bias BC Junction is reverse bias
Use α and β $I_E = I_B + I_E = (1 + \beta)I_B$ $I_C = \beta I_B = \alpha I_E$ $\alpha = (\beta / (1 + \beta))$ $\beta = \alpha / (1 - \alpha)$	Use β forced Or β minimum $I_E = I_B + I_E$	$I_B = 0$ $I_E = 0$ $I_C = 0$
$V_{BE} = 0.7 \text{ V for NPN}$ $V_{EB} = 0.7 \text{ V for PNP}$	$V_{BE} = 0.7 \text{ V For NPN}$ $V_{EB} = 0.7 \text{ V for PNP}$ $V_{CE} = 0.2 \text{ V For NPN}$ $V_{EC} = 0.2 \text{ for PNP}$	

Example

The transistor shown in Fig. has $\beta = 100$ and v_{BE} of 0.7 V at $I_C = 1$ mA. Design the circuit so that a current of 2 mA flows through the collector and a voltage of +5 V appears at the collector

Assume transistor operates in Active region

$$R_C = \frac{15 - V_C}{I_C} = \frac{15 - 5}{2mA} = 5K\Omega$$


Since $I_C = 1$ mA at $V_{BE} = 0.7$, then

$$V_{BE2} - V_{BE1} = V_T * \ln(\frac{I_{C2}}{I_{C1}})$$

$$V_{BE2} - 0.7 = 0.025 * \ln(2/1) \quad V_{BE2} = 0.717V \quad V_E = -0.717V$$

$$I_E = I_C / \alpha = 2mA / 100/101 = 2.02mA$$
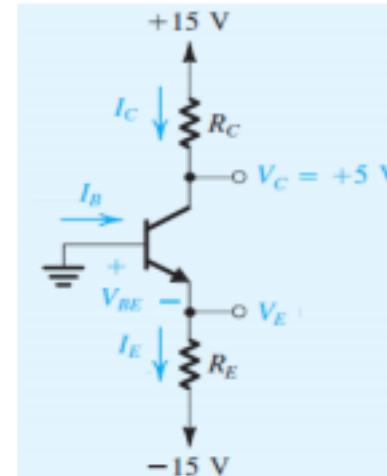
$$R_E = \frac{V_E - V_{EE}}{I_E} = \frac{-0.717 + 15}{2.02} = 7.07K\Omega$$



Check

$$V_E = -0.717, V_B = 0, V_C = 5$$

Since $V_B > V_E$ Then EB_J is Forward

Sine $V_C > V_B$ Then BC_J is reverse

Then Transistor operates in Active Region

Example

For the circuit shown, given $\beta=50$, find all currents and voltages

Assume operate in active

$$V_B = 0, V_E = -0.7 \text{ V}$$

$$I_E = (-0.7 - (-10)) / 10 = 0.93 \text{ mA}$$

$$I_C = \alpha I_E = (50/51) * 0.93 = 0.911764 \text{ mA}$$

$$I_B = I_E / (1 + \beta) = 0.93 / 51 = 0.0182353 \text{ mA}$$

$$V_C = 10 - I_C * R_C = 10 - 0.911764 * 5 = 5.4412 \text{ V}$$

Check

$$V_E = -0.7 \text{ V}, V_B = 0 \text{ V}, V_C = 5.44 \text{ V}$$



Since $V_B > V_E$

Then EB_J is Forward

Since $V_C > V_B$

Then BC_J is reverse

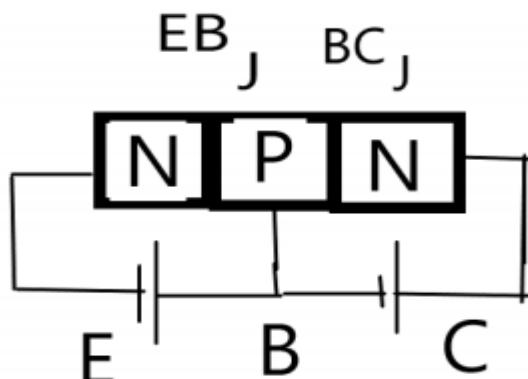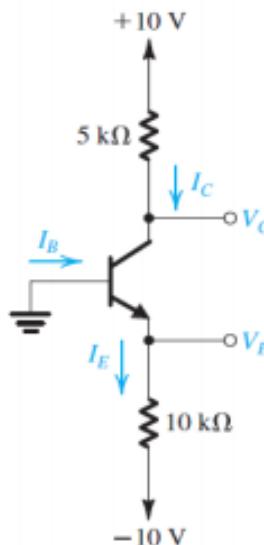Then Transistor operates in Active Region as assumed



Example

In the circuit shown , measurement indicates V_B to be +1.0 V. What are α and β for this transistor?
What voltage V_C do you expect at the collector

Assume operate in active

$$V_B = 1, V_E = V_B + 0.7 = 1.7 \text{ V}$$

$$I_E = (10 - V_E)/5 = (10 - 1.7)/5 = 1.66 \text{ mA}$$


$$I_B = V_B/R_B = 1.0/100 = 0.01 \text{ mA}$$

$$I_C = I_E - I_B = 1.66 - 0.01 = 1.65 \text{ mA}$$

$$\beta = I_C / I_B = 1.65 / 0.01 = 165$$

$$\alpha = (\beta / 1 + \beta) = 165 / 166 = 0.99397$$
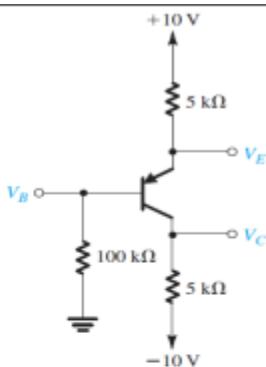
$$V_C = I_C * R_C - 10 = 1.65 * 5 - 10 = -1.75 \text{ V}$$



Check

$$V_E = 1.7 \text{ V}, V_B = 1 \text{ V}, V_c = -1.75 \text{ V}$$


Since $V_E > V_B$

Then EB_J is Forward

Sine $V_B > V_c$

Then BC_J is reverse

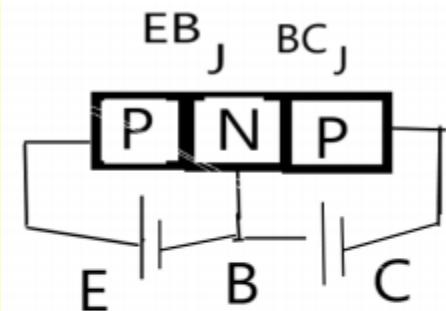Then Transistor operates in Active Region as assumed



Example

Consider the circuit shown, β is specified to be 100. find all node voltages and currents

Assume operate in active


$$V_B = 4\text{ V}, V_E = 4 - 0.7 = 3.3 \text{ V}$$

$$I_E = (3.3 - 0) / 3.3 = 1.0 \text{ mA}$$

$$I_C = \alpha I_E = (100/101) * 1.0 = 0.9901 \text{ mA}$$

$$I_B = I_E / (1 + \beta) = 1.0 / 101 = 0.009901 \text{ mA}$$
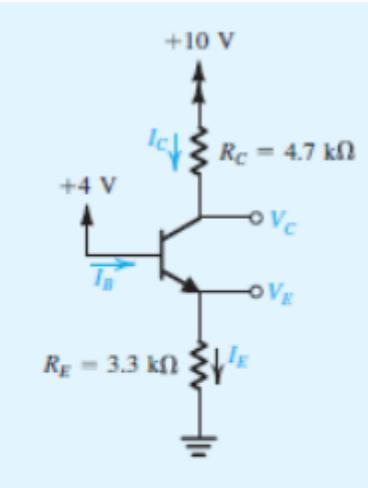
$$V_C = 10 - I_C * R_C = 10 - 0.9901 * 4.7 = 5.34653 \text{ V}$$



Check

$$V_E = 3.3 \text{ V}, V_B = 4 \text{ V}, V_C = 5.34653 \text{ V}$$


Since $V_B > V_E$

Then EB_J is Forward

Sine $V_C > V_B$

Then BC_J is Reverse

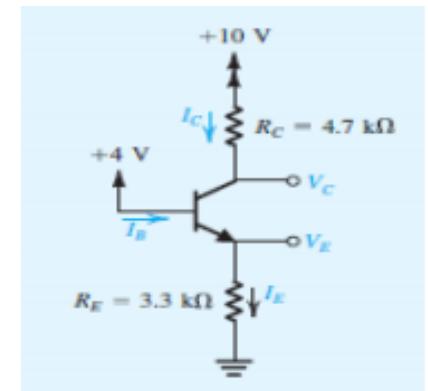Then Transistor operates in active region
as assumed



Example

Consider the circuit shown, β is specified to be 100. find all node voltages and currents

Assume operate in active

$$V_B = 6\text{ V}, V_E = 6 - 0.7 = 5.3 \text{ V}$$

$$I_E = (5.3 - 0) / 3.3 = 1.6061 \text{ mA}$$

$$I_C = \alpha I_E = (100/101) * 1.6061 = 1.59016 \text{ mA}$$

$$I_B = I_E / (1 + \beta) = 1.6061 / 101 = 0.015902 \text{ mA}$$

$$V_C = 10 - I_C * R_C = 10 - 1.59016 * 4.7 = 2.52625 \text{ V}$$

Check

$$V_E = 5.3 \text{ V}, V_B = 6 \text{ V}, V_C = 2.52625 \text{ V}$$



Since $V_B > V_E$

Then EB_J is Forward

Sine $V_B > V_C$

Then BC_J is forward

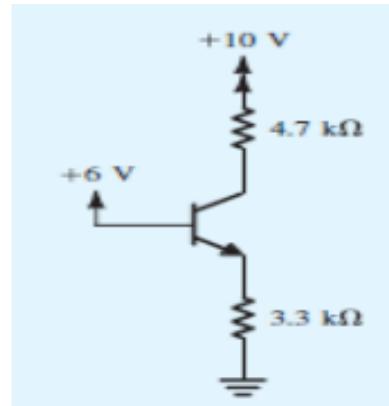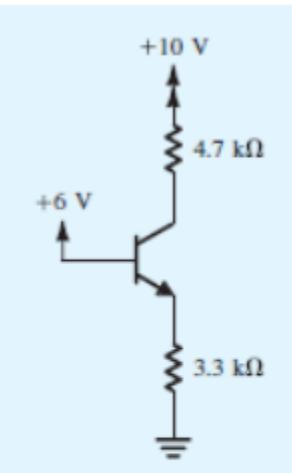
Then Transistor operates in saturation Region



So, the transistor operates in Saturation region

$$V_B = 6\text{ V}, V_E = 6 - 0.7 = 5.3 \text{ V}$$
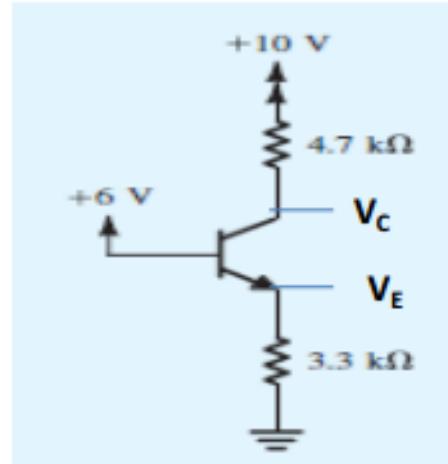
$$I_E = (5.3 - 0) / 3.3 = 1.6061 \text{ mA}$$



$$\text{Since } V_{CE} = 0.2 \text{ V, then } V_C = V_E + 0.2 = 5.3 + 0.2 = 5.5 \text{ V}$$

$$I_C = (10 - 5.5) / 4.7 = 0.95744 \text{ mA}$$

$$I_B = I_E - I_C = 1.6061 - 0.95744 = 0.64866 \text{ mA}$$

$$B_{\text{forced}} = I_C / I_B = 0.95744 / 0.64855 = 1.476$$

Example

Consider the circuit shown, β is specified to be 100. find all node voltages and currents

Assume operate in active

$$V_B = 0 \text{ V}$$

$$V_E = 0 - 0.7 = -0.7 \text{ V}$$

$$I_E = (-0.7 - 0) / 3.3 = -0.5263 \text{ mA}$$


The current pass in reverse direction, so transistor is in cut off

Then $I_C = 0$, $I_B = 0$, $I_E = 0$

$$V_C = 10.0 \text{ V}$$

$$V_B = 0.0 \text{ V}$$

$$V_E = 0.0 \text{ V}$$

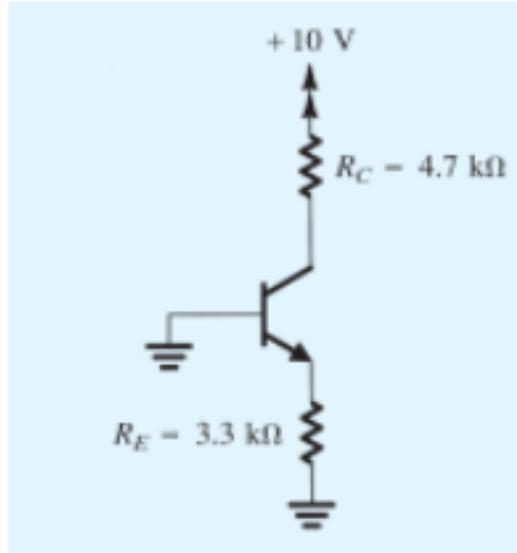

Example

Consider the circuit shown,

$$\beta_{\text{minimum}} = 30$$

.find all node voltages and currents

Assume operate in saturation

$$V_{EC} = 0.2V, V_{EB} = 0.7$$

$$V_E = V_C + 0.2, V_B = V_E - 0.7 = V_C - 0.5$$


$$I_E = I_B + I_C$$

$$\frac{5 - V_E}{1} = \frac{V_B - 0}{10} + \frac{V_C + 5}{10}$$

$$\frac{5 - V_c - 0.2}{1} = \frac{V_c - 0.5}{10} + \frac{V_c + 5}{10}$$

$$V_c = 3.625V, V_B = 3.125V, V_E = 3.825V$$
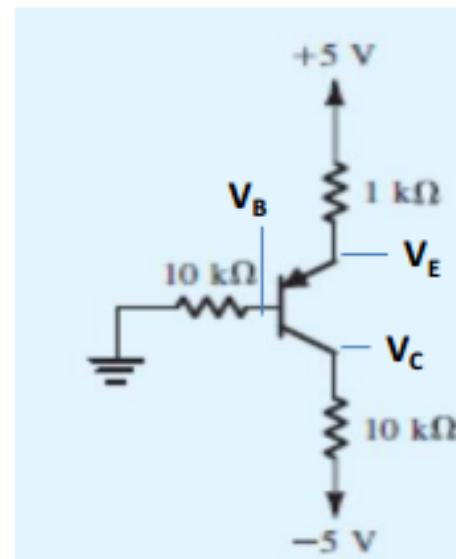
$$I_c = 0.8625mA, I_B = 0.3125mA, I_E = 1.175mA$$



$$V_c = 3.625V, V_B = 3.125V, V_E = 3.825V$$

Check

$$V_E = 3.825V, V_B = 3.125V, V_c = 3.625V$$

Since $V_E > V_B$

Then EB_J is Forward


Sine $V_c > V_B$

Then BC_J is forward

Then Transistor operates in saturation Region

$$B_{\text{forced}} = I_c / I_B = 0.8625 / 0.3125 = 2.76$$

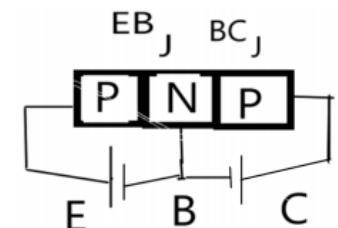Which is much smaller than B_{minimum} given



Example

Determine the voltages at all nodes and the currents through all branches. Assume $\beta = 100$

Assume operate in active

$$V_{th} = 15 * 50 / (100 + 50) = 5 \text{ V}$$

$$R_{th} = (100 * 50) / (100 + 50) = 33.33 \text{ k}\Omega$$

$$5 = I_B * R_B + 0.7 + I_E * R_E$$

$$5 = I_B * R_B + 0.7 + I_B(1 + \beta) * R_E$$

$$5 = I_B * 33.33 + 0.7 + I_B(1 + 100) * 3$$

$$I_B = 0.012785 \text{ mA}$$



$$I_C = 1.2785 \text{ mA}$$

$$I_E = 1.29129 \text{ mA}$$

$$V_E = I_E * R_E = 3.87387 \text{ V}$$

$$V_B = V_E + 0.7 = 4.57387 \text{ V}$$
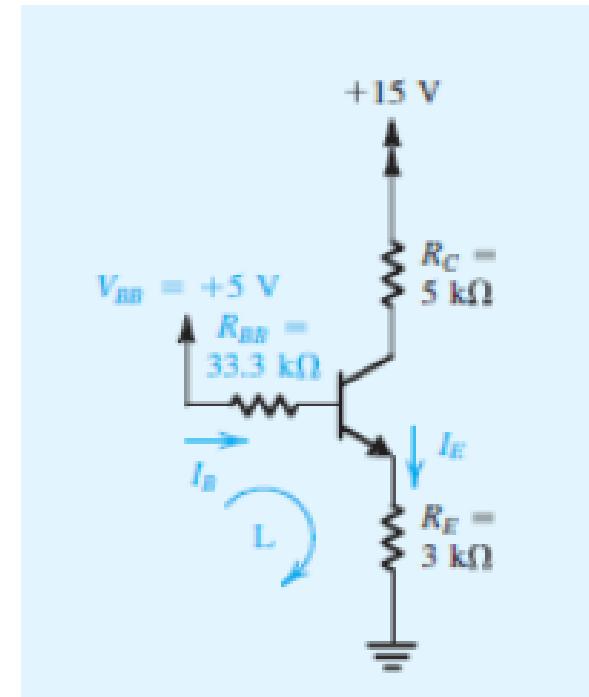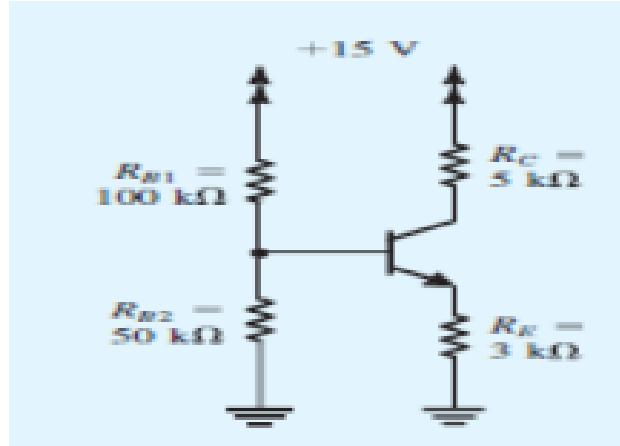
$$V_C = 15 - I_C * R_C = 15 - 1.2785 * 5 = 8.61 \text{ V}$$




Small signal models


**Hybrid- π
Model**

T Model

Hybrid- π Model

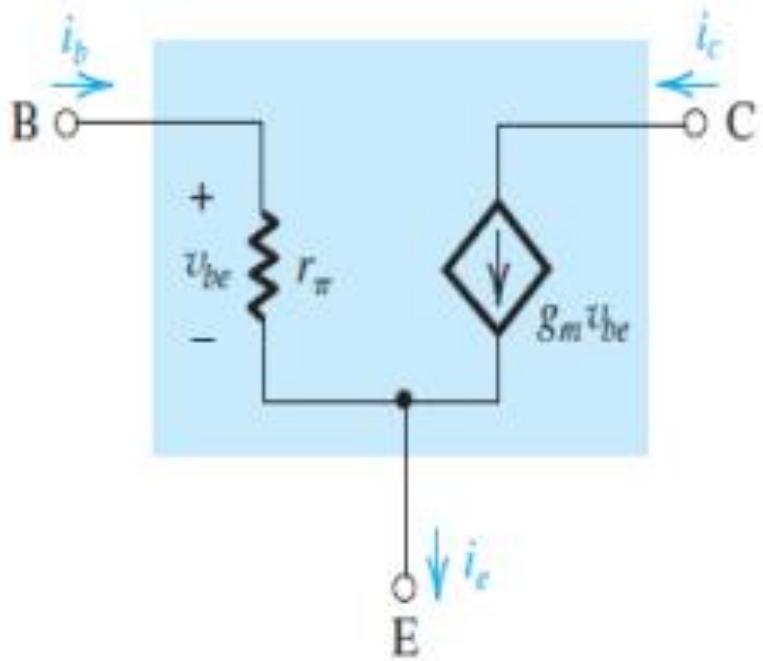

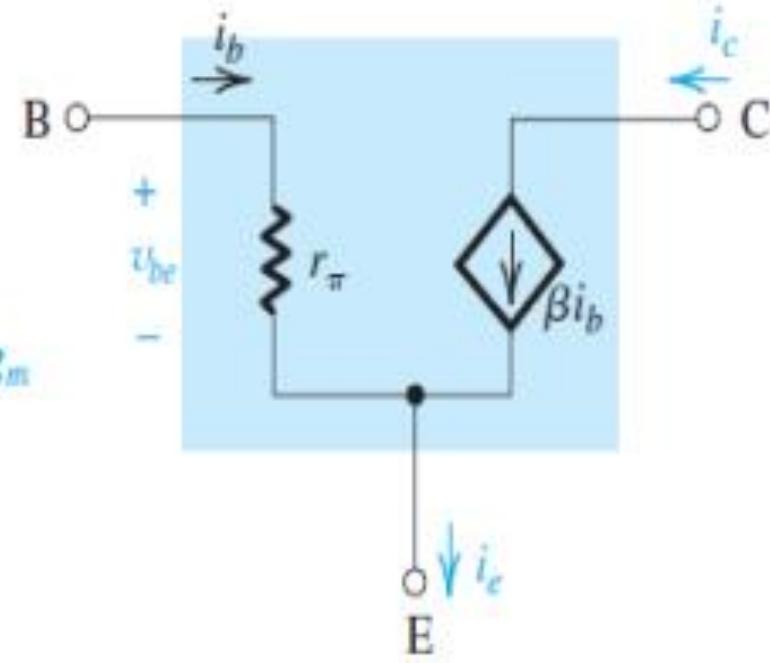
$$g_m = I_C / V_T$$
$$r_\pi = V_T / I_B = \beta / g_m$$



$$g_m v_{be} = g_m (i_b r_\pi)$$
$$= (g_m r_\pi) i_b = \beta i_b$$

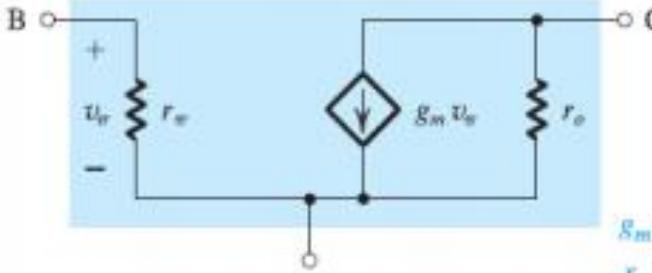The Hybrid- π Model take ro into consideration




(a)

$$g_m = I_C/V_T$$



$$r_\pi = V_T/I_B = \beta/g_m$$

$$r_o = V_A/I_C$$

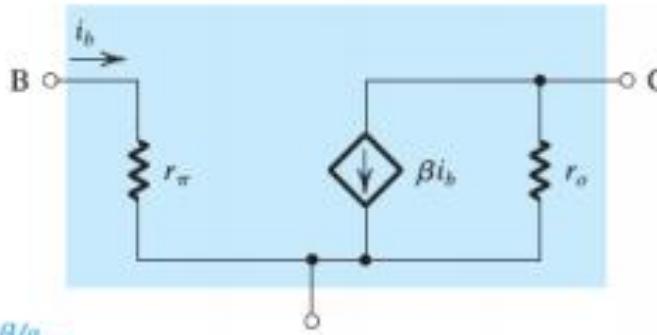


(b)


$$r_o = \frac{V_A}{I_C}$$

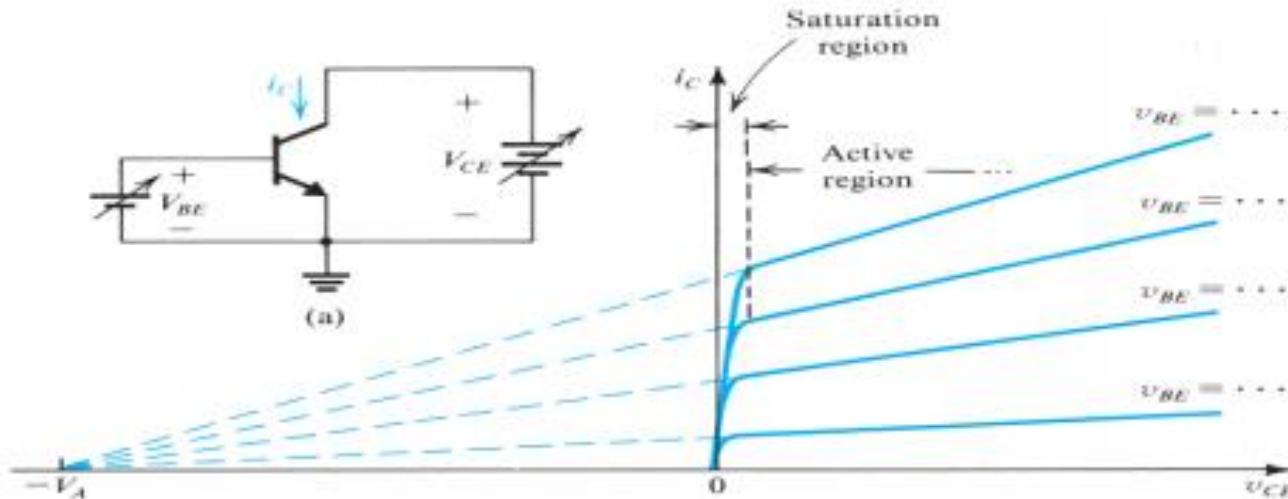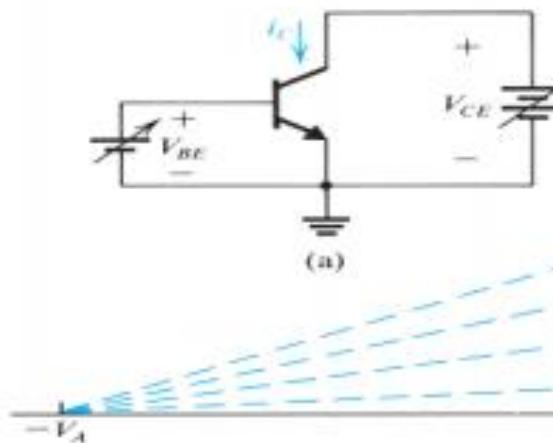

The T Model

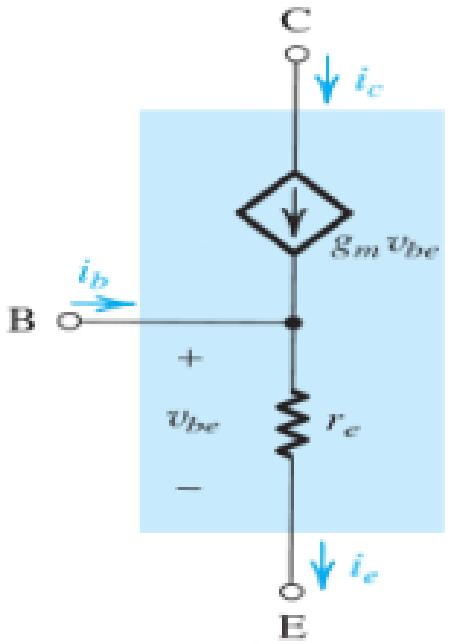

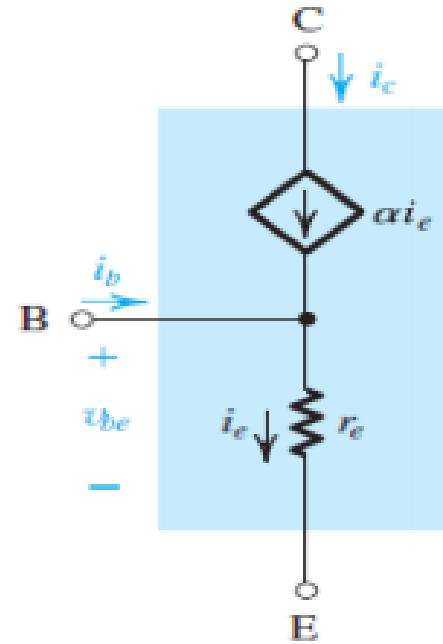
$$g_m = I_C/V_T$$
$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$



$$\begin{aligned} g_m v_{be} &= g_m (i_e r_e) \\ &= (g_m r_e) i_e = \alpha i_e \end{aligned}$$


The T Model take ro into consideration

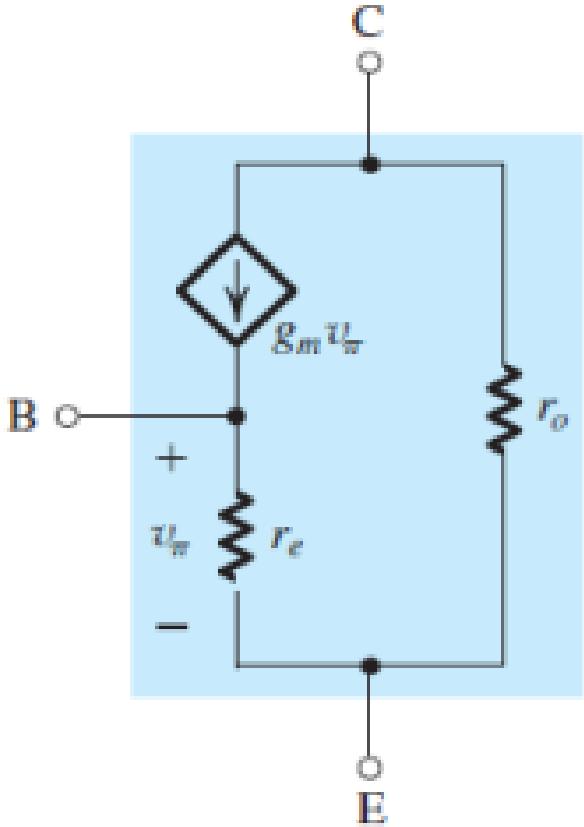

$$g_m = I_C / V_T$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$

$$r_o = V_A / I_C$$

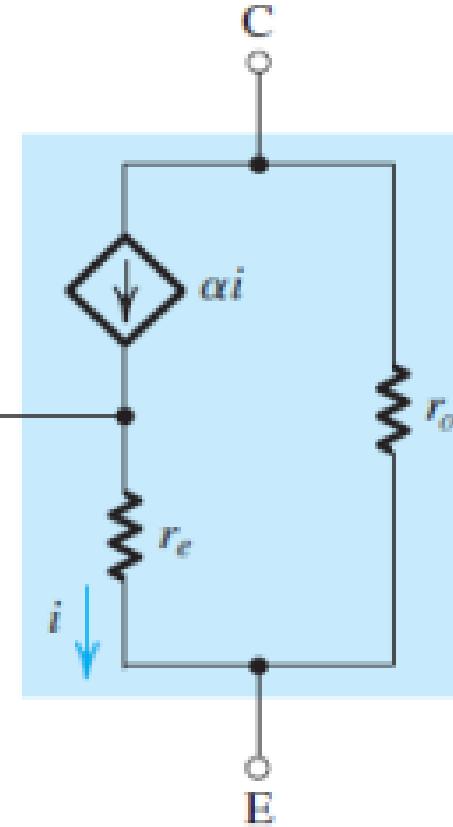

*Thank
you*

