



**Electronic Devices and Circuits**

**EME306**

**(Summer 2021-2022)**

**Lecture 12**



## **BJT as Amplifier Circuits**


**INSTRUCTOR**

**Dr / Ayman Soliman**


## ➤ Contents

- 1) The Three Basic Configurations
- 2) Common Emitter
- 3) Common-Emitter Amplifier with Emitter Resistance


# The Three Basic Configurations

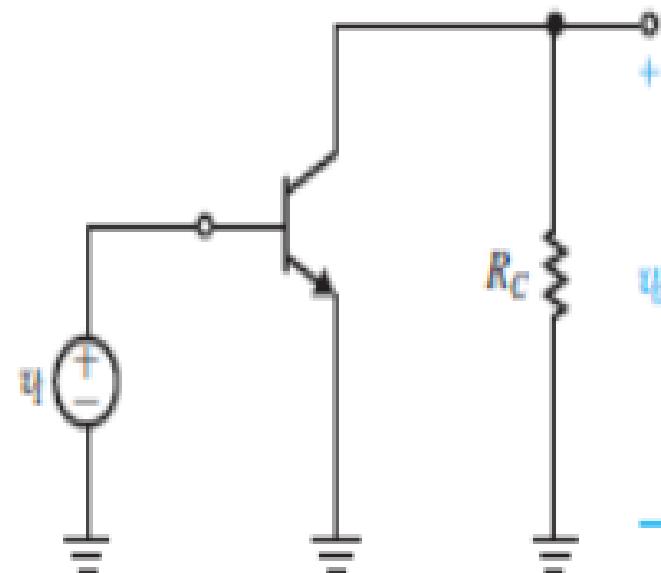

(d) Common-Emitter (CE)

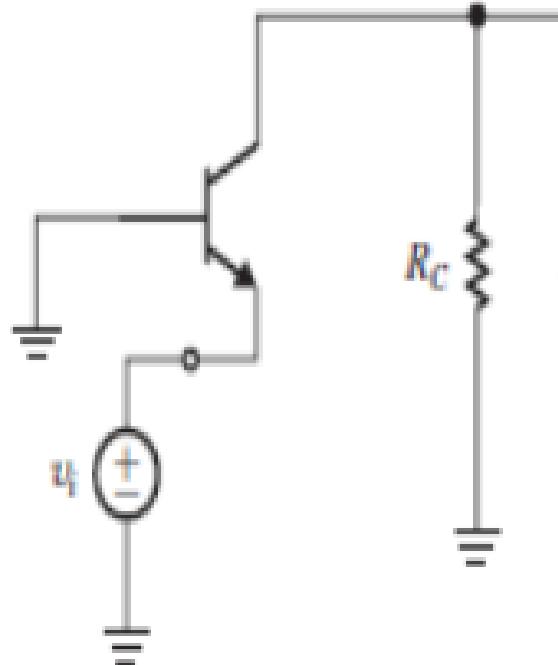

(e) Common-Base (CB)

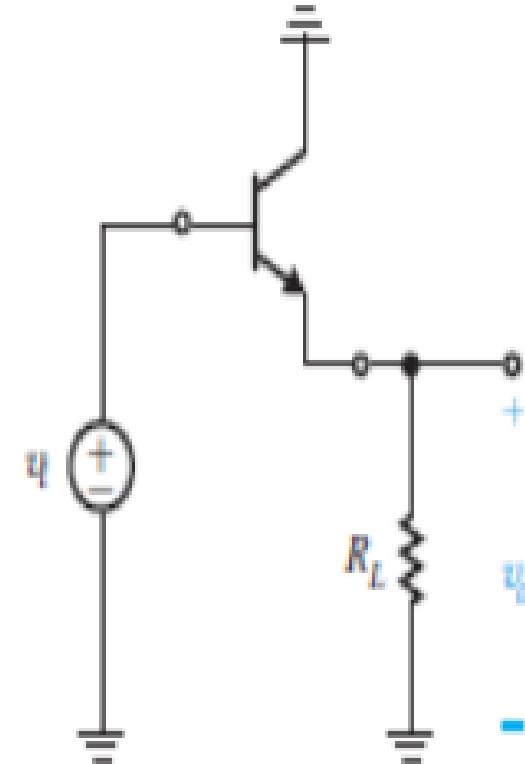

(f) Common-Collector (CC)  
or Emitter Follower

# 1- Common Emitter


Example

For the transistor amplifier shown in Figure, determine its voltage gain  $v_o/v_i$ . Assume  $\beta = 100$  and neglect the Early effect.

## Dc analysis

- All capacitors are Open circuits
- All ac voltage are short circuit
- All ac currents are open circuits

Solve as usual

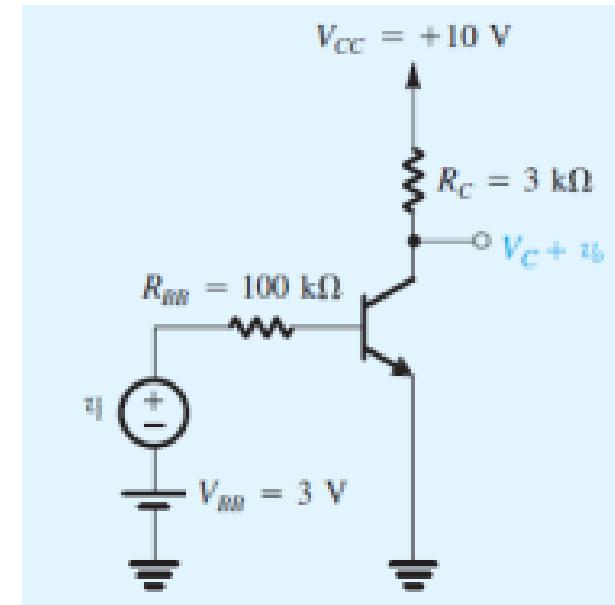

Assume transistor is in active region

Take loop shown

$$V_{BB} = I_B * R_{BB} + V_{BE}$$

$$3.0 = I_B * 100 + 0.7$$

$$I_B = 0.023mA$$

$$I_c = \beta I_B = 2.3mA$$

$$V_C = 10 - 3 * I_c = 3.1V$$

$$V_E = 0, \quad V_B = 0.7v$$

Check



$$V_E = 0v, V_B = 0.7v, V_C = 3.1v$$

Since  $V_B > V_E$  Then  $EB_J$  is Forward

Sine  $V_C > V_B$  Then  $BC_J$  is reverse

Then Transistor operates in Active as assumed
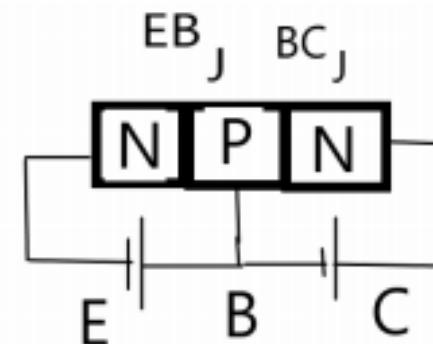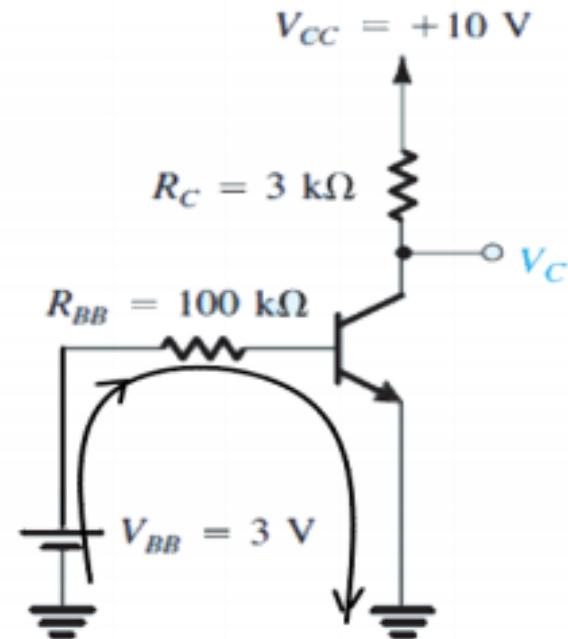
$$r_\pi = V_T / I_B = 0.025 / 0.023 = 1.0869K\Omega$$



## ac analysis

- All capacitors are short circuits
- All Dc voltage are short circuit
- All Dc currents are open circuits
- Replace transistor by equivalent model

$$v_i = i_b(R_{BB} + r_\pi) \quad (1)$$



$$v_{be} = i_b(r_\pi)$$

$$R_{in} = \frac{v_{be}}{i_b} = r_\pi = 1.087 K\Omega \quad (2)$$


$$v_o = -\beta i_b R_c \quad (3)$$

From Eqs. (1) and (3)
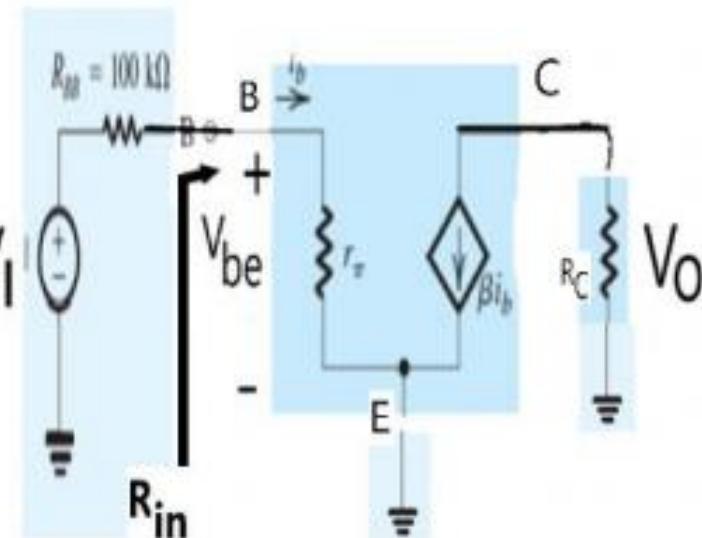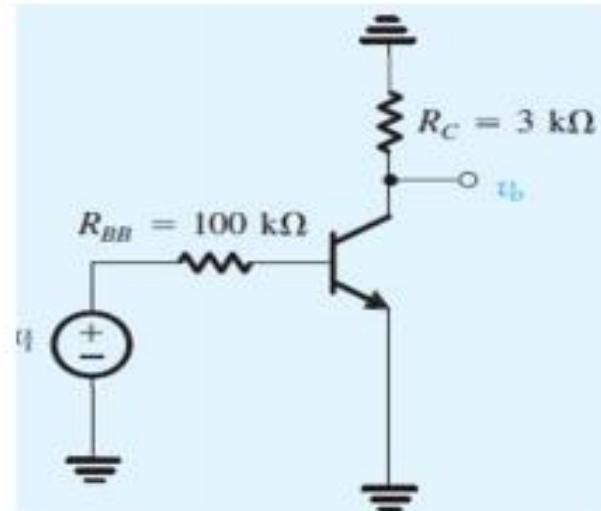
$$\frac{v_o}{v_i} = \frac{-\beta R_c}{R_{BB} + r_\pi} = -2.96 v/v \quad (4)$$


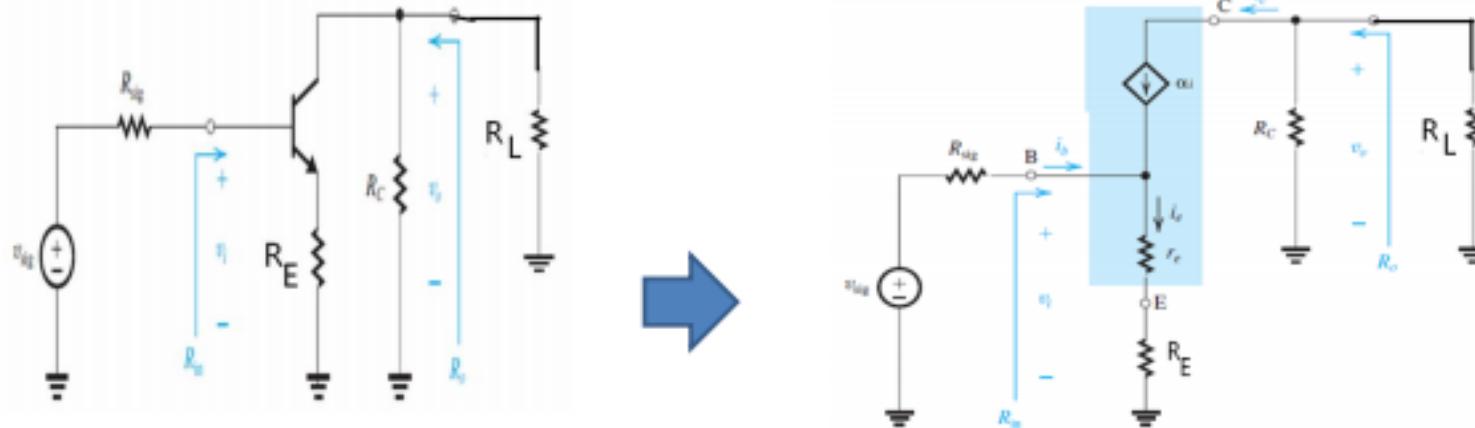
# Common-Emitter Amplifier with Emitter Resistance



$$v_i = i_e(r_e + R_E) = (1 + \beta)i_b(r_e + R_E) \quad (1) \quad \text{From Eqs (1) & (2), then}$$

$$i_i = i_b$$

$$R_{in} = v_i/i_i = (1 + \beta)(r_e + R_E)$$

$$A_{vo} = \frac{v_{oo}}{v_i} = -\alpha \frac{R_c}{r_e + R_E}$$

$$v_{oo} = -\alpha i_e R_c \quad (2)$$

$$A_{vo} = \frac{v_{oo}}{v_i} = -\alpha \frac{R_c}{r_e + R_E} = -\alpha \frac{\text{total resistance in collector}}{\text{total resistance in emitter}}$$


$$A_{vo} = \frac{v_{oo}}{v_i} = -\alpha \frac{R_c}{r_e + R_E}$$

$$v_i = i_e(r_e + R_E) \quad (1)$$

$$v_o = -\alpha i_e (R_c // R_L) \quad (3)$$

From Eqs (1) & (3), then
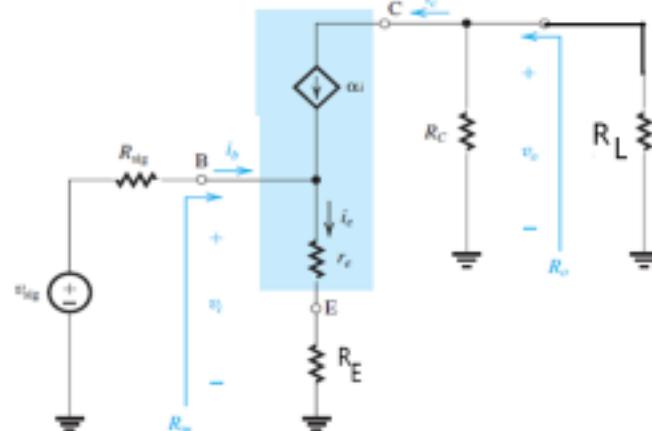
$$A_v = \frac{v_o}{v_i} = -\alpha \frac{R_c // R_L}{r_e + R_E}$$



$$G_{vo} = \frac{v_{oo}}{v_i} \frac{v_i}{v_{sig}} = -\frac{\alpha R_c}{r_e + R_E} \cdot \frac{R_{in}}{R_{in} + R_{sig}}$$

$$G_v = \frac{v_o}{v_i} \frac{v_i}{v_{sig}} = -\frac{\alpha R_c // R_L}{r_e + R_E} \cdot \frac{R_{in}}{R_{in} + R_{sig}}$$

$$G_v = -\beta \frac{R_c // R_L}{R_{sig} + (1 + \beta)(r_e + R_E)}$$

$$R_o = R_c$$

*Thank  
you*

