



**Electronic Devices and Circuits**

**EME306**

**(Summer 2021-2022)**

**Lecture 13**



## **Amplifier Circuits other modes**


**INSTRUCTOR**

**Dr / Ayman Soliman**


## ➤ Contents

- 1) The Three Basic Configurations
- 2) The Common-Base (CB) Amplifiers
- 3) The common collector ( Emitter Follower)


# The Three Basic Configurations

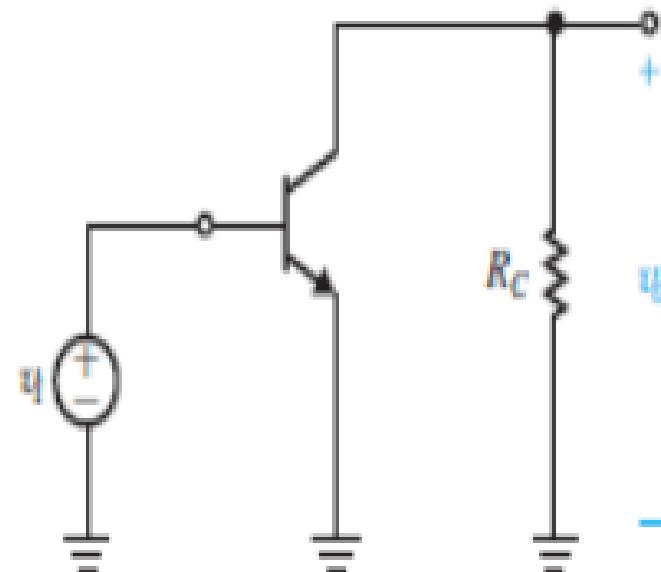

(d) Common-Emitter (CE)

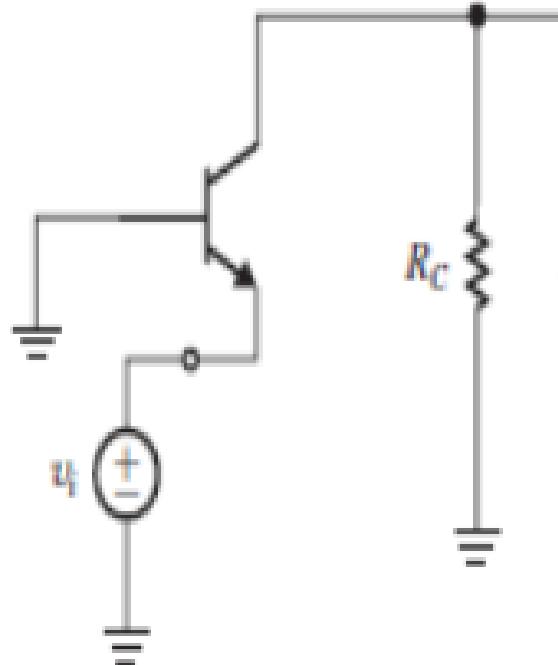


(e) Common-Base (CB)

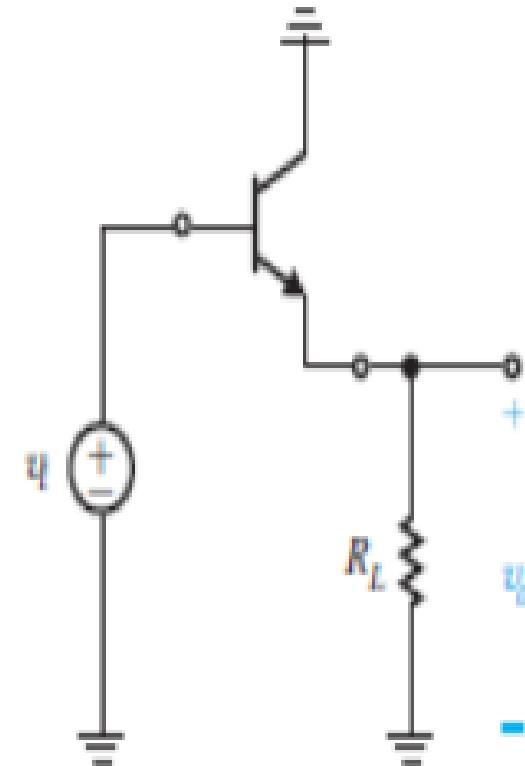

(f) Common-Collector (CC)  
or Emitter Follower


# 1-The Common-Base (CB) Amplifiers

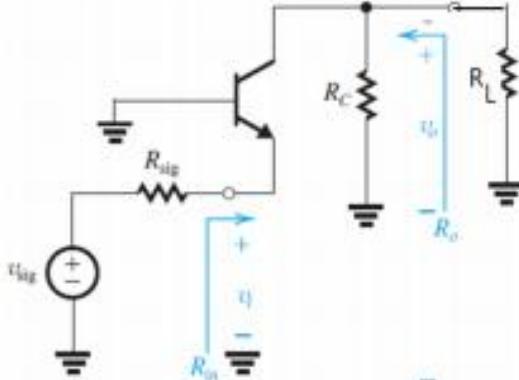

$$v_i = - i_e r_e$$

$$i_i = - i_e$$
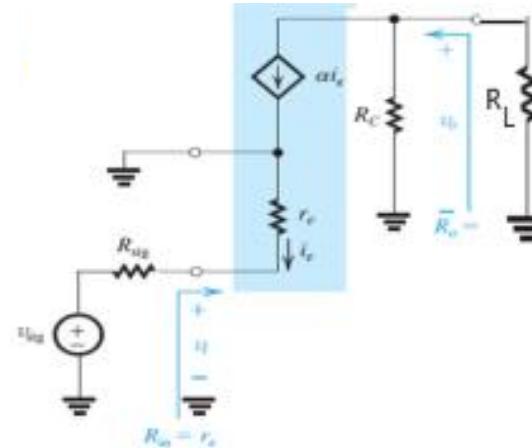
$$R_{in} = \frac{v_i}{i_i} = r_e = \frac{\alpha}{g_m}$$



$$v_o = -\alpha i_e (R_c // R_L)$$

$$v_{oo} = -\alpha i_e (R_c)$$

$$A_{vo} = \frac{v_{oo}}{v_i} = -\alpha \frac{R_c}{r_e} = -g_m R_c$$

$$A_v = \frac{v_o}{v_i} = -\alpha \frac{R_c // R_L}{r_e} = -g_m (R_c // R_L)$$

$$R_{in} = \frac{v_i}{i_i} = r_e = \frac{\alpha}{g_m}$$

$$A_{vo} = \frac{v_{oo}}{v_i} = -\alpha \frac{R_c}{r_e} = -g_m R_c$$


$$A_v = \frac{v_o}{v_i} = -\alpha \frac{R_c // R_L}{r_e} = -g_m (R_c // R_L)$$

$$v_i = \frac{v_{sig} R_{in}}{R_{sig} + R_{in}} \rightarrow \frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}}$$

$$G_v = \frac{v_o}{v_i} \frac{v_i}{v_{sig}} = -g_m (R_c // R_L) \cdot \frac{R_{in}}{R_{sig} + R_{in}} = -g_m (R_c // R_L) \frac{r_e}{R_{sig} + r_e} = -\frac{\alpha (R_c // R_L)}{R_{sig} + r_e}$$

$$G_{vo} = \frac{v_{oo}}{v_i} \frac{v_i}{v_{sig}} = -g_m R_c \cdot \frac{R_{in}}{R_{sig} + R_{in}} = -g_m R_c \frac{r_e}{R_{sig} + r_e} = -\frac{\alpha R_c}{R_{sig} + r_e}$$

$$R_o = R_c$$

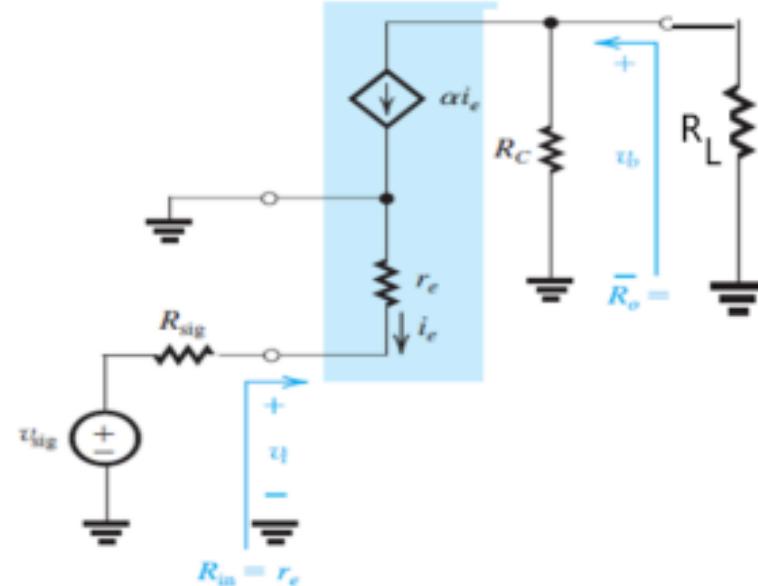

### Example

For the circuit shown, determine the voltage gain and the signal waveforms at various points. Given  $\beta=100$ .

Sketch the o/p when  $v_i=10\text{mV}$  sinusoidal

### Dc analysis

- All capacitors are Open circuits
- All ac voltage are short circuit
- All ac currents are open circuits

### Assume Active



$$V_B = 0, \quad V_E = 0.7$$

$$I_E = \frac{10 - 0.7}{10} = 0.93\text{mA}$$

$$I_c = \alpha I_E = (100/101) * 0.93 = 0.9208\text{mA}$$

$$V_c = -10 + 5 * I_c = -5.396\text{v}$$

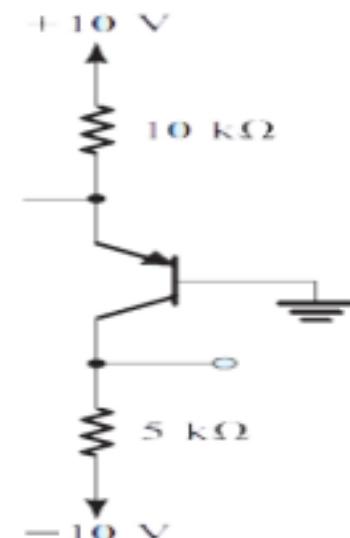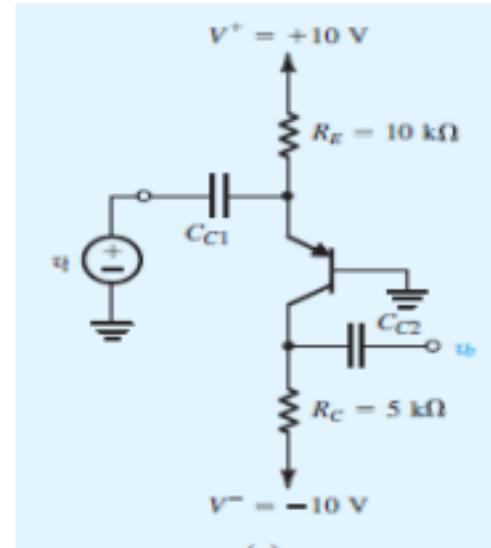
$$r_e = \frac{V_t}{I_E} = \frac{0.025}{0.93} = 0.0269\text{K}\Omega$$



Check



$$V_E = 0.7\text{v}, V_B = 0\text{v}, V_C = -5.396\text{v}$$

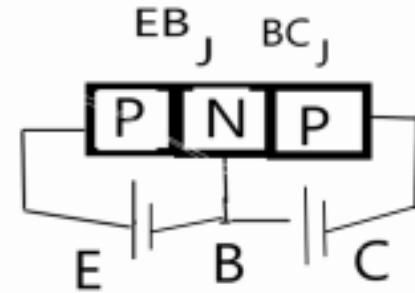Since  $V_E > V_B$ , Then  $EB_J$  is Forward  
Since  $V_B > V_C$ , Then  $BC_J$  is reverse  
Then Transistor operates in Active


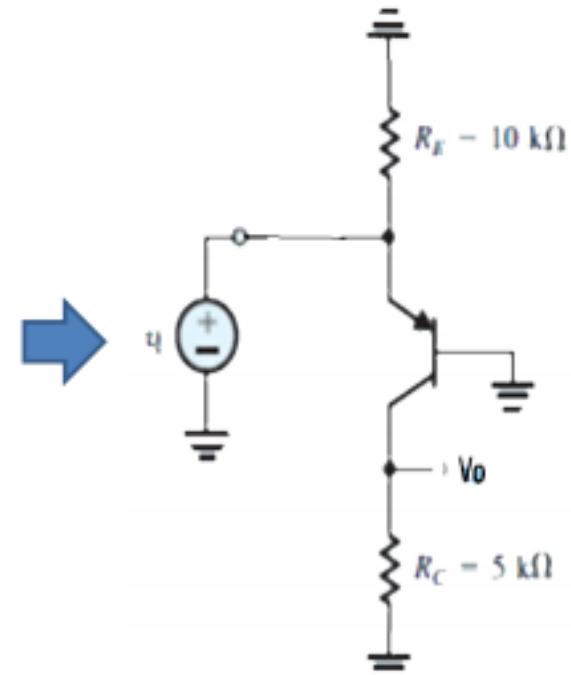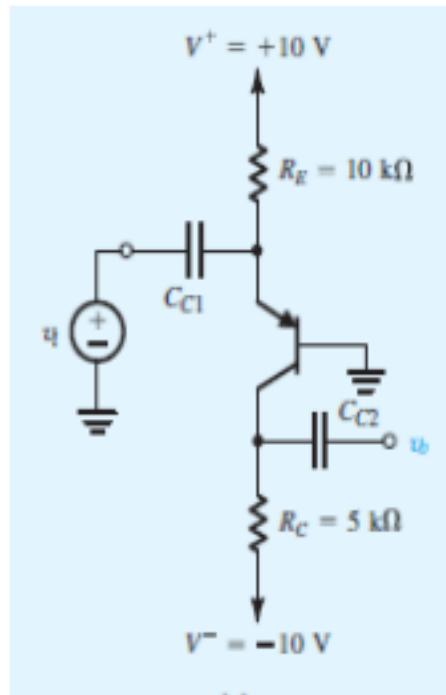
### ac analysis

- All capacitors are short circuits
- All Dc voltage are short circuit (grounded)
- All Dc currents are open circuits
- Replace transistor by equivalent model



$$v_o = -\alpha i_e * R_c$$



$$v_i = -i_e * r_e$$

$$\frac{v_o}{v_i} = \frac{\alpha R_c}{r_e} = \frac{(100/101)*5}{0.0269} = 184.03 \text{ v/v}$$


When  $v_i=10 \text{ mV}$ , then

$$v_o = 10 \text{ mV} * 184.03 = 1.8403 \text{ V}$$
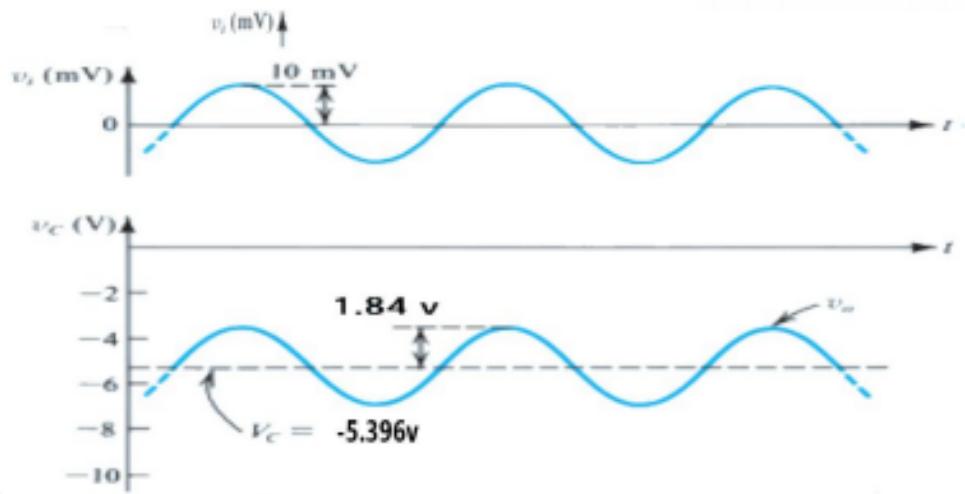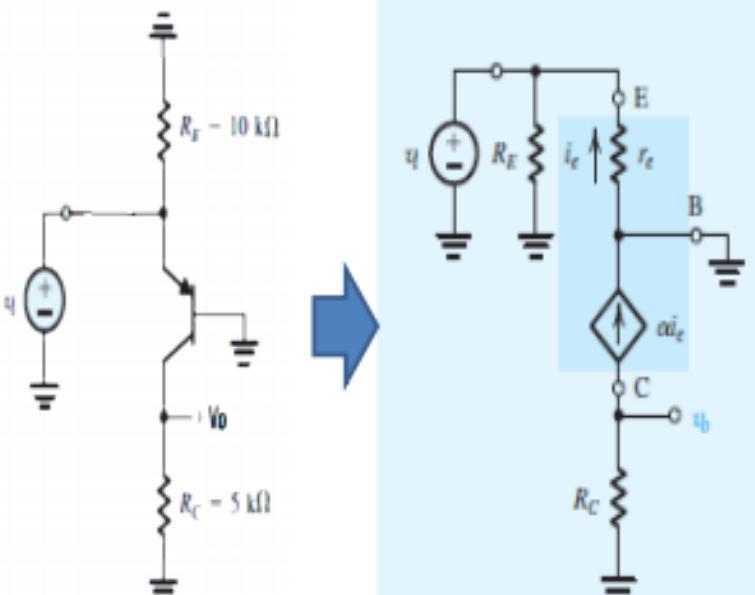
$$V_C = -5.396 \text{ V} \quad v_o = 1.84 \text{ V}$$


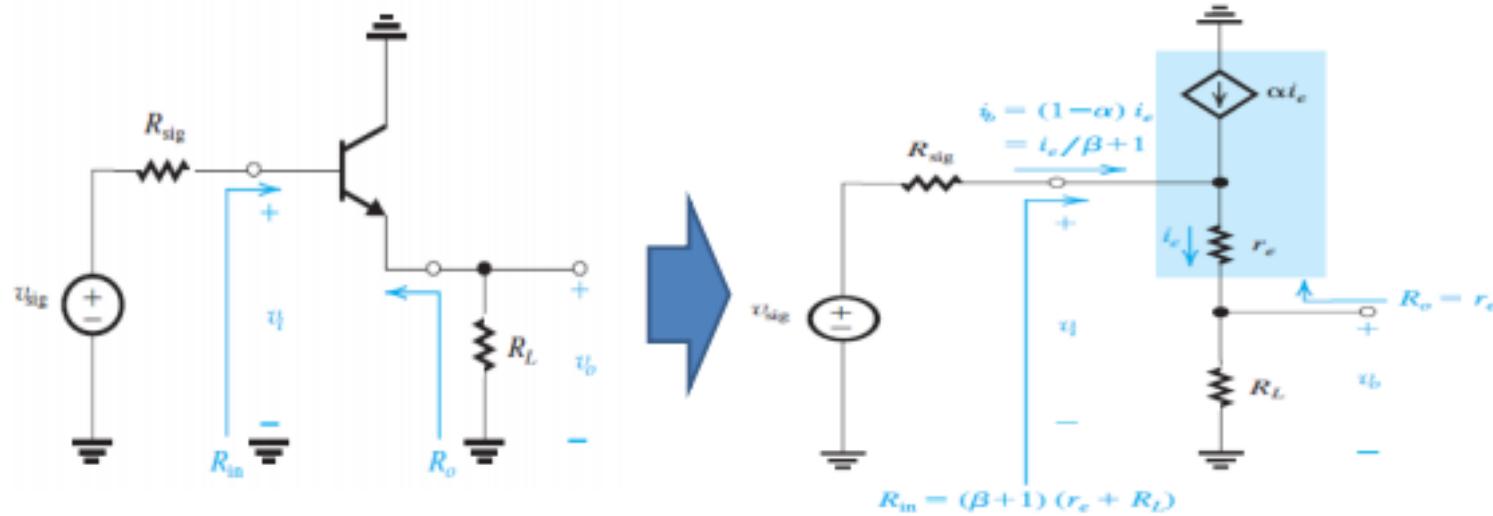
## 2-The common collector ( Emitter Follower)



$$v_i = i_e (r_e + R_L) = (1 + \beta) i_b (r_e + R_L)$$

$$i_i = i_b$$

$$R_{in} = \frac{v_i}{i_i} = (1 + \beta) (r_e + R_L)$$

$$v_o = i_e R_L$$

$$A_v = \frac{v_o}{v_i} = \frac{R_L}{(r_e + R_L)} \cong 1$$


$$A_v = \frac{v_o}{v_i} = \frac{R_L}{(r_e + R_L)} \cong 1$$

$$R_{in} = (1 + \beta)(r_e + R_L)$$

$$v_i = \frac{v_{sig} \cdot R_{in}}{(R_{sig} + R_{in})}$$

$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{(R_{sig} + R_{in})}$$
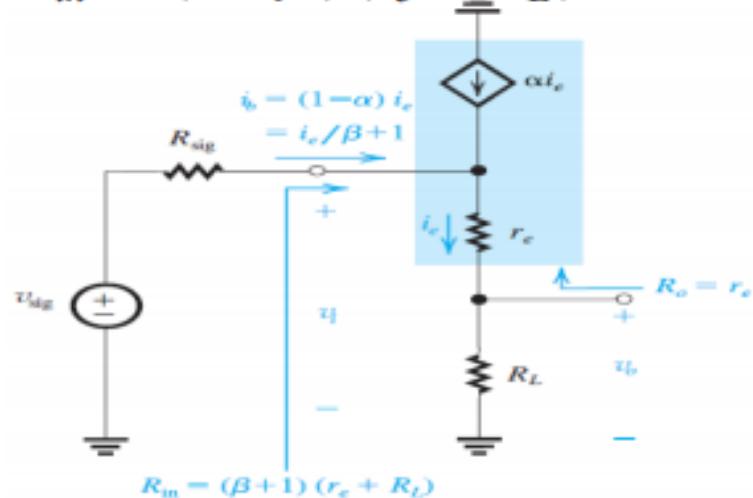
$$G_v = \frac{v_o}{v_i} \frac{v_i}{v_{sig}} = \frac{R_L}{r_e + R_L} \cdot \frac{R_{in}}{R_{sig} + R_{in}} = \frac{(1 + \beta)R_L}{R_{sig} + (1 + \beta)(r_e + R_L)}$$



Because the gain is nearly =1 , so any change in input will be followed by a change in output, so it is **called emitter follower**

## Calculation of $R_o$ $C$

When make S.C on  $V_i$ , then  $\rightarrow R_o = r_e$


When make S.C on  $V_{sig}$  then

- 1- Make short circuit on supply  $v_{sig}$
- 2- Apply source  $V_x$  pass current  $i_x$

$$V_x = -i_e r_e + -\frac{i_e}{1+\beta} R_{sig}$$

$$i_x = -i_e$$
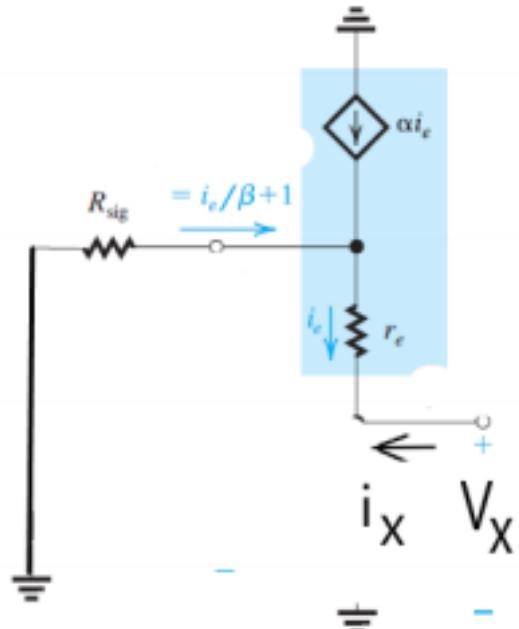
$$R_o = \frac{V_x}{i_x} = r_e + \frac{R_{sig}}{1+\beta}$$



*Thank  
you*

