



Electronic Devices and Circuits

EME306

(Summer 2021-2022)

Lecture 3

DIODE MODELS

INSTRUCTOR

Dr / Ayman Soliman



➤ Contents

- 1) DIODE MODELS
- 2) The Ideal Diode Model
- 3) The Practical Diode Model
- 4) The Complete Diode Model
- 5) The Actual Diode Model
- 6) Diodes circuits
- 7) examples

DIODE MODELS

```
graph LR; A[DIODE MODELS] --- B[Ideal Diode Model]; A --- C[Practical Diode Model]; A --- D[Complete Diode Model]; A --- E[Actual Diode Model];
```


Ideal Diode Model

Practical Diode Model


Complete Diode Model

Actual Diode Model


The Ideal Diode Model

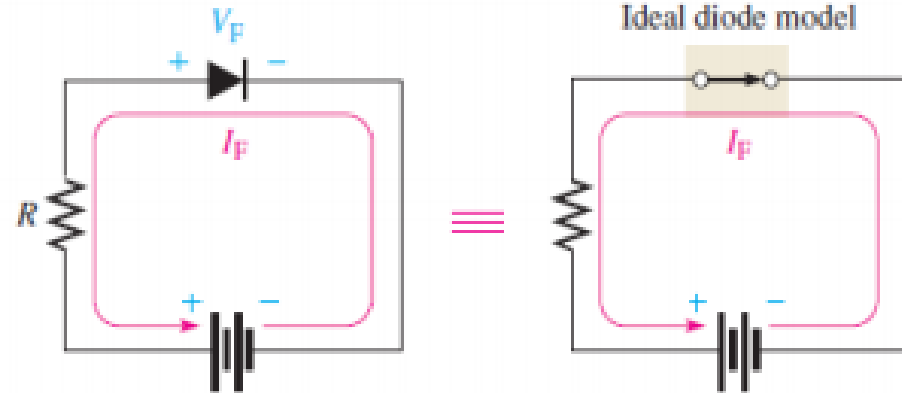

(a) Forward bias

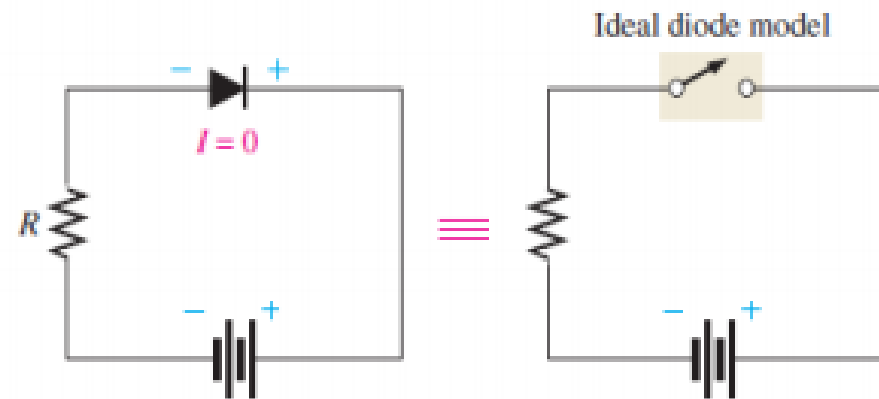


(b) Reverse bias

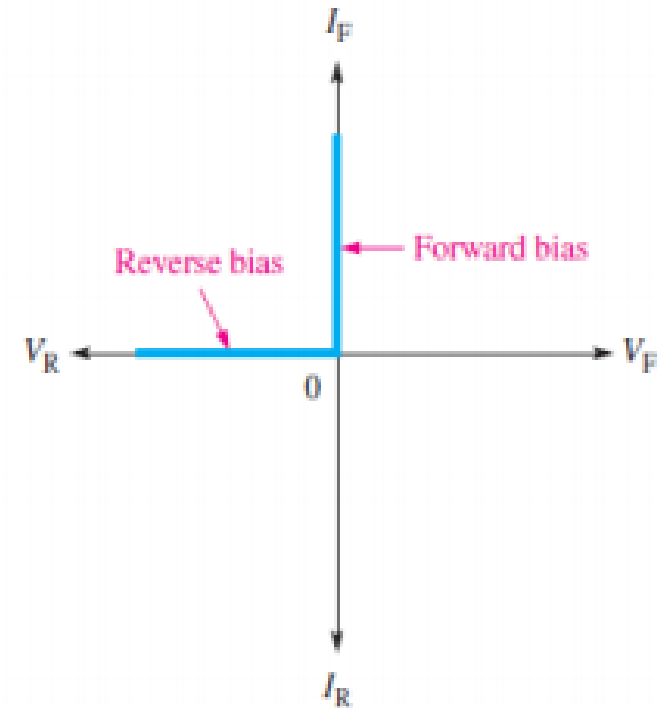


(c) Ideal V-I characteristic curve (blue)


The Practical Diode Model

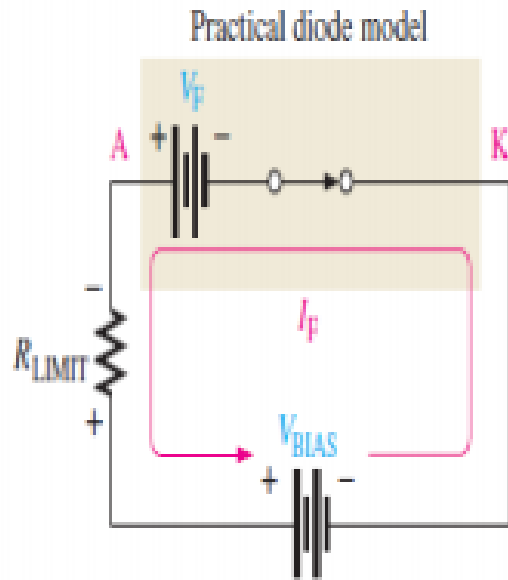

(a) Forward bias



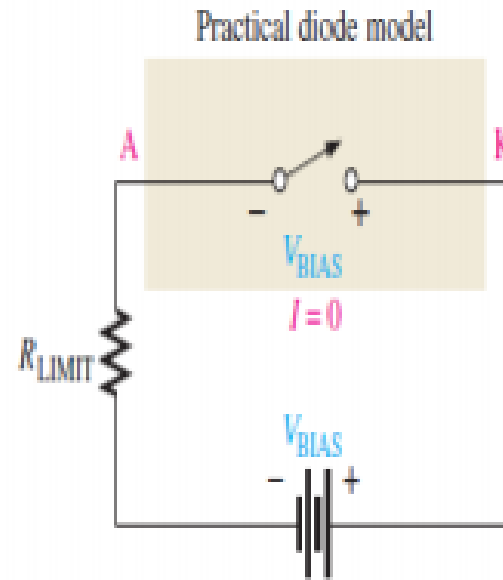


(b) Reverse bias

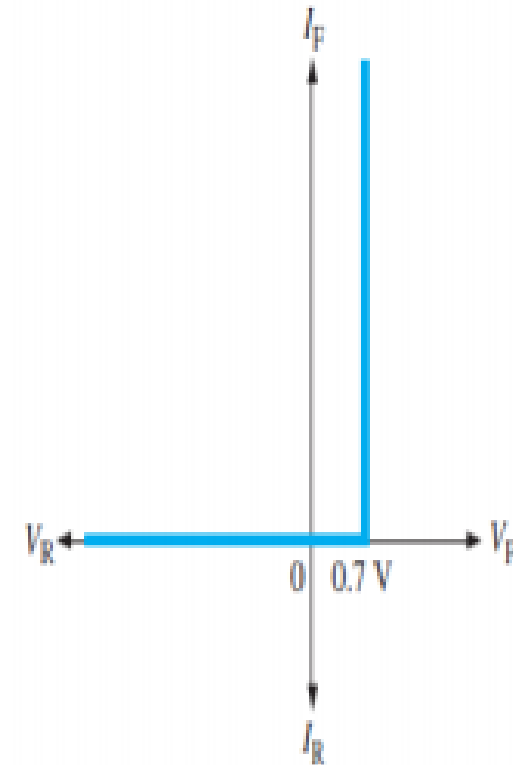

(c) Characteristic curve (silicon)

The Complete Diode Model

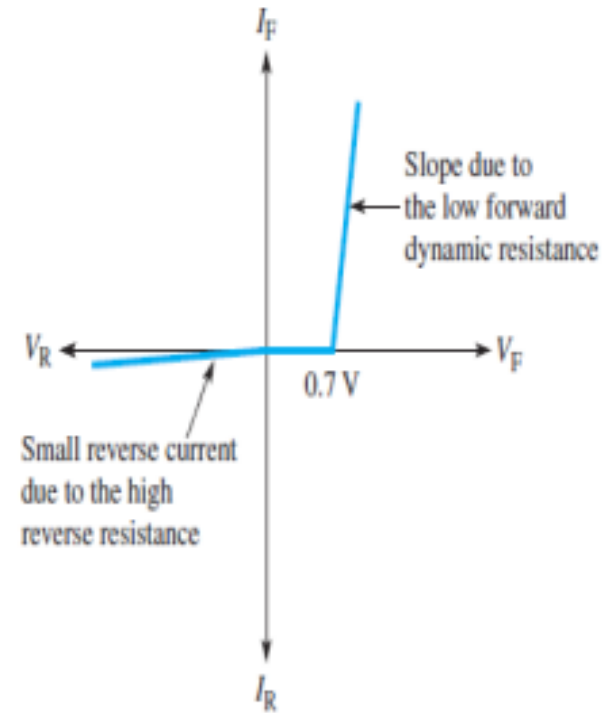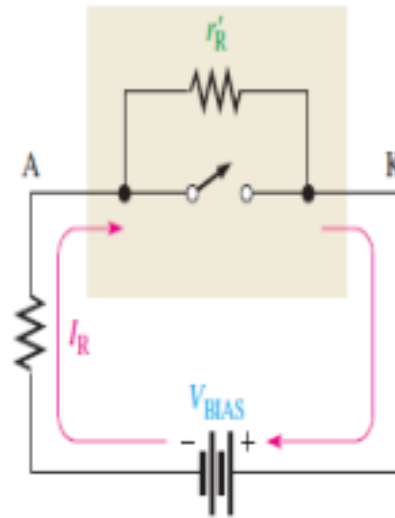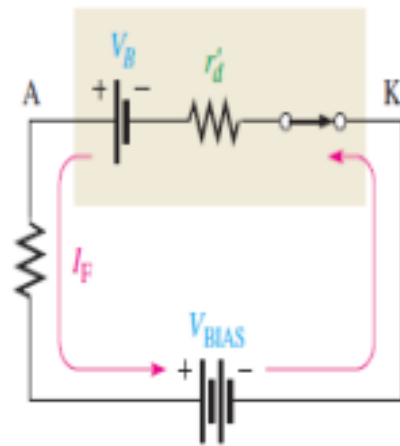


The Actual Diode Model

$$I_D = I_S \left(e^{\frac{V_D}{nV_t}} - 1 \right)$$

I_S scale current

n constant



V_t thermal voltage = 25mv

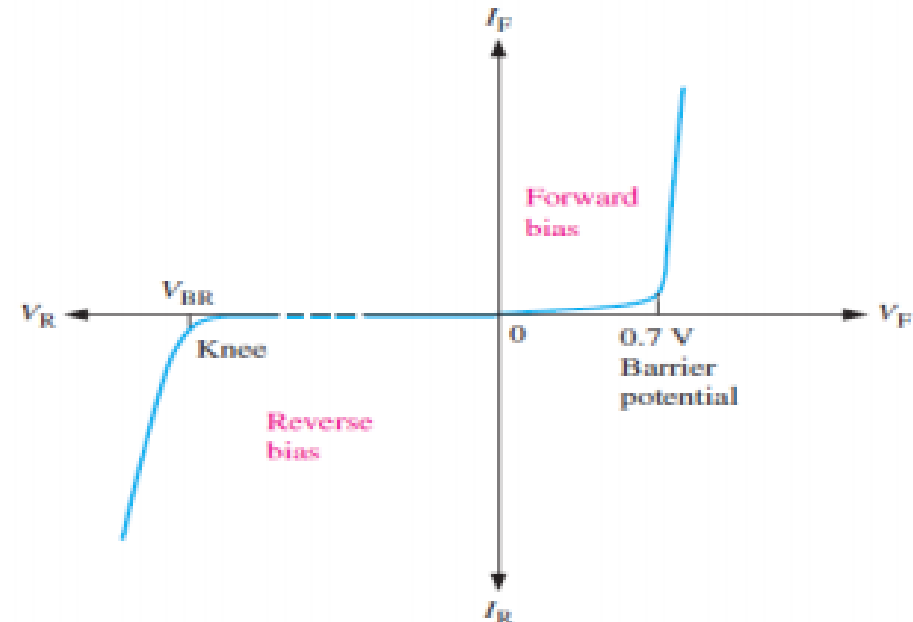


The complete V-I characteristic curve for a diode.

Diodes circuits

➤ Ideal diode model

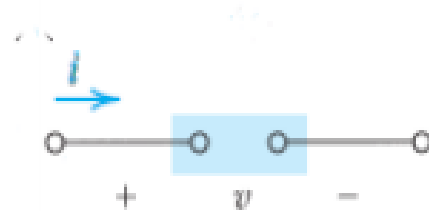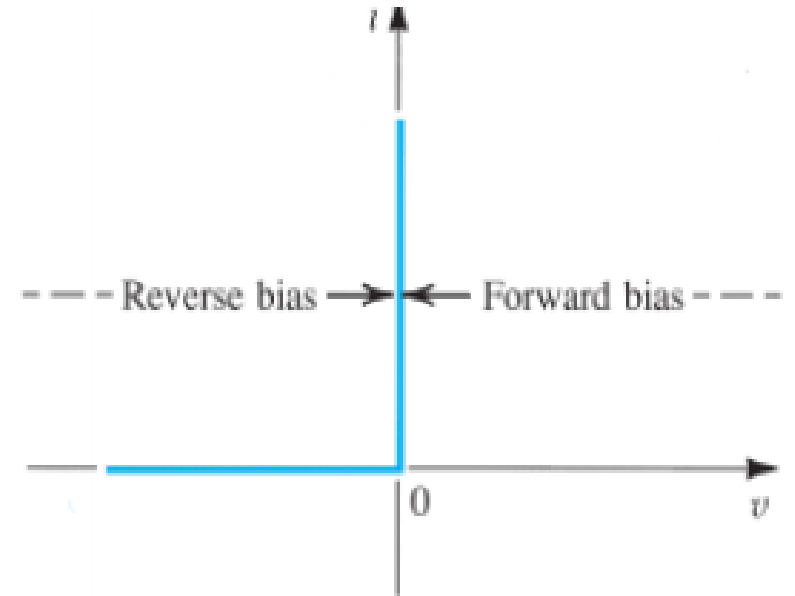

$$v < 0 \Rightarrow i = 0$$

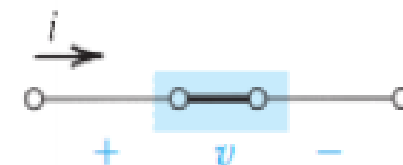

$$i > 0 \Rightarrow v = 0$$

Example

- For the circuit shown, assume ideal diode; find the current in the circuit shown?

For diode in circuit (a)

Diode is on,

Because diode is ideal diode

$$V_D = 0 \text{ v}$$


$$I_D = (10 - 0) / 1 \text{ k}\Omega = 10 \text{ mA}$$

For diode in circuit (b)

Diode is off, so it is open circuit,

$$\text{and } V_D = 10 \text{ v}$$

$$I_D = 0 \text{ mA}$$

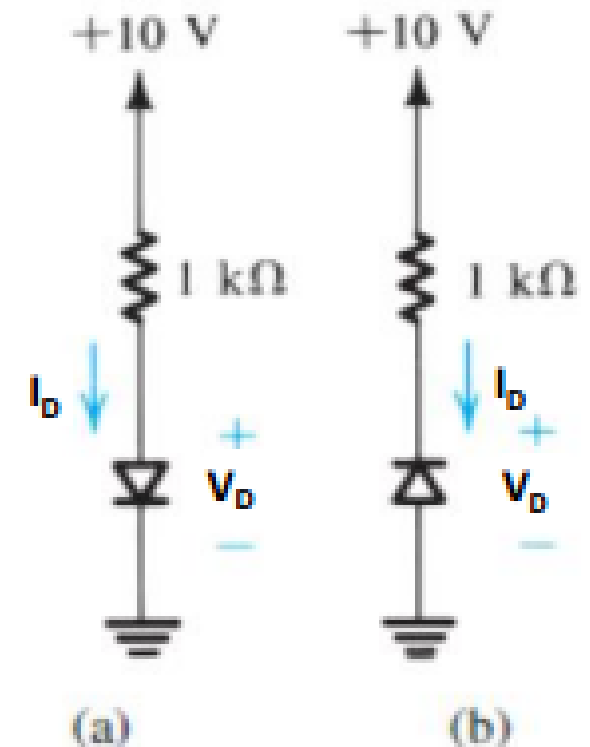

Example

- Assuming the diodes to be ideal, find the values of I and V in the circuits shown?

For circuit shown in Fig (a)

Assume diode D_1 is on, so $V_B = 0V$

Then diode D_2 will be on

$$I_{D2} = (10 - 0) / 10 = 1mA$$


At node B

$$I + I_{D2} = I_{5k\Omega}$$

$$I + 1mA = (0 - (-10)) / 5$$

Then $I = 1 mA$

$$V = V_B = 0V$$

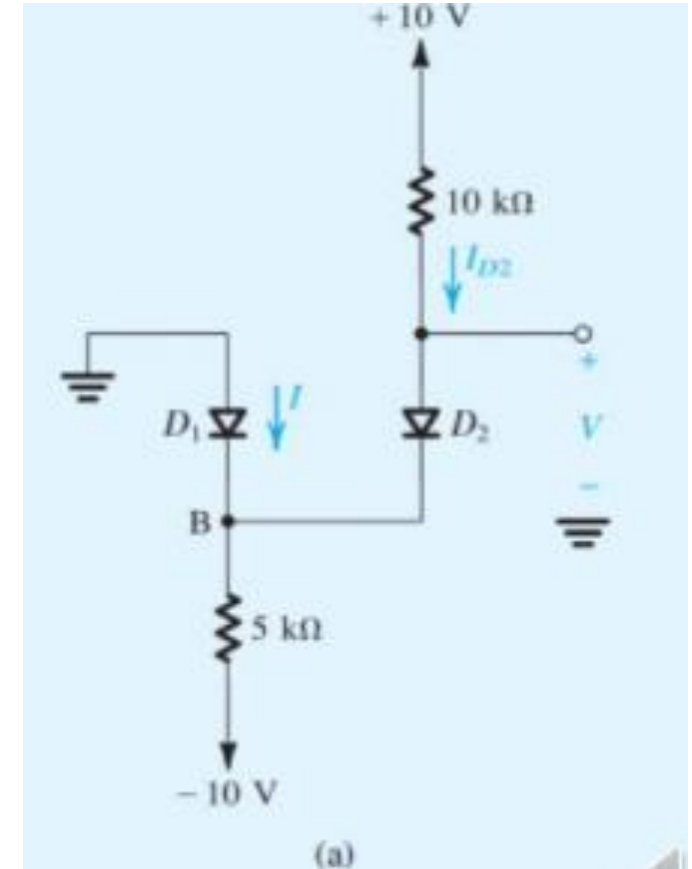

Example

For circuit shown in Fig (b)

Assume diode D_1 is on, so $V_B=0\text{v}$

Then diode D_2 will be on

$$I_{D2} = (10-0)/5 = 2\text{mA}$$

At node B

$$I + I_{D2} = I_{10\text{k}\Omega}$$

$$I + 2\text{mA} = (V_B - (-10))/10 = (0-10)/10 = 1\text{mA}$$

Then $I = -1\text{ mA}$,

so diode D_1 will be off (open circuit) and


$$I = 0\text{ mA}$$

While diode D_2 will be on, so

$$I_{D2} = I_{5\text{k}\Omega} = I_{10\text{k}\Omega} = (10 - (-10))/(5+10) = 20/15 = 1.333\text{mA}$$

$$V = 10 - 1.333 \cdot 5 = 3.3333\text{V}, \quad \text{or}$$
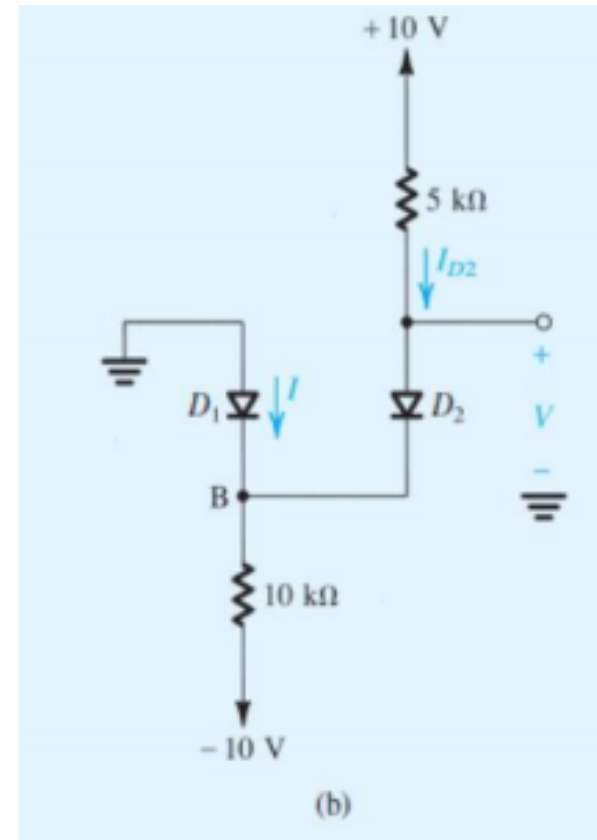
$$V = -10 + 1.333 \cdot 10 = 3.3333\text{V}$$



Thank
you

