



Electronic Devices and Circuits

EME306

(Summer 2021-2022)

Lecture 4

Diode Applications

INSTRUCTOR

Dr / Ayman Soliman



➤ Contents


- 1) The Half-Wave Rectifier
- 2) Average value
- 3) FULL-WAVE RECTIFIERS
- 4) Effect of the Turns Ratio on the Output Voltage

The Half-Wave Rectifier

- A half-wave rectifier allows current through the load only during one-half of the cycle.


During +ve half cycle (t_0-t_1)

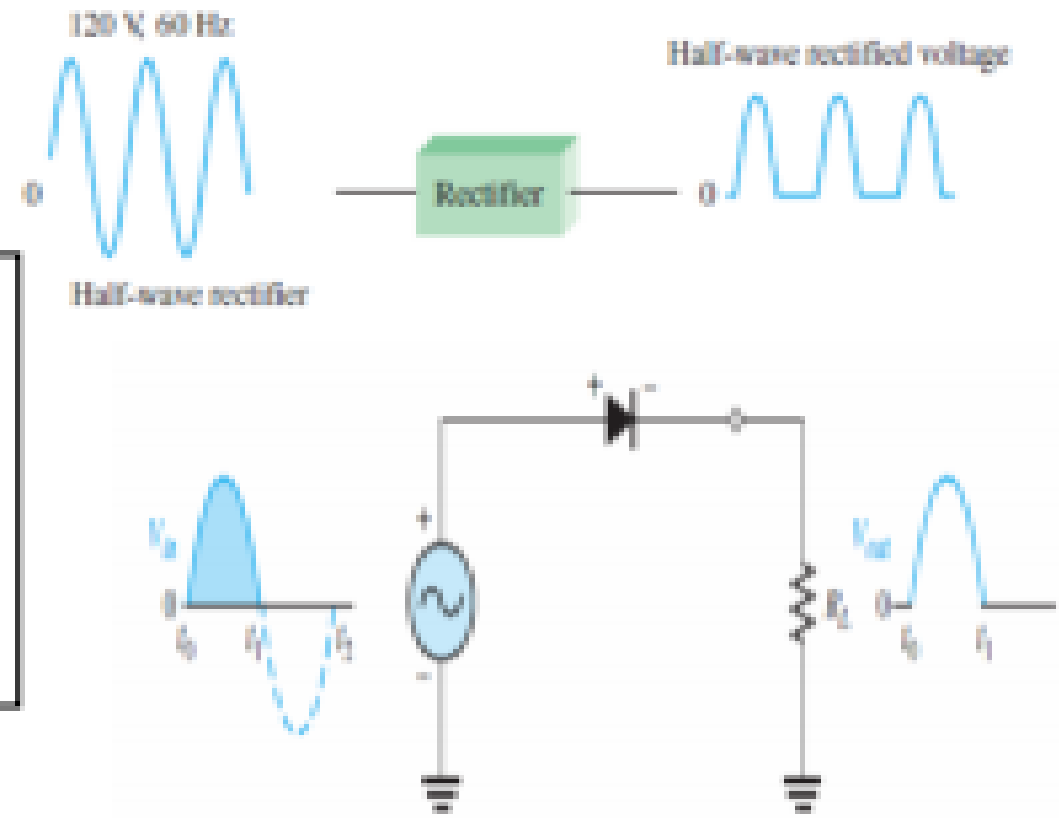- For diode is ideal, so it is on, and be like short circuit
Then $V_o = V_i$



During -ve half cycle (t_1-t_2)

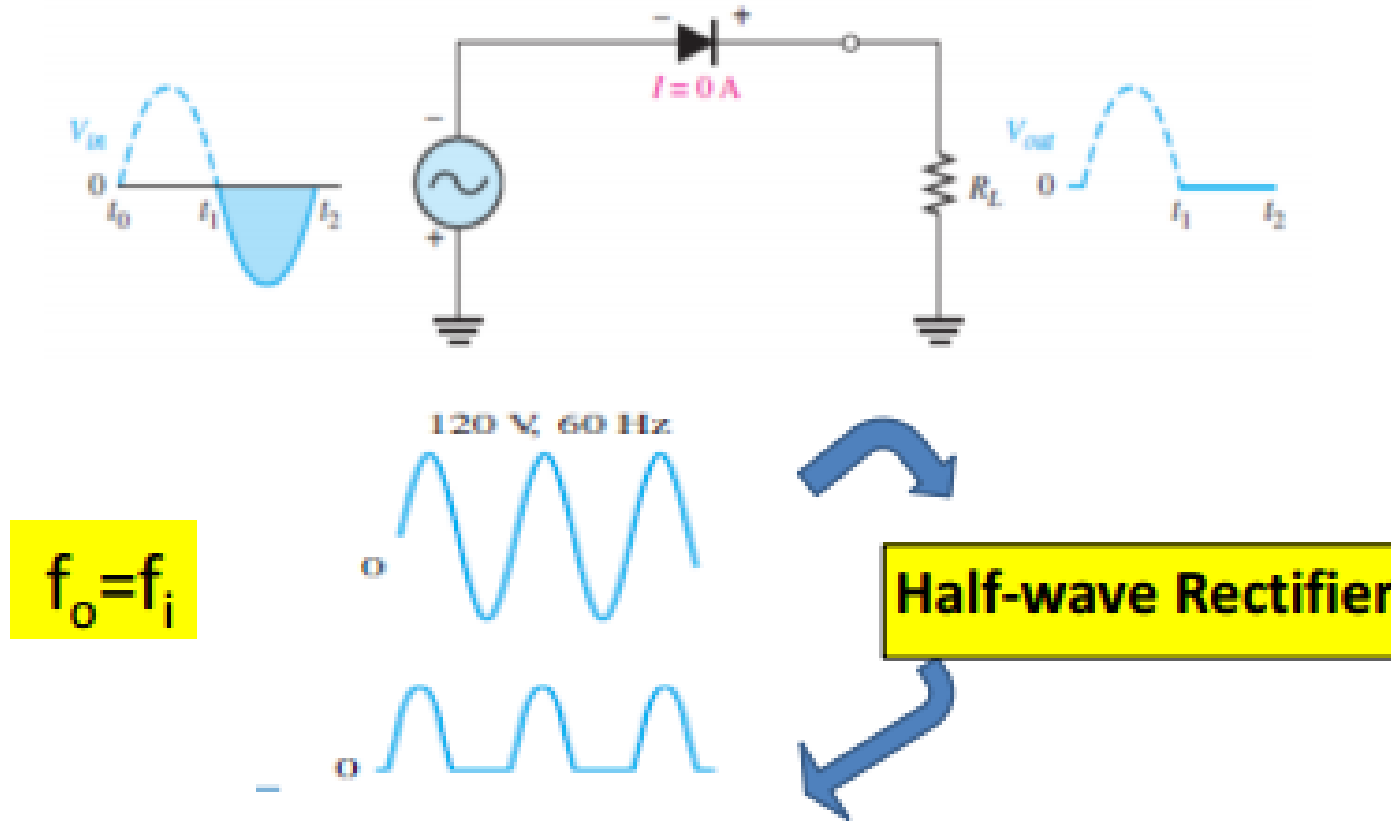- Diode is off, so no current pass and voltage drop on resistor is zero Then $V_o=0$ V



Average value

- Corresponding to how much the Dc value obtained from an alternating signal

For half-wave rectifier



$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

$$V_{avg} = \frac{V_P}{\pi} = 0.318V_P$$

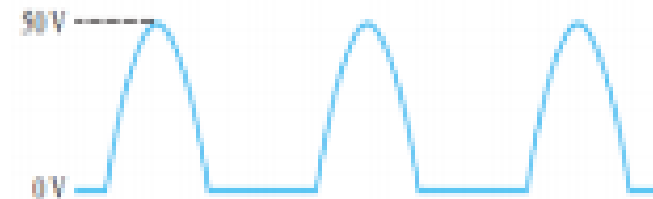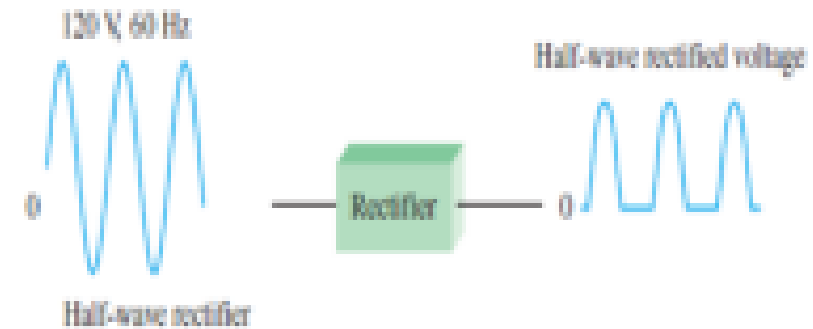Example

What is the average value of the half-wave rectified voltage shown?

$$V_{avg} = \frac{V_P}{\pi} = \frac{50}{\pi} = 15.9V$$




Effect of the Barrier Potential ($V_D=0.7\text{v}$) on the Half Wave Rectifier output

During +ve half cycle

For $V_D=0.7\text{ v}$,

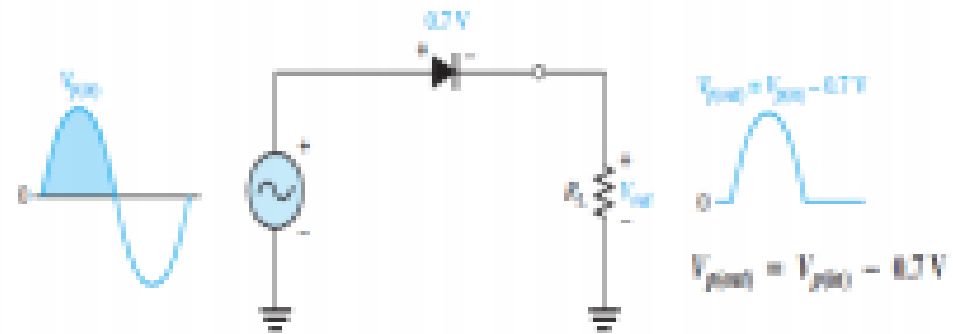- When $V_i < 0.7\text{ v}$, then diode off and $V_o=0$
- When $V_i \geq 0.7\text{ v}$, then diode on and $V_o=V_i-0.7$



During -ve half cycle

diode is off, so no current pass and voltage drop on resistor is zero , Then $V_o=0\text{ V}$

Example

Draw the output voltages of each rectifier for the indicated input voltages, as shown in Figure, where 1N4001 and 1N4003 are specific rectifier diodes with $V_D=0.7$ when be on


For circuit in Fig (a)

$$\begin{aligned} V_{p(out)} &= V_{p(in)} - 0.7 \text{ V} \\ &= 5 \text{ V} - 0.7 \text{ V} = 4.30 \text{ V} \end{aligned}$$

For circuit in Fig (b)


$$\begin{aligned} V_{p(out)} &= V_{p(in)} - 0.7 \text{ V} \\ &= 100 \text{ V} - 0.7 \text{ V} = 99.3 \text{ V} \end{aligned}$$

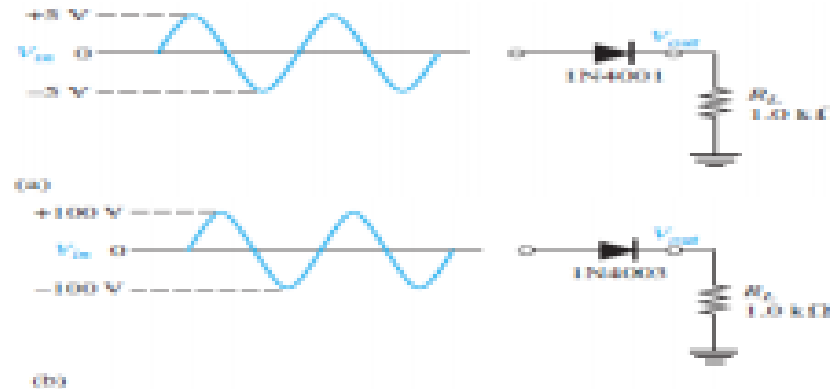For -ve half cycle, both circuits are off



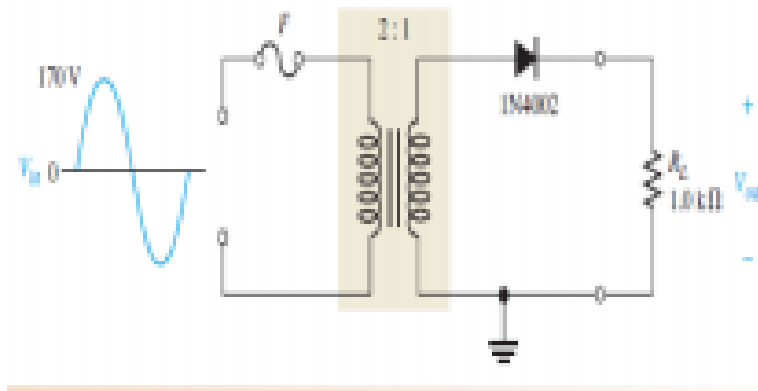Example


Determine the peak value of the output voltage.



The peak secondary voltage is

$$V_{p(sec)} = 0.5(170 \text{ V}) = 85 \text{ V}$$
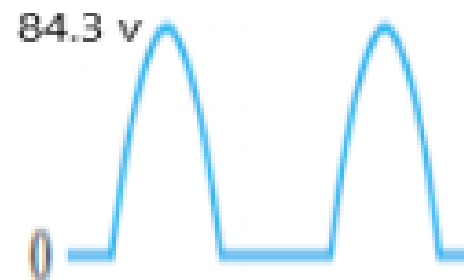
$$\begin{aligned} V_{p(out)} &= V_{p(sec)} - 0.7 \text{ V} \\ &= 85 \text{ V} - 0.7 \text{ V} = 84.3 \text{ V} \end{aligned}$$



Thank
you

