



Electronic Devices and Circuits

EME306

(Summer 2021-2022)

Lecture 5

Full-Wave Rectifiers

INSTRUCTOR

Dr / Ayman Soliman




➤ Contents

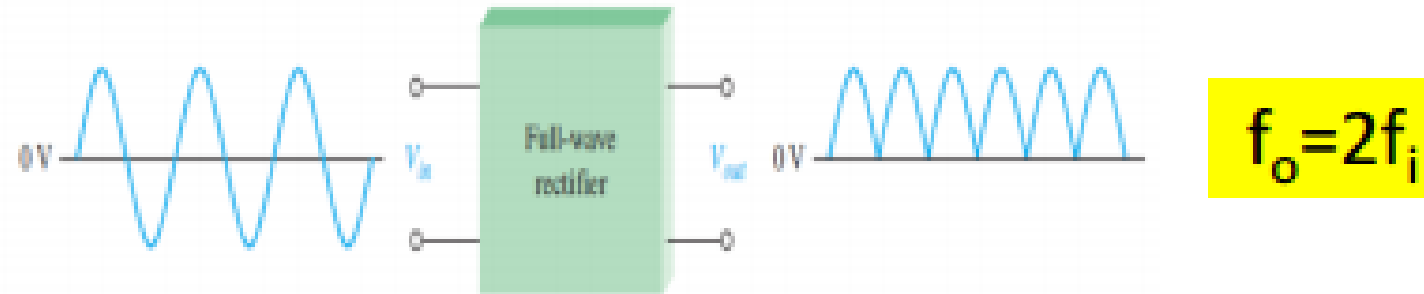- 1) FULL-WAVE RECTIFIERS
- 2) Types of full wave rectifiers
- 3) Effect of the Turns Ratio on the Output Voltage

FULL-WAVE RECTIFIERS

- A full-wave rectifier allows unidirectional (one-way) current through the load during the entire of the input cycle.
- The output voltage of full-wave rectification have a frequency twice the input frequency
- $f_o=2f_i$




Full-wave rectifier average value

$$V_{avg} = \frac{2v_p}{\pi} = 2 * .318v_p = .636v_p$$


Types of full wave rectifiers

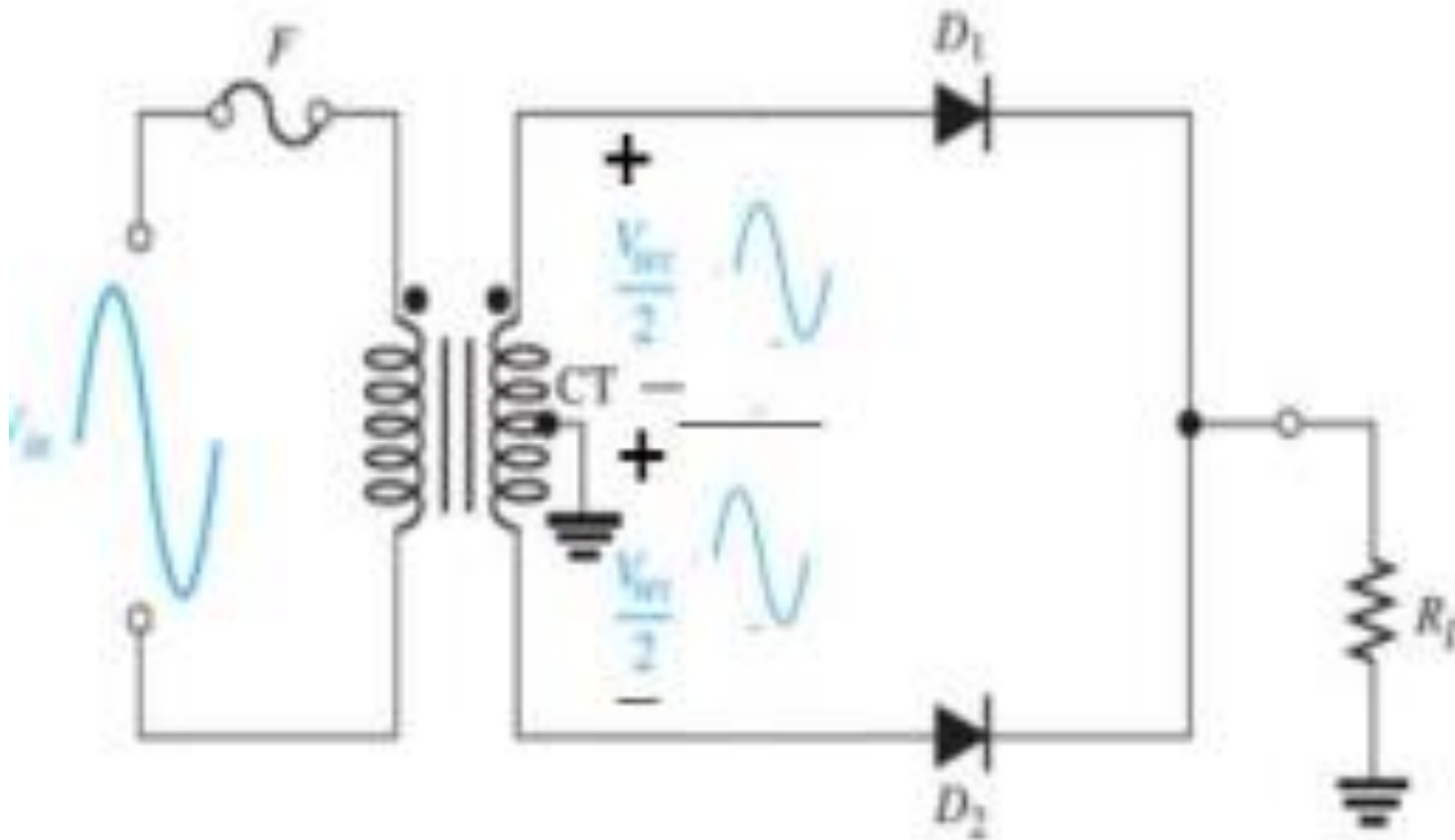- 1- Center-Tapped Full-Wave Rectifier Operation




For +ve half cycle

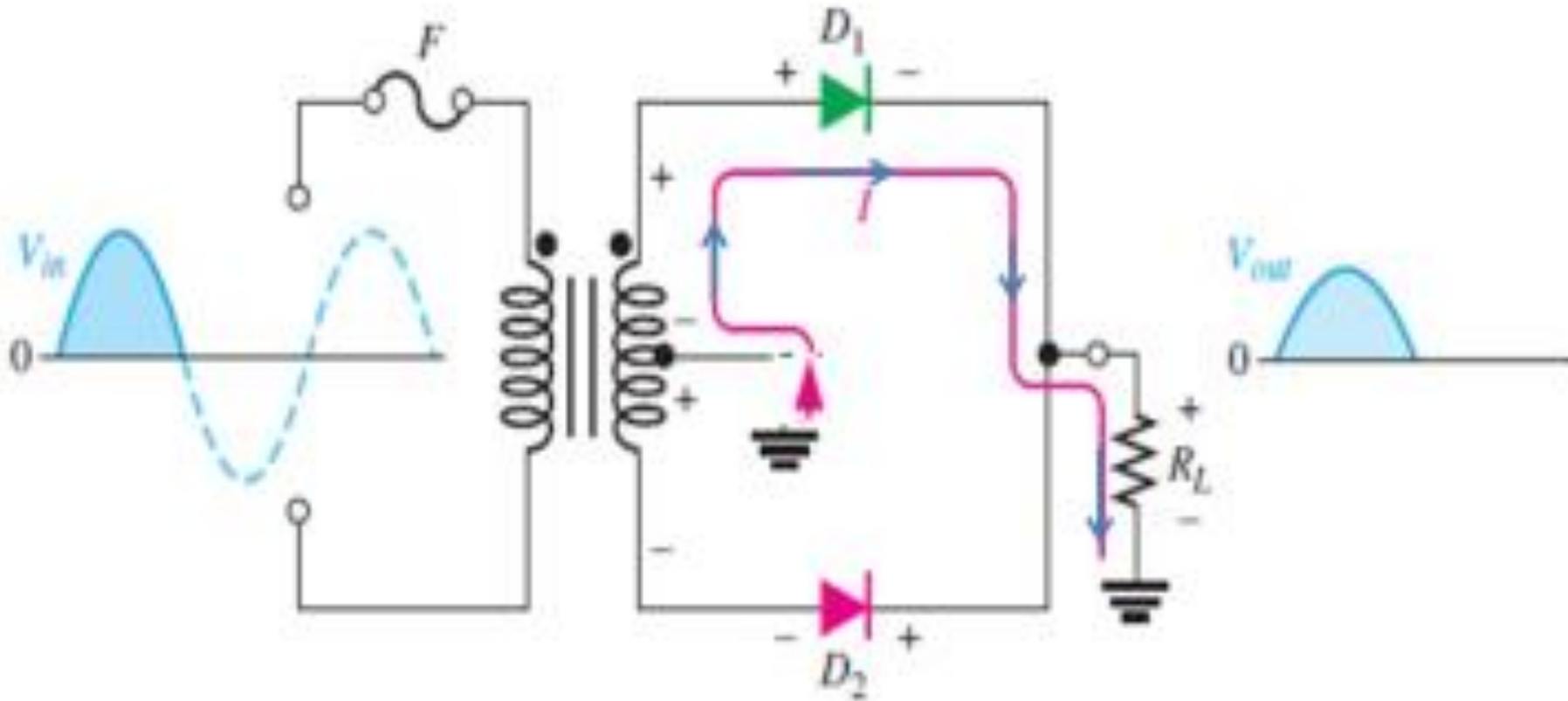- This condition will forward-biases diode D_1 and reverse biases diode D_2 .
- The current path is through D_1 and the load resistor R_L , as indicated




For -ve half cycle

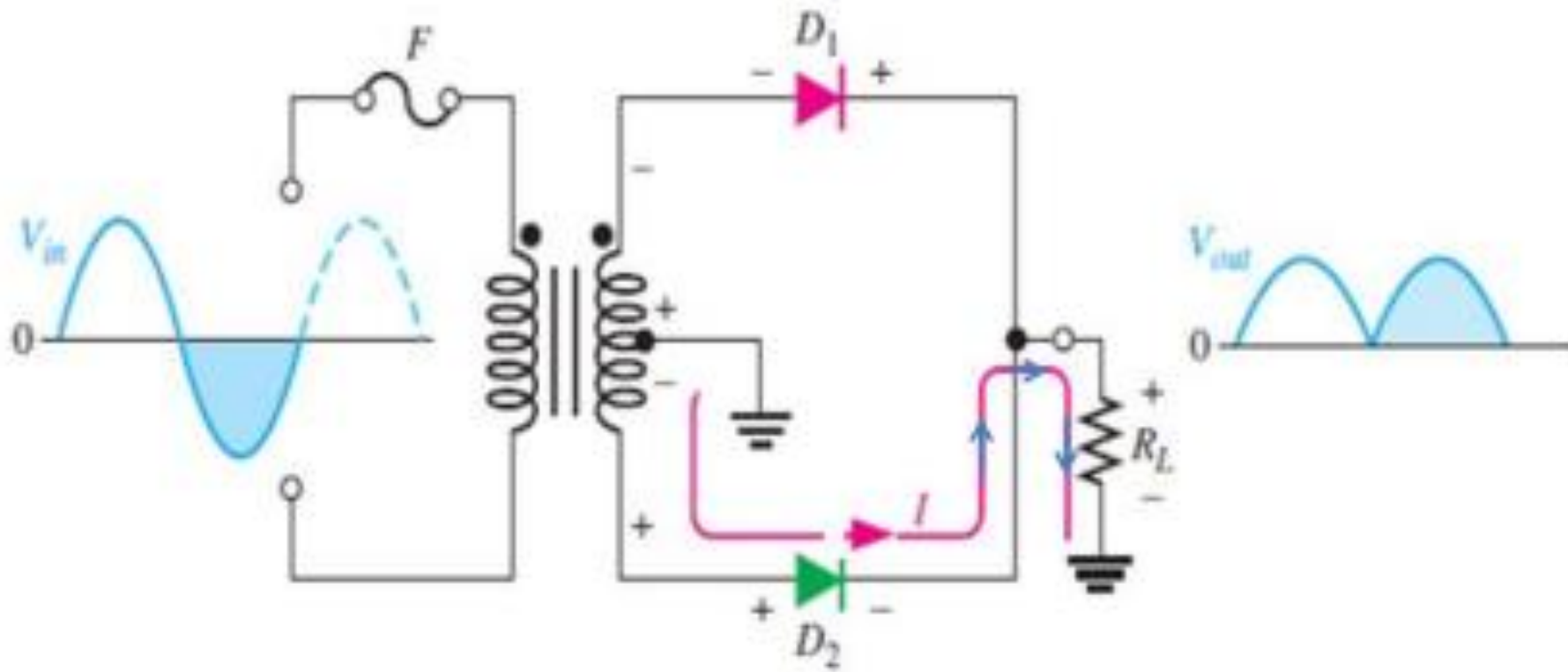- This condition will forward-bias diode D_2 and reverse biases diode D_1 .
- The current path is through D_2 and the load resistor R_L , as indicated





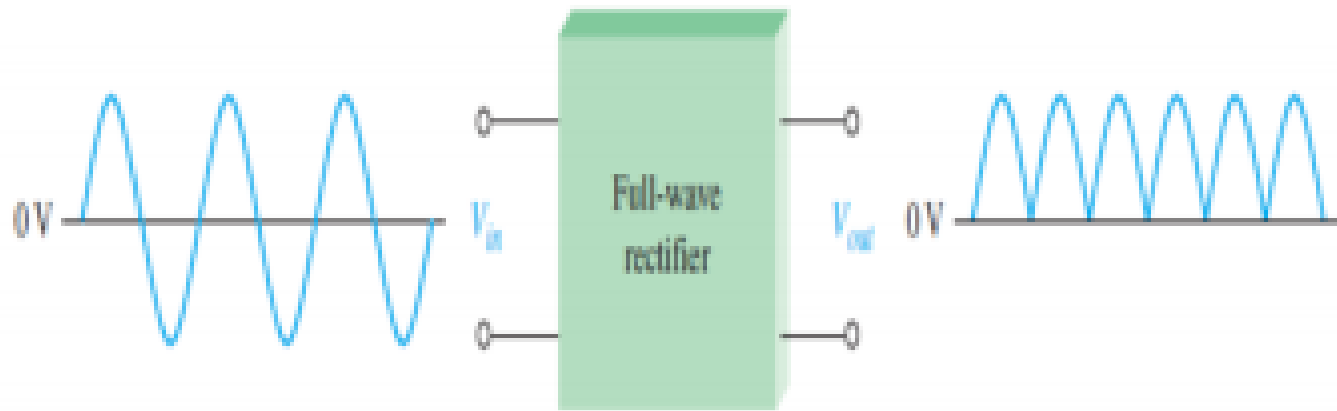- ❖ The output current during both the positive and negative portions of the input cycle is in the same direction through the load
- ❖ The output voltage developed across the load resistor is a full-wave rectified dc voltage, as shown



$$f_o = 2f_i$$

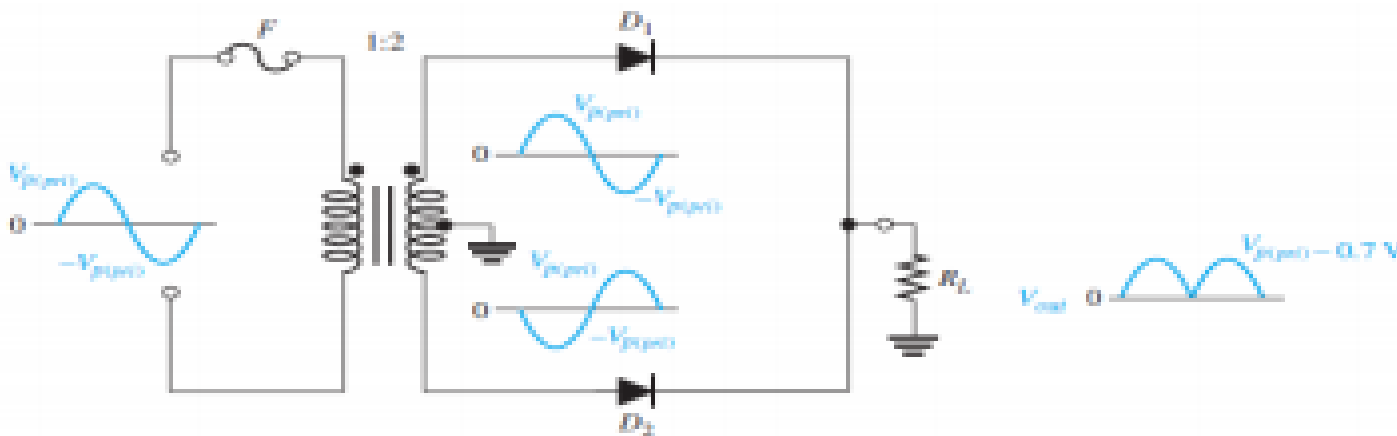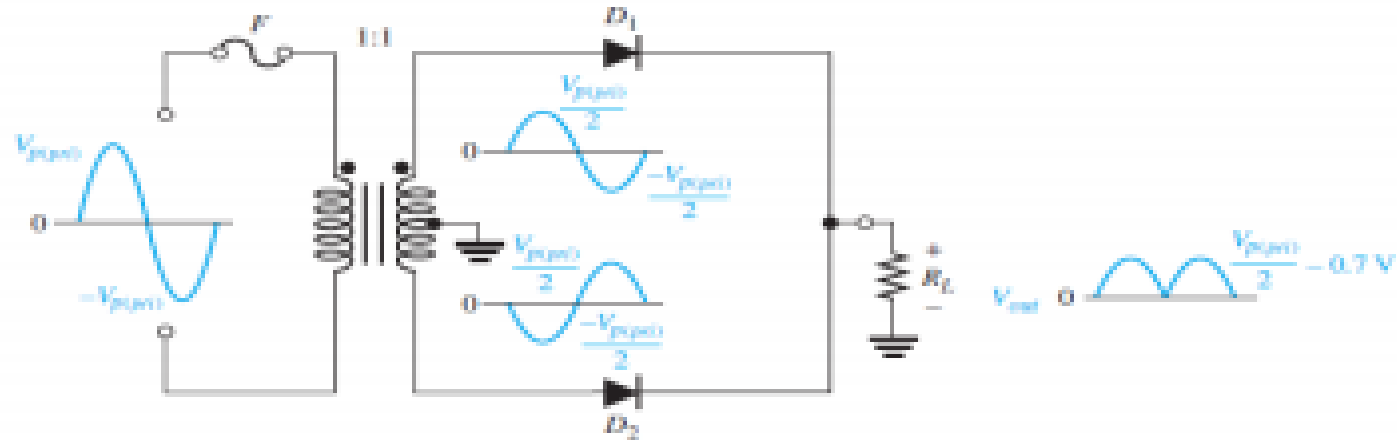
Effect of the Turns Ratio on the Output Voltage



When D_1 is on , while D_2 off

The peak inverse voltage across D_2 will be
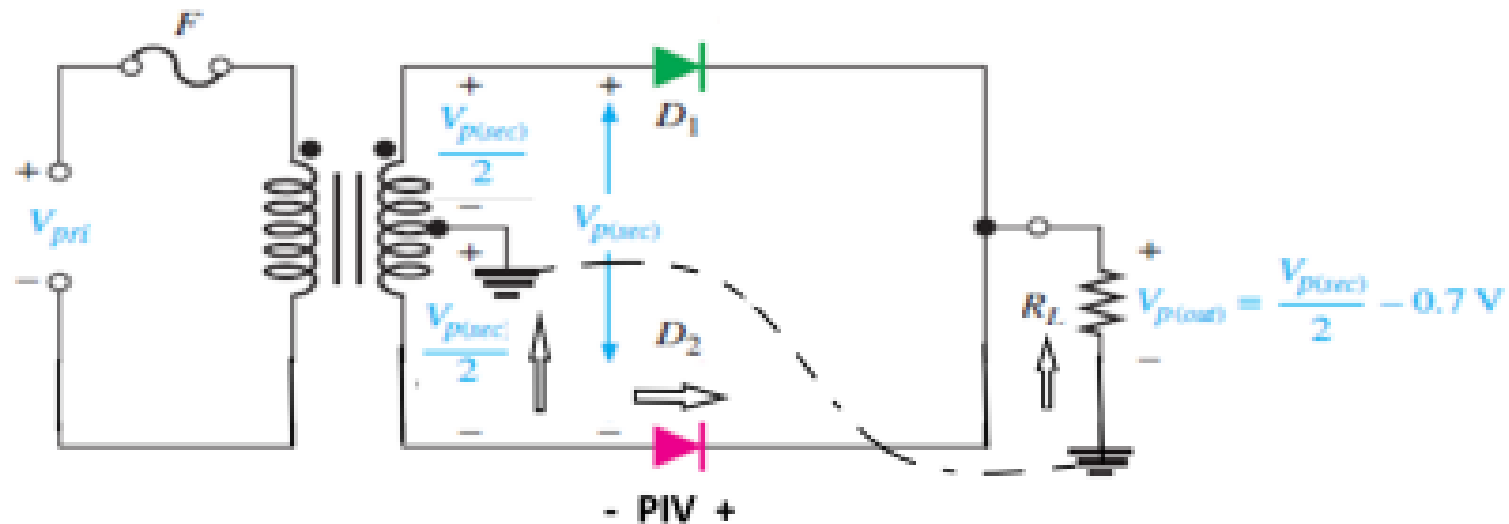
$$PIV = V_{p(out)} + \left(\frac{V_{P(sec)}}{2} \right) = \left(\frac{V_{P(sec)}}{2} - 0.7 \right) + \left(\frac{V_{P(sec)}}{2} \right) = V_{P(sec)} - 0.7$$




Since $V_{p(out)} = (V_{p(sec)}/2) - 0.7$

Then

$$PIV = 2V_{P(out)} + 0.7$$

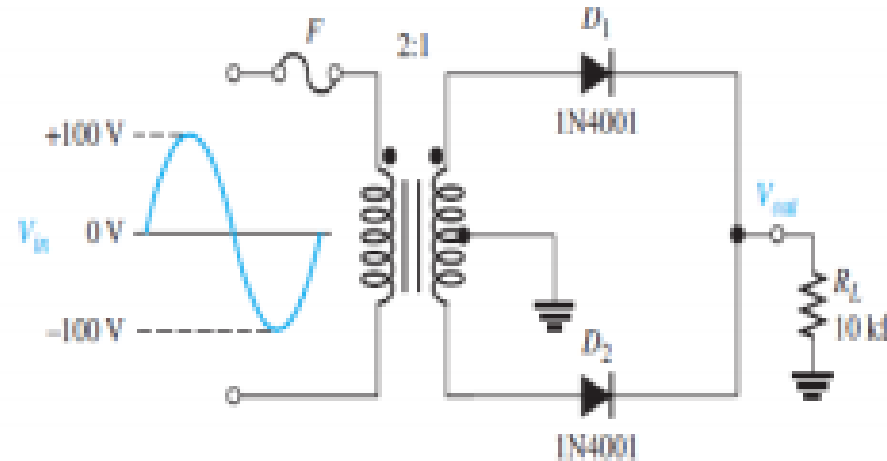Example


For the circuit shown, find the PIV?. The sketch V_{out}



$$V_{p(sec)} = nV_{p(pri)} = 0.5(100 \text{ V}) = 50 \text{ V}$$

$$V_{p(out)} = (V_{p(sec)}/2) - 0.7 = (50/2) - 0.7 = 24.3 \text{ V}$$
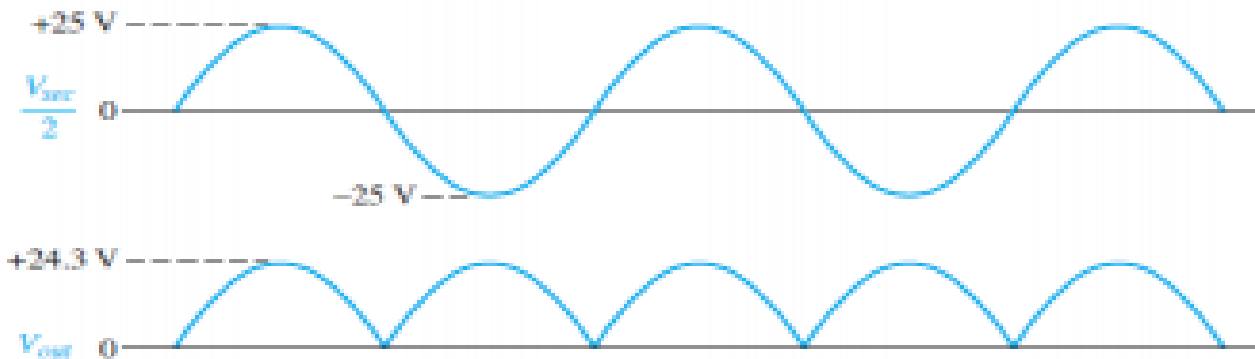
$$PIV = 2V_{p(out)} + 0.7 = 2 * (24.3) + 0.7 = 49.3 \text{ V}$$



Thank
you

