



Electronic Devices and Circuits

EME306

(Summer 2021-2022)

Lecture 9



Diode Types and Applications

INSTRUCTOR

Dr / Ayman Soliman

➤ Contents

- 1) DIODE LIMITERS (CLIPPER)
- 2) Biased Limiters
- 3) THE ZENER DIODE
- 4) Zener applications
- 5) Zener Limiter
- 6) Other Diode Types

DIODE LIMITERS (CLIPPER)

- Positive Diode Limiters
- Figure shows a diode positive limiter (also called clipper) that limits or clips the positive part of the input voltage.

At +ve half cycle

- If $V_{in} < 0.7\text{ v}$, diode off

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

So V_{out} is directly proportional to V_{in}


- If $V_{in} \geq 0.7\text{ v}$, diode on, $V_{out} = 0.7\text{ v}$

At -ve half cycle

- Diode off and

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

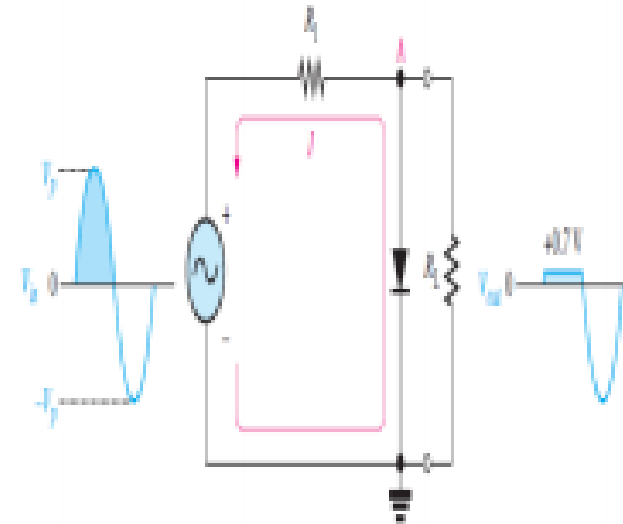So V_{out} is directly proportional to V_{in}



Negative Diode Limiters

At +ve half cycle

- Diode off, so

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

So V_{out} is directly proportional to V_{in}


At -ve half cycle

- If $v_{in} > (-0.7)$, diode off and

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

So V_{out} is directly proportional to V_{in}

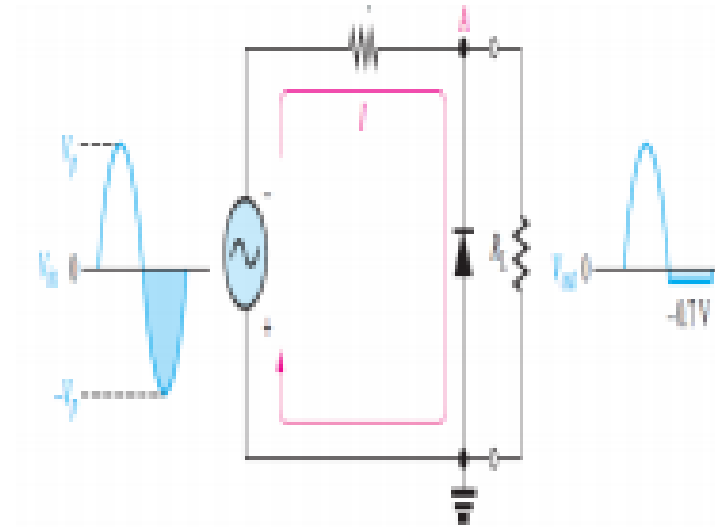- If $v_{in} \leq (-0.7)$, diode on and $V_{out} = -0.7v$




Example

- What would you expect to see displayed on an oscilloscope connected across R_L in the limiter shown in Figure?


At +ve half cycle

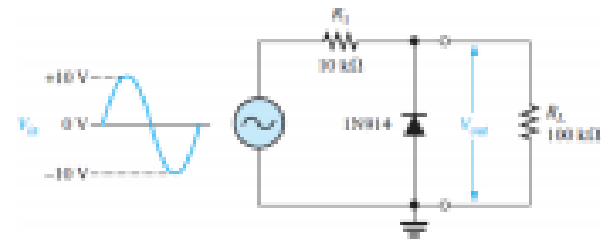- Diode off, so $V_{out} = \left(\frac{R_L}{R_1 + R_L} \right) V_{in}$



So V_{out} is directly proportional to V_{in}
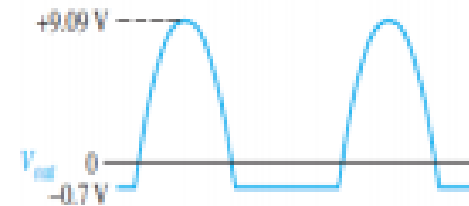
$$V_{P(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{P(in)} = \left(\frac{100}{10 + 100} \right) 10 = 9.09V$$



At -ve half cycle

- If $v_{in} > (-0.7)$, diode off and $V_{out} = \left(\frac{R_L}{R_1 + R_L} \right) V_{in}$

So V_{out} is directly proportional to V_{in}

- If $v_{in} \leq (-0.7)$, diode on and $V_{out} = -0.7v$

Biased Limiters

➤ +ve biased limiter

For +ve half cycle

- If $v_{in} < (V_{Bias} + 0.7)$ diode is off, and

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

So V_{out} is directly proportional to V_{in}


- If $v_{in} \geq (V_{Bias} + 0.7)$ diode will be on, and $V_{out} = (V_{Bias} + 0.7)$

For -ve half cycle

Diode is off, so

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

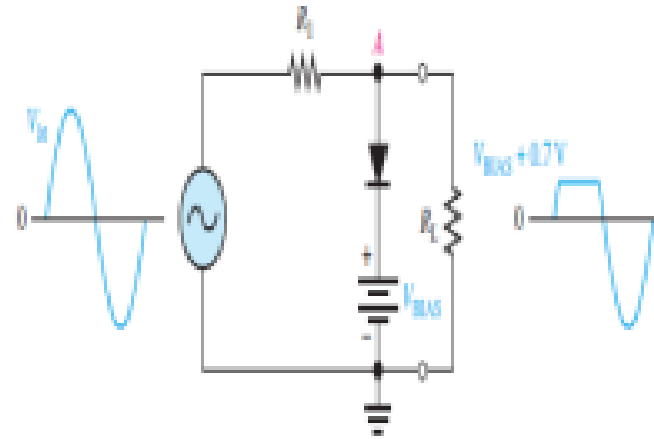So V_{out} is directly proportional to V_{in}




-ve biased limiter

For +ve half cycle

- Diode is off all times, then

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

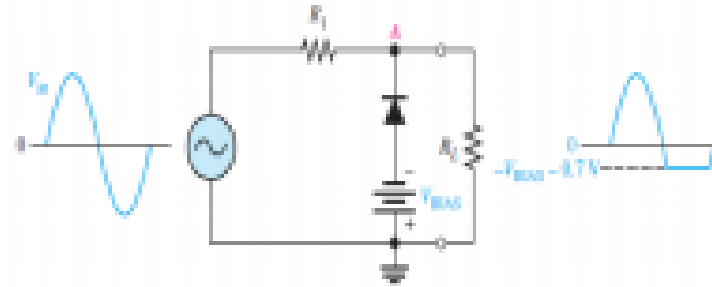So V_{out} is directly proportional to V_{in}



For - ve half cycle

- If $v_{in} > -(V_{Bias} + 0.7)$ diode is off, and


$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)} \text{ So } V_{out} \text{ is directly proportional to } V_{in}$$

- If $v_{in} \leq -(V_{Bias} + 0.7)$ diode will be on, and $V_{out} = -(V_{Bias} + 0.7)$

Another circuits

For +ve half cycle

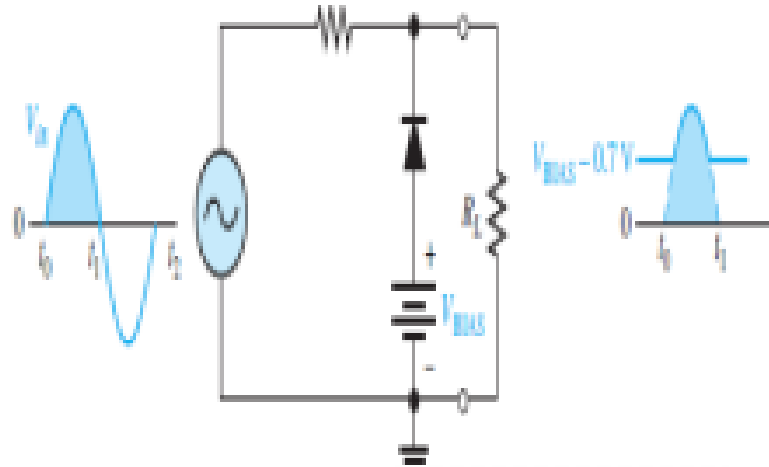- If $v_{in} < (V_{Bias} - 0.7)$ diode will be on , and $V_{out} = V_{Bias} - 0.7$




- If $v_{in} \geq (V_{Bias} - 0.7)$ diode will be off , and

$$V_{(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{(in)}$$

, So V_{out} is directly proportional to V_{in}

For -ve half cycle

diode will be on , and $V_{out} = V_{Bias} - 0.7$

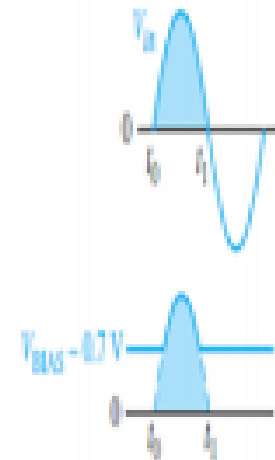

EXAMPLE 2

- Figure shows a circuit combining a positive limiter with a negative limiter. Determine the output voltage waveform.

For +ve half cycle

D_2 will be off all times

For diode D_1



- ❑ If $v_{in} < (5+0.7)$, D_1 will be off and $V_{out} = V_{in}$
- ❑ If $v_{in} \geq (5+0.7)$ diode will be on, and $V_{out} = 5+0.7 = 5.7V$

For -ve half cycle

D_1 will be off all times


For diode D_2

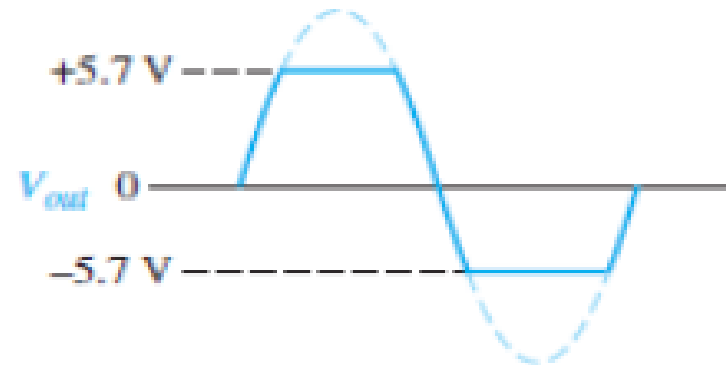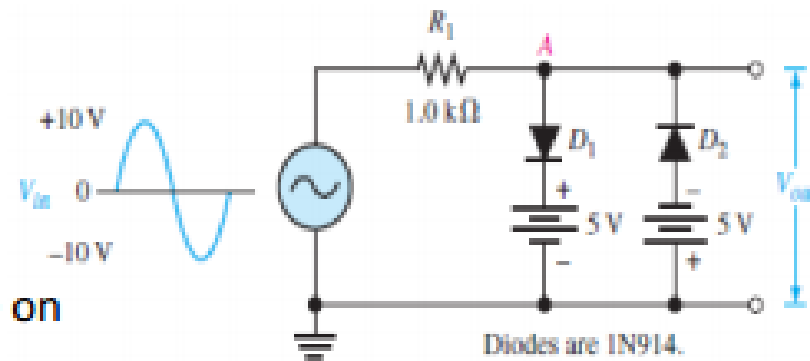- ❑ If $v_{in} > (-5-0.7)$, D_2 will be off and $V_{out} = V_{in}$
- ❑ If $v_{in} \leq (-5-0.7)$ diode will be on, and $V_{out} = -5-0.7 = -5.7V$




THE ZENER DIODE

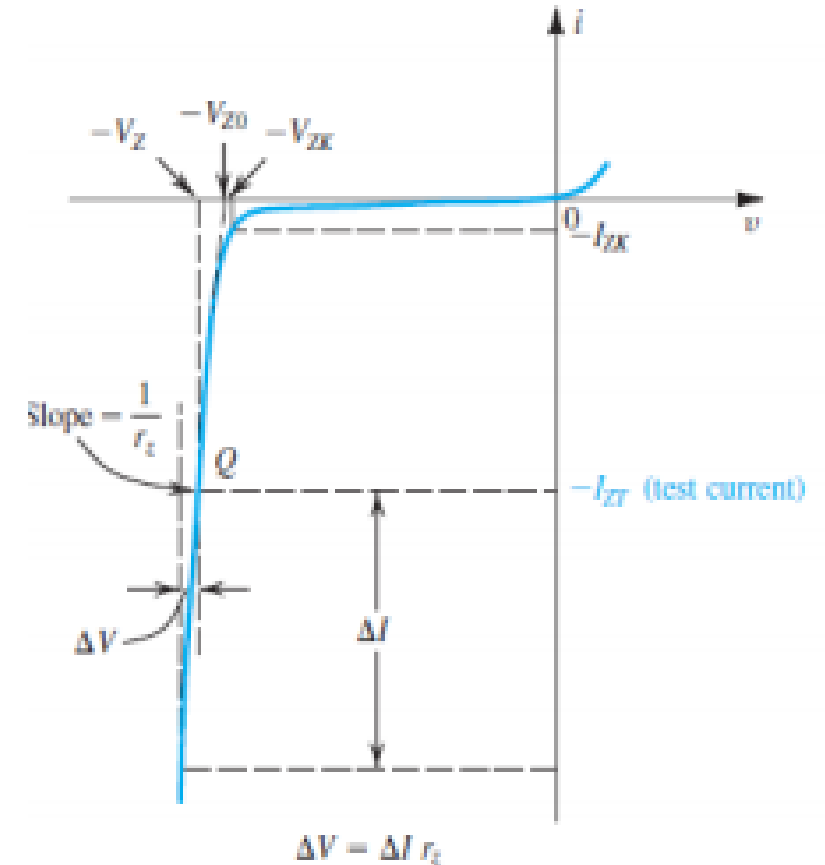- A zener diode is a silicon pn junction device that is designed for operation in the reverse-breakdown region.
- The breakdown voltage of a zener diode is set by carefully controlling the doping level during manufacture.




Zener Equivalent Circuits

1- The ideal model

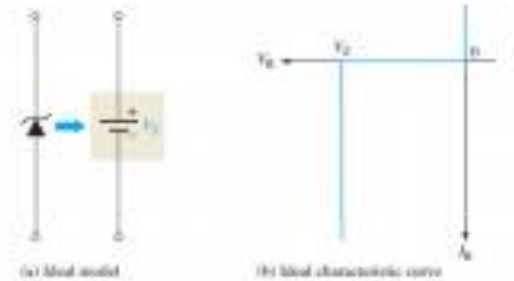

2- The practical model

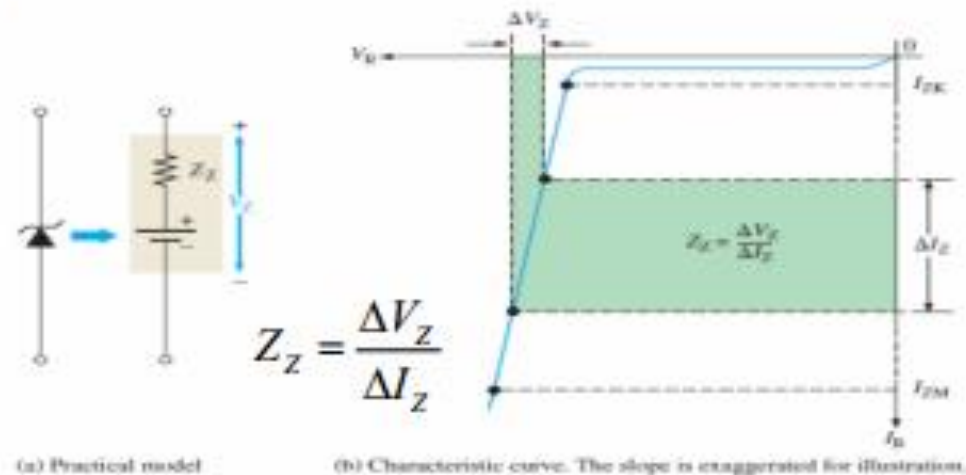

Z_z (r_z) is the dynamic resistance and it is in the range of a few ohms to a few tens of ohms

For $V_Z < V_{Z0}$


$$V_Z = V_{Z0} - \Delta I_Z r_z$$

For $V_Z > V_{Z0}$

$$V_Z = V_{Z0} + \Delta I_Z r_z$$

Zener power dissipation

$$P_Z = V_Z * I_Z$$

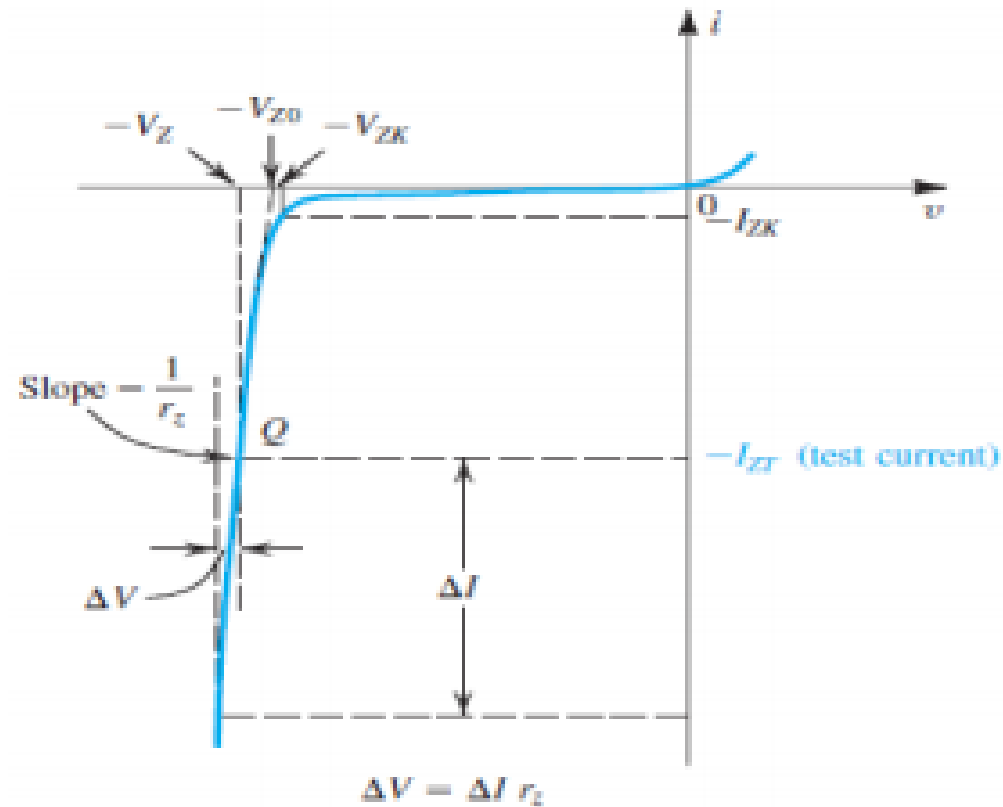

The lower the value of r_z is, the more constant the Zener voltage remains as its current varies, and thus used in the design of voltage regulators.

Zener applications

➤ Zener Regulation with a Variable input

Example

Determine the minimum and the maximum input voltages that can be regulated by the zener diode. Given $V_Z = 5.1\text{ V}$ at $I_Z = 49\text{ mA}$, $I_{ZK} = 1\text{ mA}$, and $r_z = 7\Omega$ at I_Z , and $P_{Dmax} = 1\text{ watt}$

For $I_Z = 1\text{ mA}$ and $V_Z < V_{ZO}$



$$V_Z = V_{ZO} - \Delta I_Z r_z$$

$$V_Z = 5.1 - (49 - 1)\text{mA} * 7\Omega = 4.76\text{v}$$

$$V_{in(\min)} = V_Z + I_{ZK} * 100\Omega$$

$$V_{in(\min)} = 4.76 + 1\text{mA} * 100\Omega$$

$$= 4.86\text{v}$$

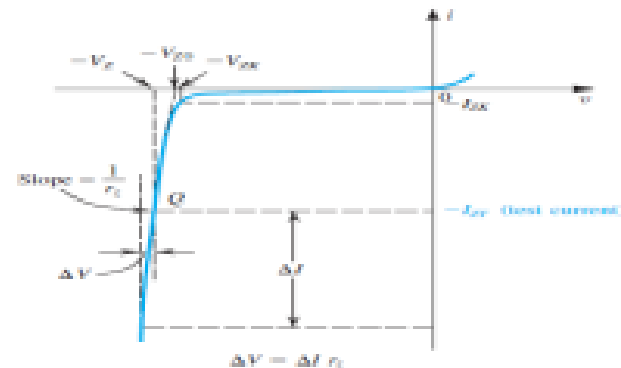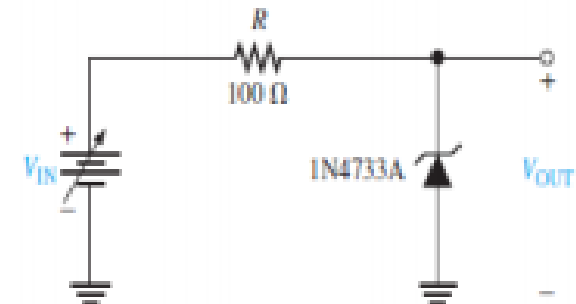

For $P_{Dmax} = 1 \text{ watt}$,
 then $I_{zmax} = (P_{Dmax}/V_z)$
 $= (1W/5.1v) = 196mA$

For $I_z = 196 \text{ mA}$ and $V_z > V_{z0}$

$$V_z = V_{z0} + \Delta I_z r_z$$



$$V_z = 5.1 + (196 - 49) \text{ mA} * 7\Omega = 6.129 \text{ v}$$

$$V_{in(max)} = V_z + I_{zm} * 100\Omega$$

$$V_{in(max)} = 6.129 + 196 \text{ mA} * 100\Omega$$




$$= 25.729 \text{ v}$$
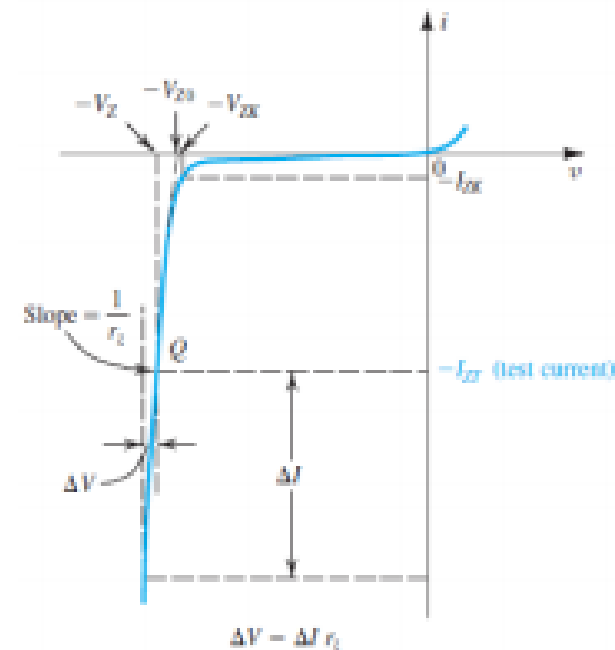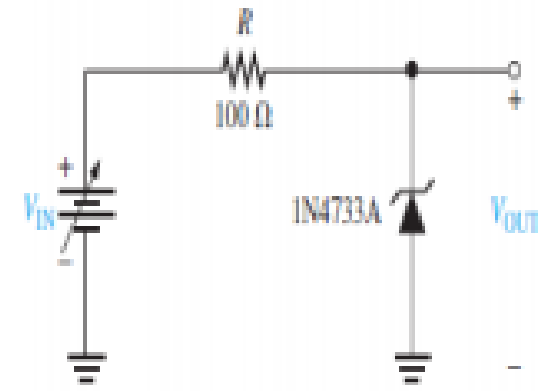
$$4.86 \text{ v} < V_{in} < 25.729 \text{ v}$$



Zener Limiter

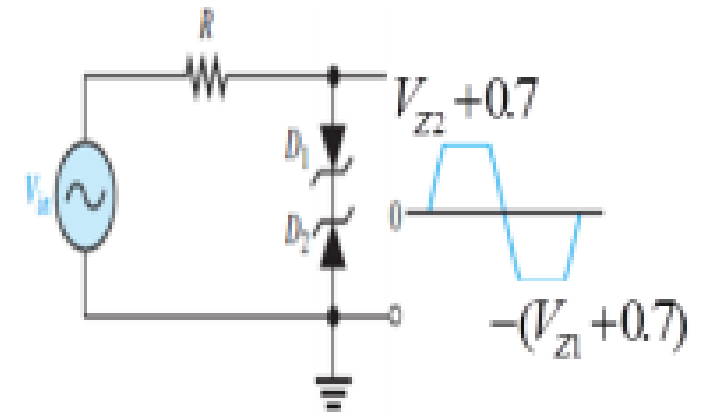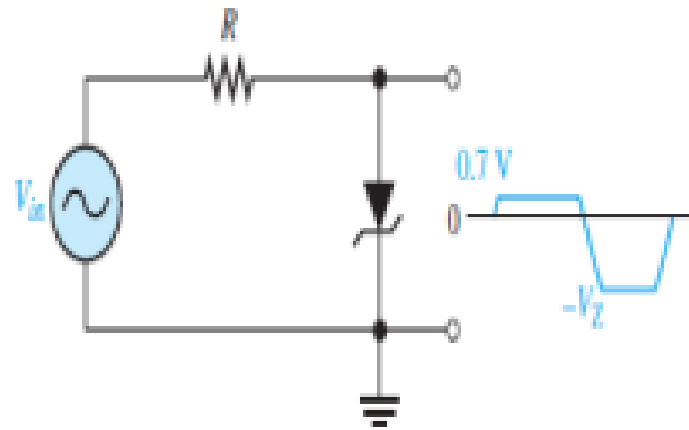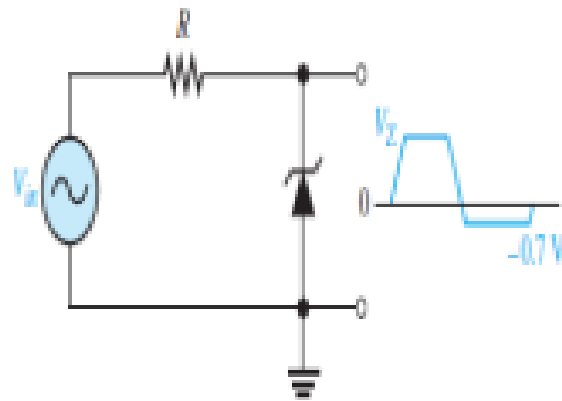- In forward region connection, it work as regular diode, but in reverse bias connection work as zener diode (battery)





Example

For the circuit shown, sketch the o/p voltage

For +ve half cycle,
 D_1 work as regular diode and have voltage drop of 0.7v, while D_2 work as zener diode with voltage drop 5.1v, so $V_o = 0.7 + 5.1 = 5.8v$

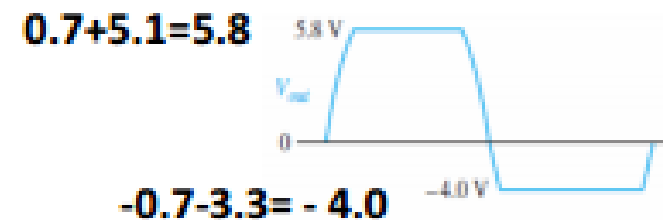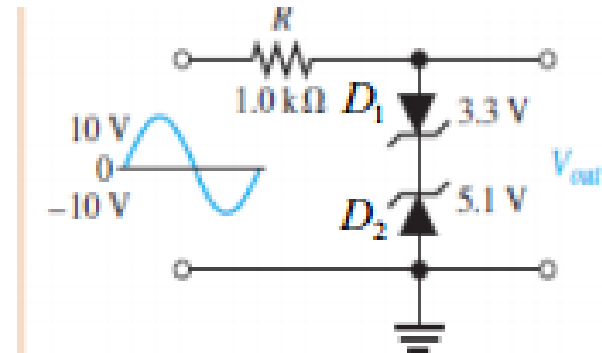For -ve half cycle,
 D_2 work as regular diode and have voltage drop of - (-0.7)v, while D_1 work as zener diode with voltage drop (-3.3)v, so $V_o = -0.7 - 3.3 = -4.0$





Example

For the circuit shown, sketch the o/p voltage

For +ve half cycle,
 D_2 work as regular diode and have voltage drop of 0.7v , while D_1 work as zener diode with voltage drop 6.2 v , so
 $V_o = 0.7 + 6.2 = 6.9\text{ v}$

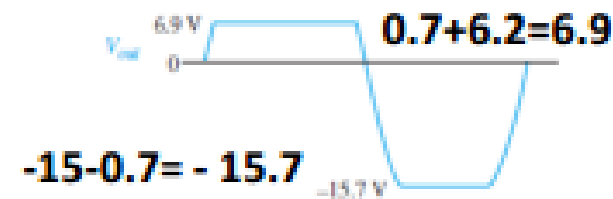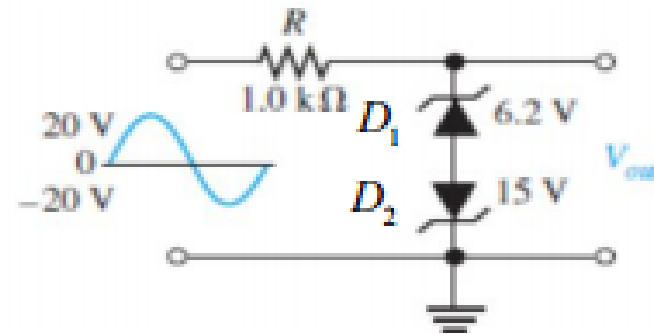
For -ve half cycle,
 D_1 work as regular diode and have voltage drop of $(-0.7)\text{v}$, while D_2 work as zener diode with voltage drop $(-15.0)\text{v}$, so
 $V_o = -0.7 - 15.0 = -15.7\text{ v}$



Other diodes types

1-Varactor


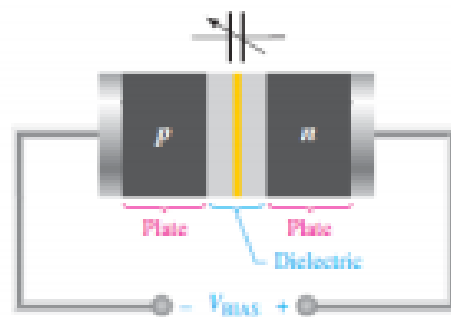
- ❑ **Varactor** is a diode that always operates in reverse bias
- ❑ It is doped to maximize the inherent capacitance of the depletion region.
- ❑ The depletion region acts as a capacitor dielectric because of its nonconductive characteristic.
- ❑ The p and n regions are conductive and act as the capacitor plates
- ❑ **Act as variable capacitor**



$$C = \frac{\epsilon A}{d}$$

2- The Light-Emitting Diode (LED)

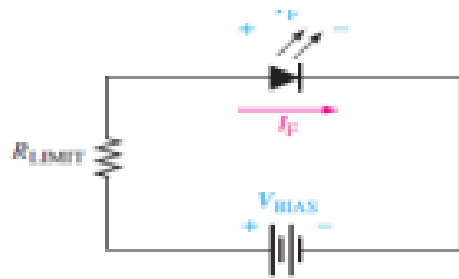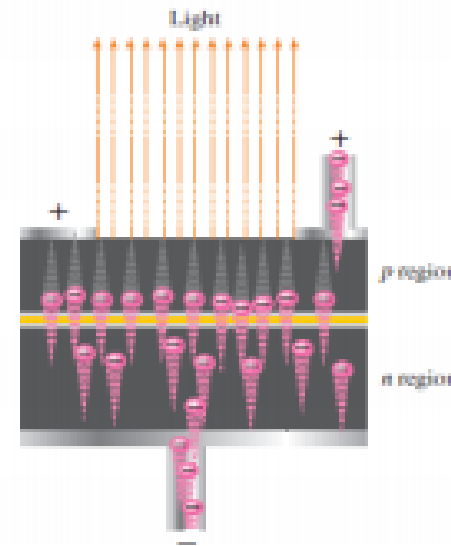- ❑ For forward-biased, electrons cross the pn junction from the n -type material and recombine with holes in the p -type material.
- ❑ these free electrons are in the conduction band and at a higher energy than the holes in the valence band.
- ❑ The difference in energy between the electrons and the holes corresponds to the energy of visible light





(a) Typical small LEDs for indicators




LED lamps are designed to work in 120 V standard fixtures.


Traffic lights




i. Seven segment display

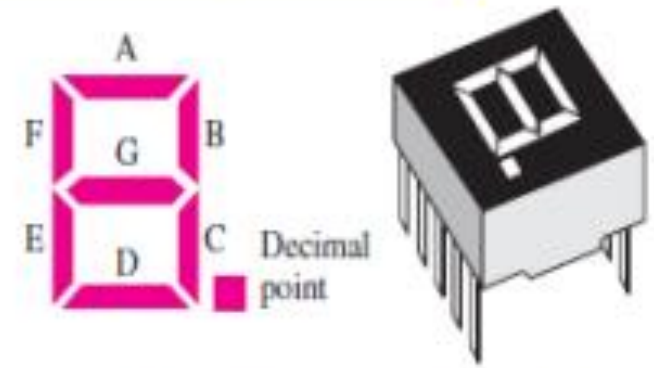

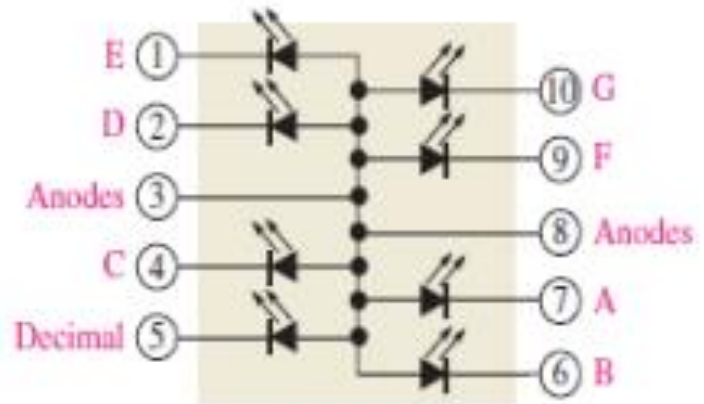(a) LED segment arrangement and typical device



(b) Common anode

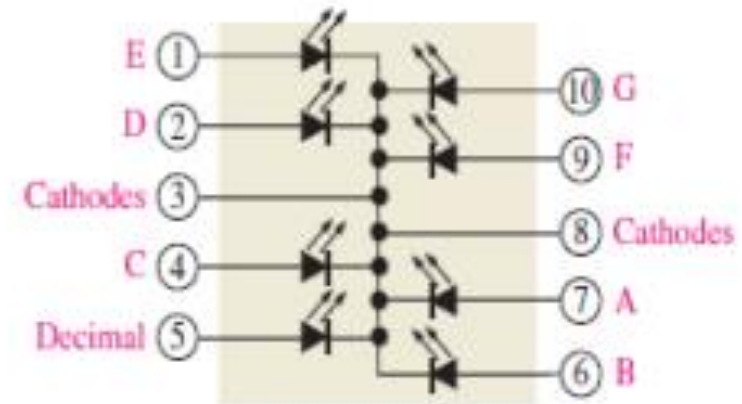

(c) Common cathode

Thank
you

