




# Electronics 1

BSC 113

Fall 2022-2023

Lecture 5

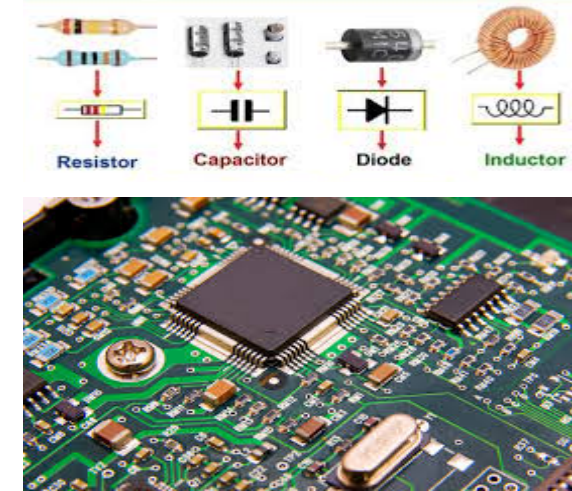

# Mesh analysis, Superposition, Thevenin's & Norton theorems

**INSTRUCTOR**

DR / AYMAN SOLIMAN

## ➤ Contents

- 1) Mesh analysis
- 2) super-mesh
- 3) CASE 1
- 4) CASE 2
- 5) Superposition
- 6) Thevenin's theorem
- 7) Norton theorem




## ➤ Terms of describing circuits

| Name             | Definitions   |
|------------------|---|
| Node             | A point where two or more circuit elements join                                     |
| Essential node   | A node where three or more circuit elements join                                    |
| Branch           | A path that connects two nodes  |
| Essential branch | A path which connects two essential nodes without passing through an essential node |
| Loop             | A path whose last node is the same as the starting node                             |
| mesh             | A loop that does not enclose any other loops  |
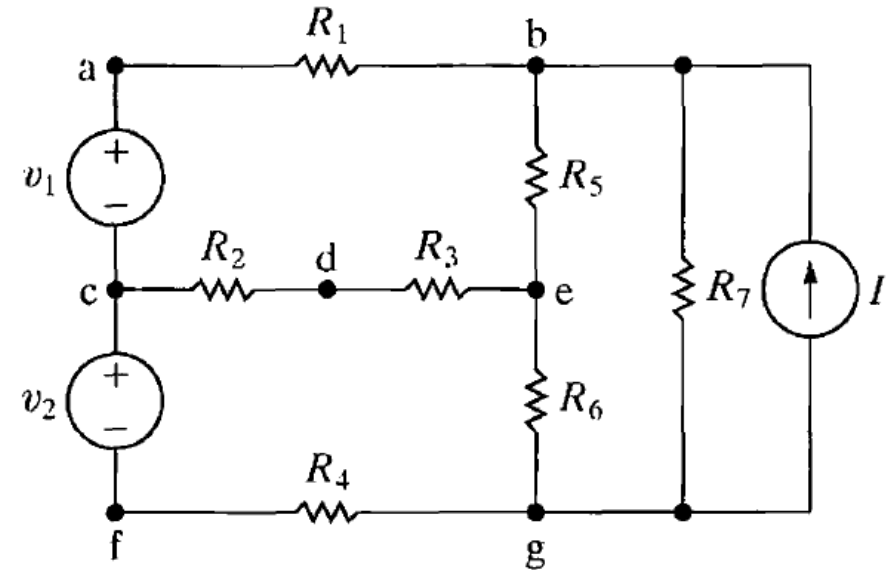
## ➤ Example 1

➤ For the circuit in the figure, identify

- all nodes.
- all essential nodes.
- all branches.
- all essential branches.
- all meshes.
- two loops that are not meshes.



## ➤ Example 1


- The nodes are a, b, c, d, e, f, and g.
- The essential nodes are b, c, e, and g.
- The branches are  $v_1$ ,  $v_2$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $R_6$ ,  $R_7$  and  $I$ .
- The essential branches are:

$v_1 - R_1$  ,

$R_2 - R_3$  ,

$v_2 - R_4$  ,

$R_5, R_6, R_7$  and  $I$

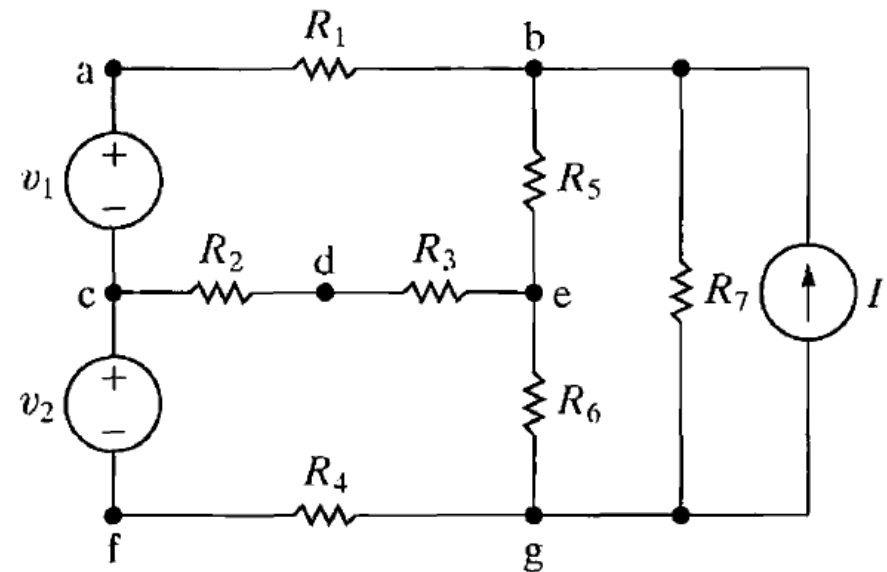

## ➤ Example 1


e) The meshes are:

$$v_1 - R_1 - R_5 - R_3 - R_2,$$

$$v_2 - R_2 - R_3 - R_6 - R_4,$$

$$R_5 - R_7 - R_6 \text{ and}$$

$$R_7 - I$$

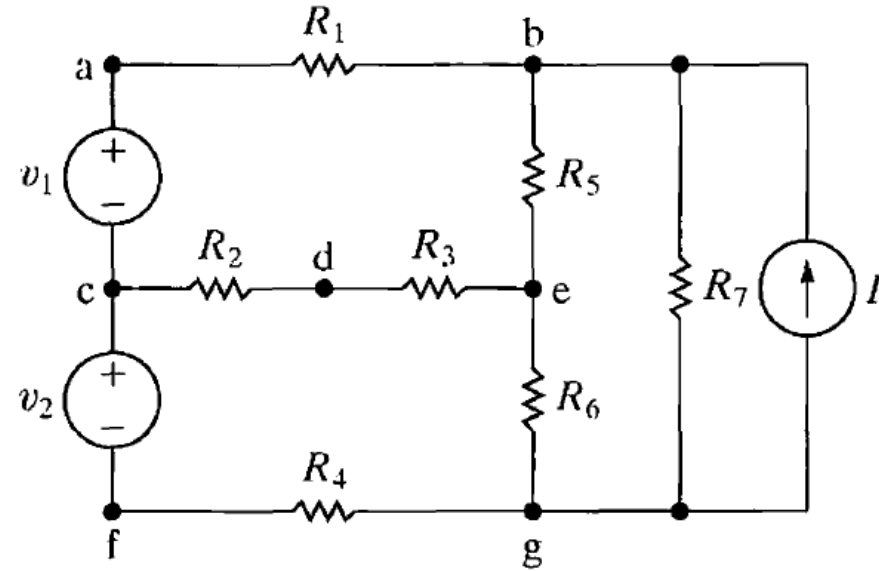


f) The two loops that are not meshes are  $v_1 - R_1 - R_5 - R_6 - R_4 - v_2$  and  $I - R_5 - R_6$ , because there are two loops within them.

# Mesh Analysis Method
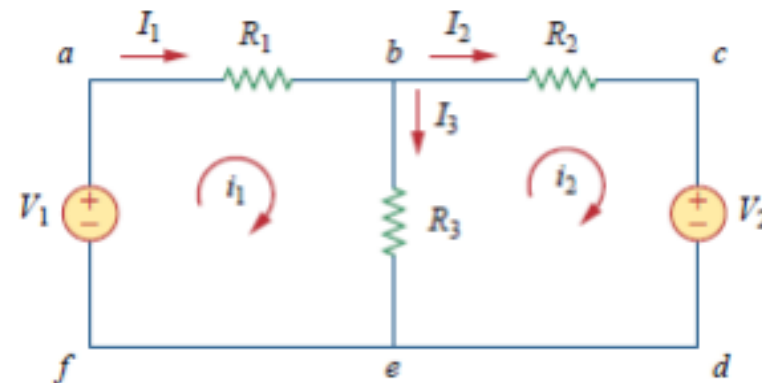
## □ Mesh analysis

- In the mesh analysis of a circuit with  $n$  meshes, we take the following three steps.
1. Assign **mesh** currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
  2. Apply **KVL** to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
  3. **Solve** the resulting  $n$  simultaneous equations to get the mesh currents.





## □ Mesh analysis

➤ As shown in figure

loop 1:


$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

loop 2:

$$R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0$$


After we will solve the two equation we can find:
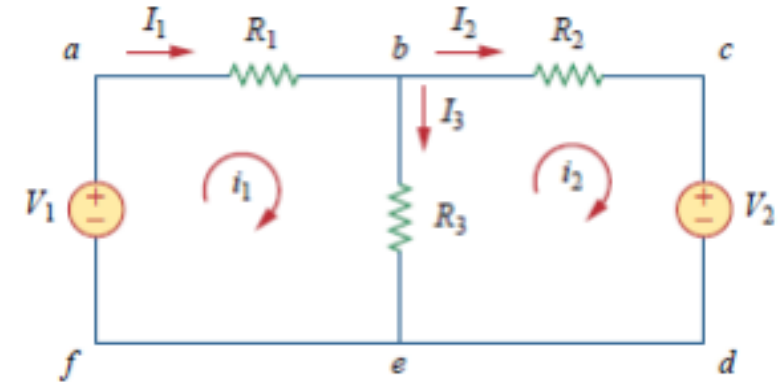
$$I_1 = i_1, \quad I_2 = i_2 \quad \text{and} \quad I_3 = i_1 - i_2$$


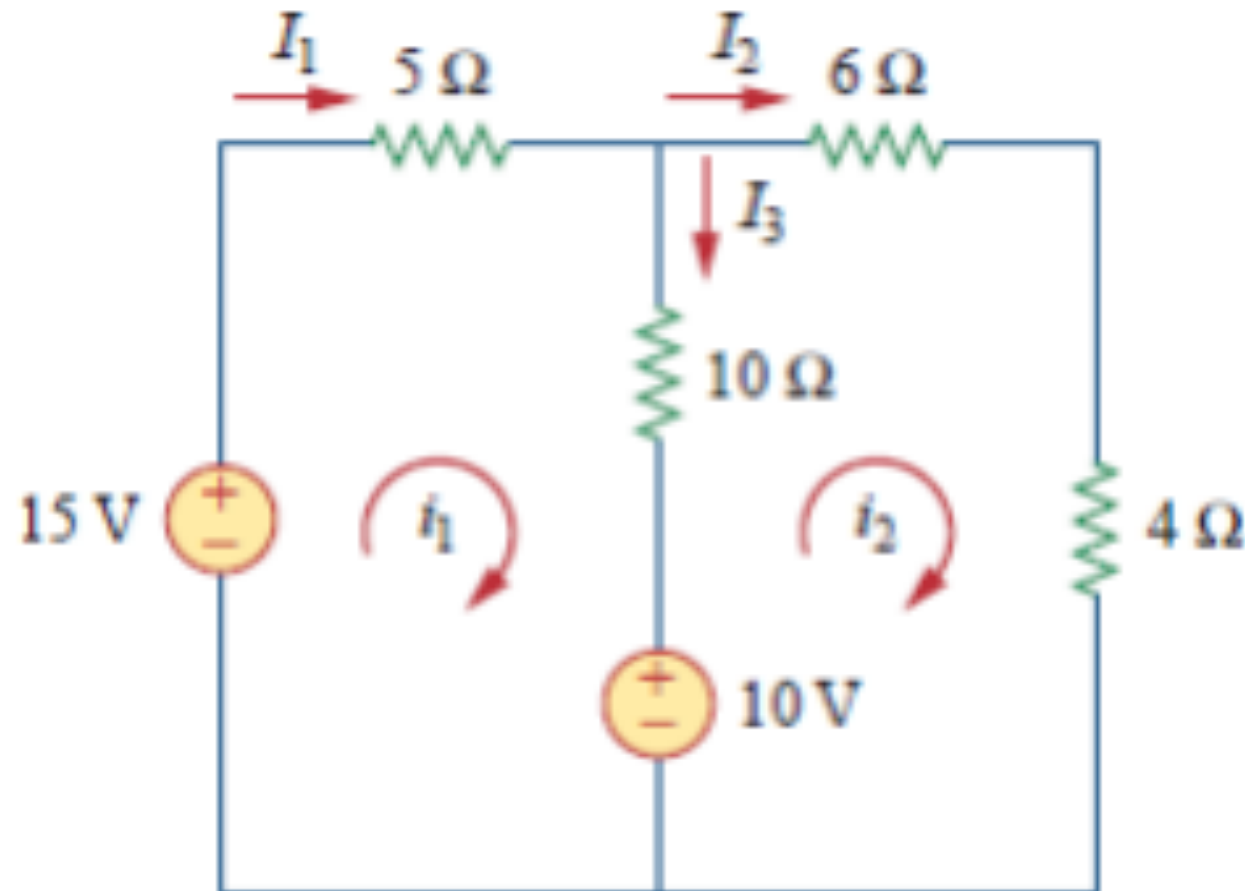
## □ Example 2

- Find the branch currents  $I_1$ ,  $I_2$  and  $I_3$  using mesh analysis.



## □ Example 2 solution:

➤ Answer: We first obtain the mesh currents using KVL.

For mesh 1,

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0 \quad (1)$$


and for mesh 2

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0 \quad (2)$$

from (1) and (2)



$$i_1 = i_2 = 1A$$
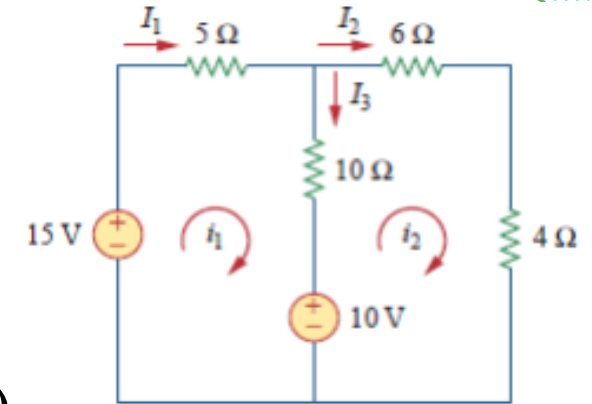
$$I_1 = i_1 = 1A, \quad I_2 = i_2 = 1A \quad \text{and} \quad I_3 = i_1 - i_2 = 0A$$


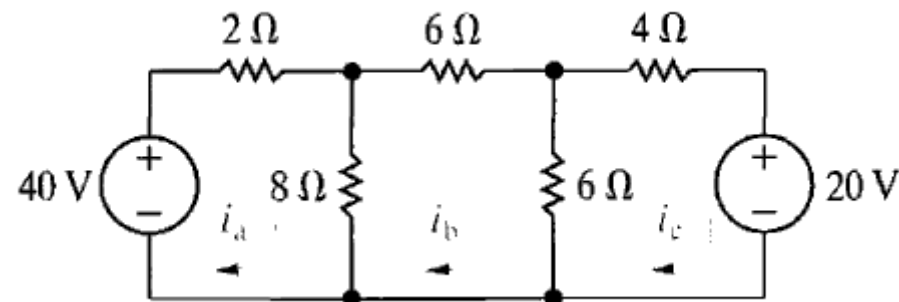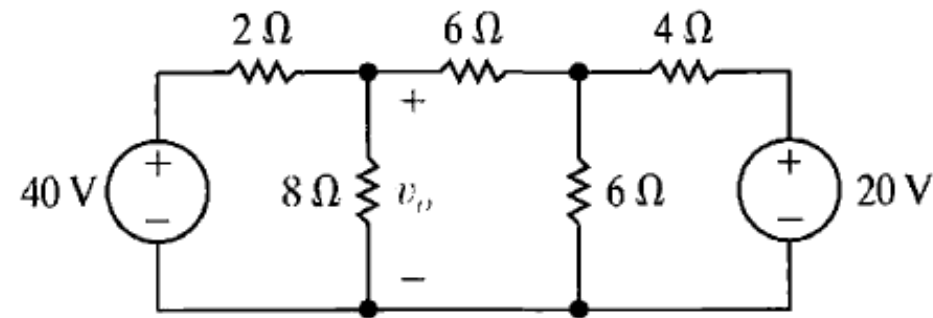
### □ Example 3

- Use the mesh-current method to determine the power associated with each voltage source in the circuit shown.
- Calculate the voltage  $v_o$  across the  $8\ \Omega$  resistor.



### □ Example 3

a) The three meshes equations are:

$$-40 + 2i_a + 8(i_a - i_b) = 0$$

$$8(i_b - i_a) + 6i_b + 6(i_b - i_c) = 0$$

$$6(i_c - i_b) + 4i_c + 20 = 0$$



Therefore, the three mesh currents are

$$i_a = 5.6 \text{ A}, \quad i_b = 2.0 \text{ A}, \quad i_c = -0.80 \text{ A}.$$

The power associated with each voltage source:



$$P_{40\text{V}} = -40i_a = -224 \text{ W}, \quad P_{20\text{V}} = 20i_c = -16 \text{ W}.$$

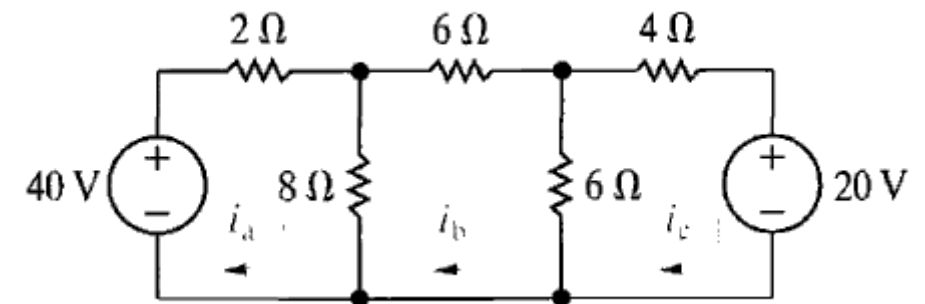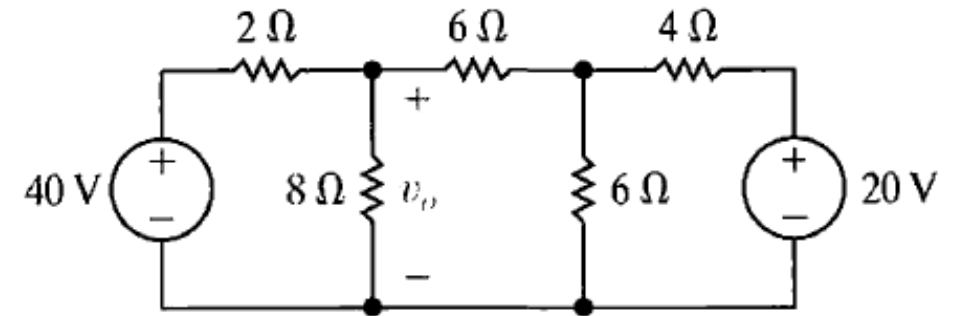b)  $v_o = 8(i_a - i_b) = 8(3.6) = 28.8 \text{ V}.$


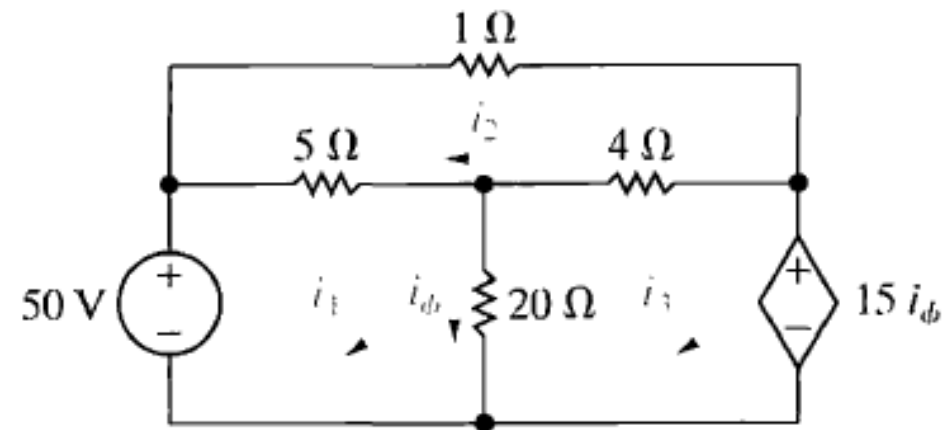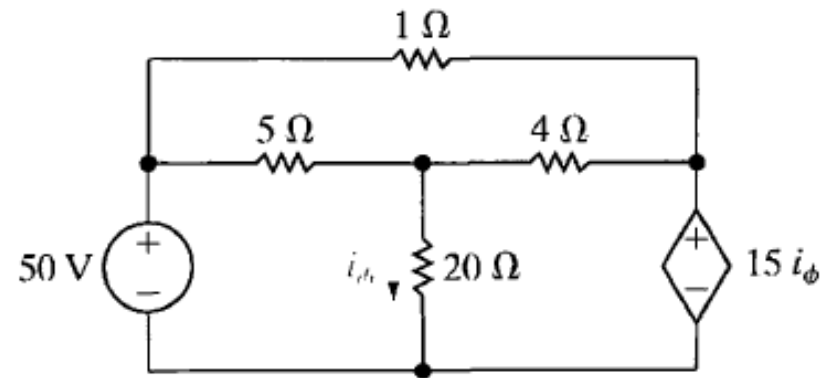
## □ Example 4

Use the mesh-current method of circuit analysis to determine the power dissipated in the  $4\Omega$  resistor in the circuit shown.



## □ Example 4

The three mesh-current equations are:

$$5(i_1 - i_2) + 20(i_1 - i_3) = 50$$

$$5(i_2 - i_1) + i_2 + 4(i_2 - i_3) = 0$$

$$20(i_3 - i_1) + 4(i_3 - i_2) + 15i_\phi = 0$$

We now express the branch current controlling the dependent voltage source in terms of the mesh currents as:



$$i_\phi = i_1 - i_3$$

Therefore, the mesh currents are:

$$i_1 = 29.6 \quad i_2 = 26 \text{ A} \quad i_3 = 28 \text{ A}$$


and
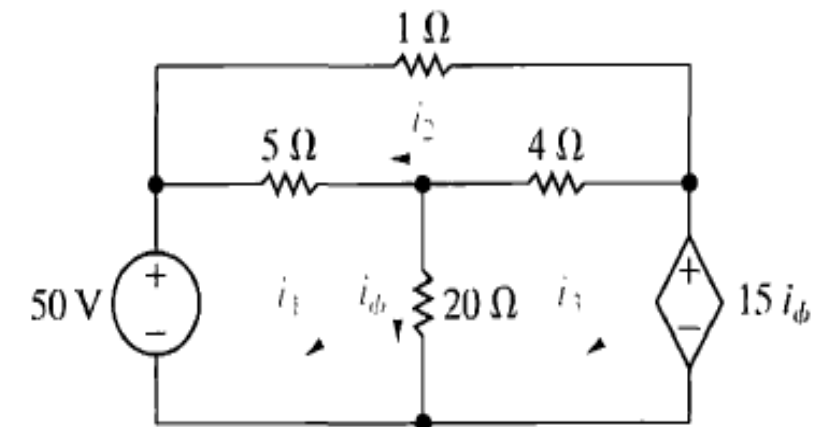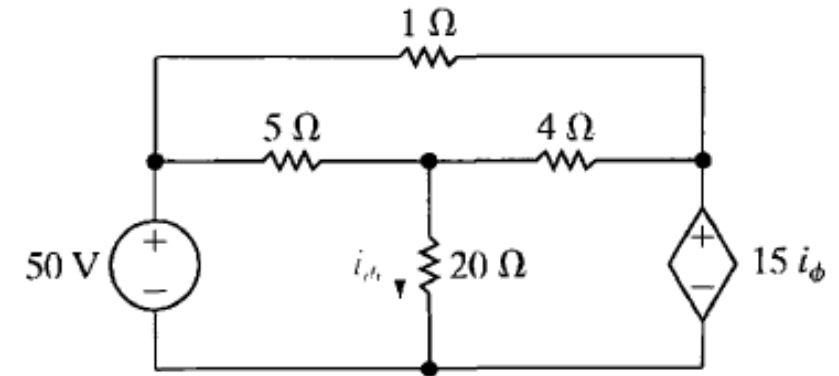
$$P_{4\Omega} = (i_3 - i_2)^2(4) = (2)^2(4) = 16 \text{ W.}$$


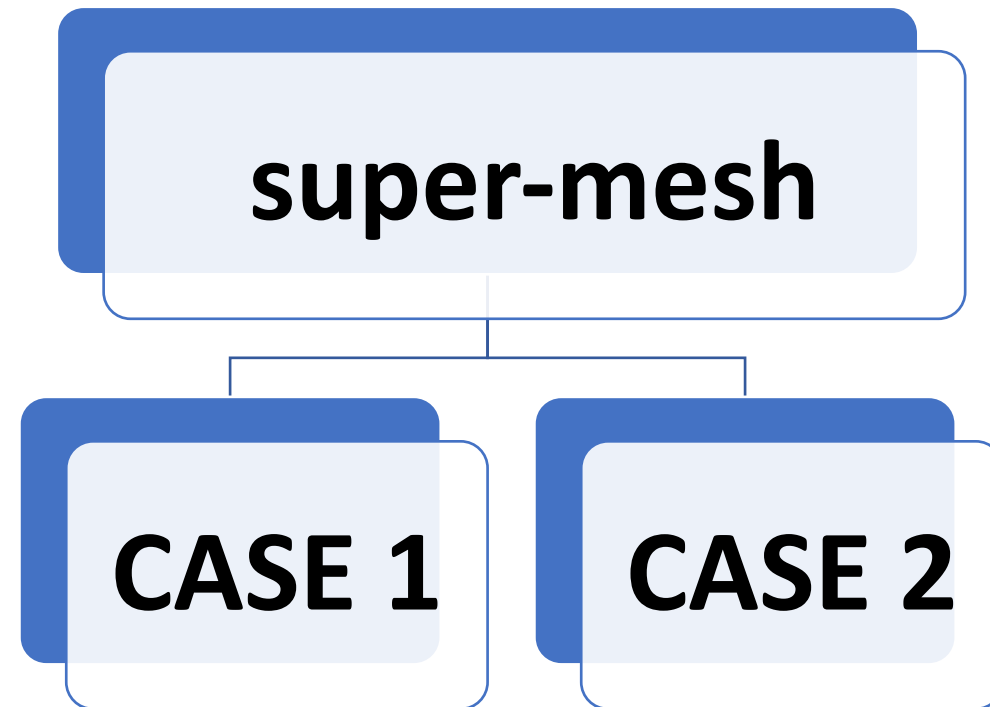
## ❑ super-mesh

- Mesh Analysis with Current Sources is called super-mesh (**A super-mesh results when two meshes have a (dependent or independent) current source in common**) and considers as special case.






## □ CASE 1

- When a **current source exists only in one mesh**
- Consider the circuit in next figure, for example. We set  $i_2 = -5 \text{ A}$  and write a mesh equation for the other mesh in the usual way; that is,



$$-10 + 4i_1 + 6(i_1 - (-5)) = 0 \rightarrow i_1 = -2\text{A}$$

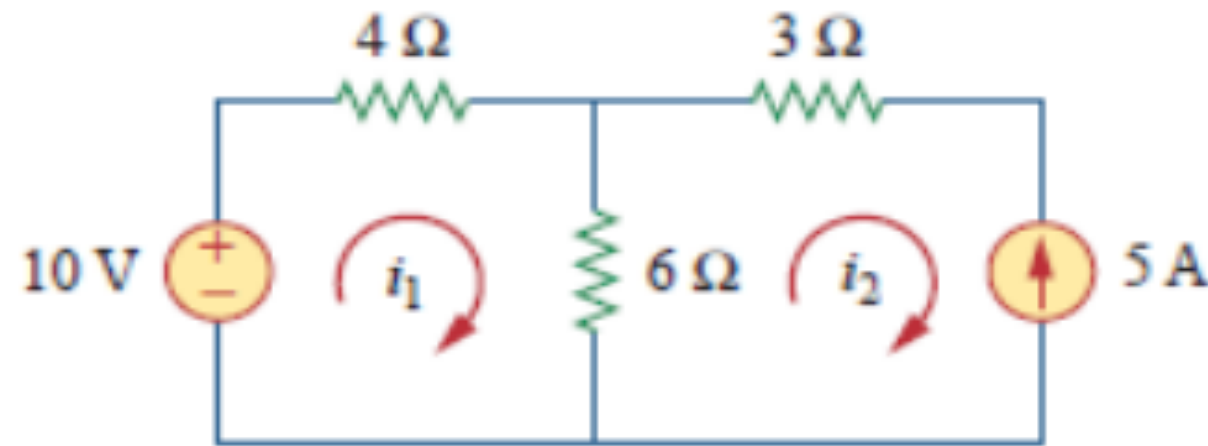- Thus, our analysis is somewhat simplified by this knowledge of the voltage at this node.




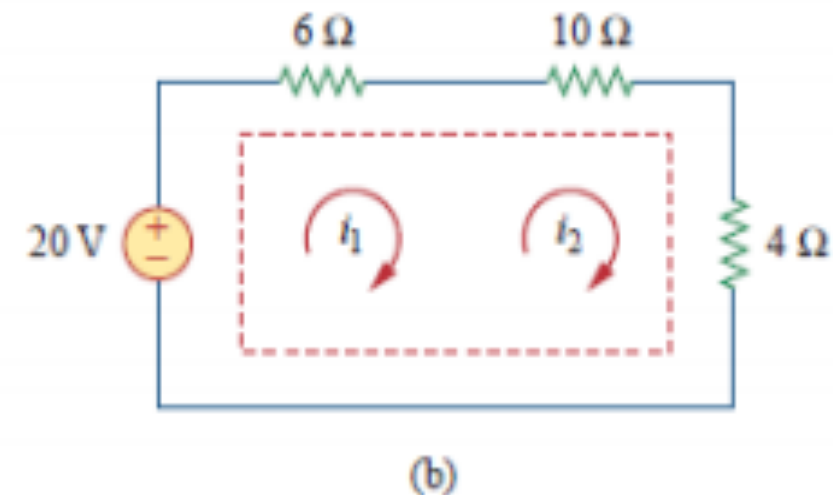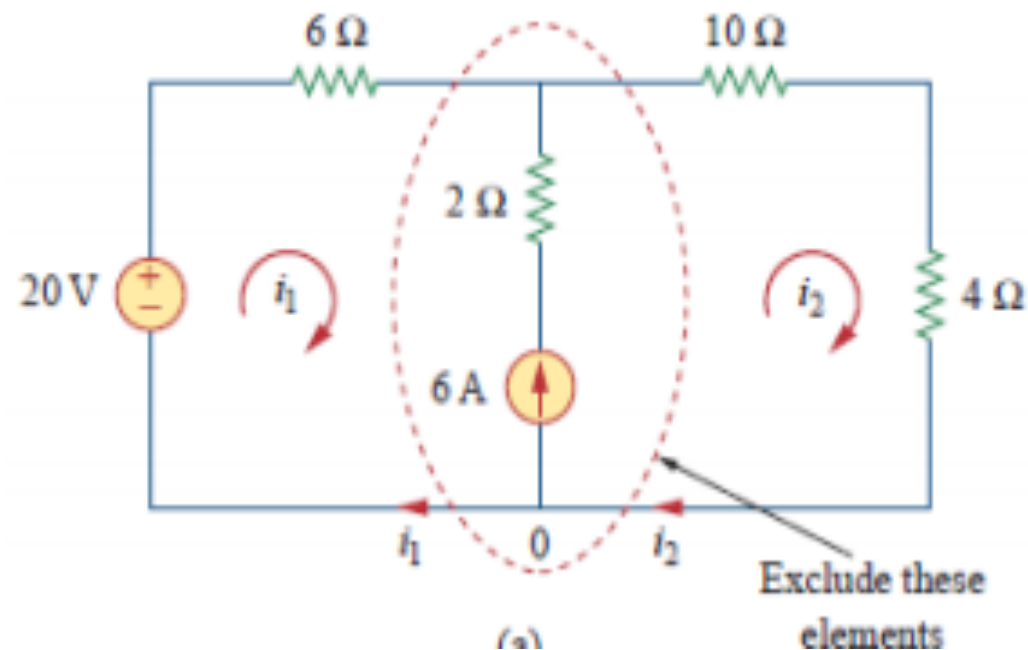
## □ CASE 2

- When a **current source exists between two meshes**
- Consider the circuit in next figure, for example. We create a **super-mesh** by excluding the current source and any elements connected in series with it.



## □ CASE 2

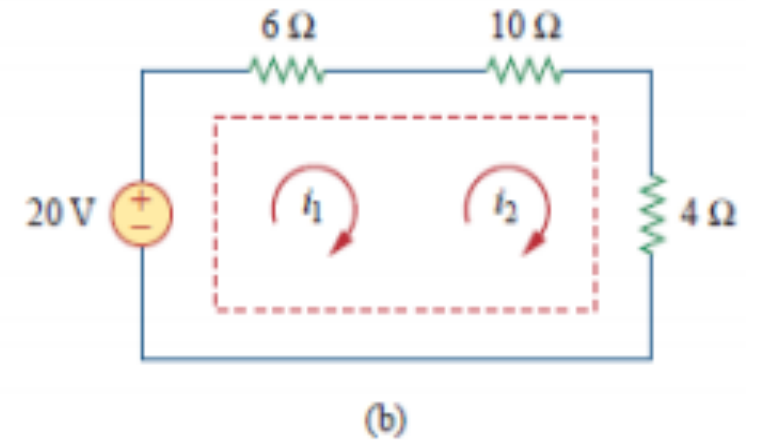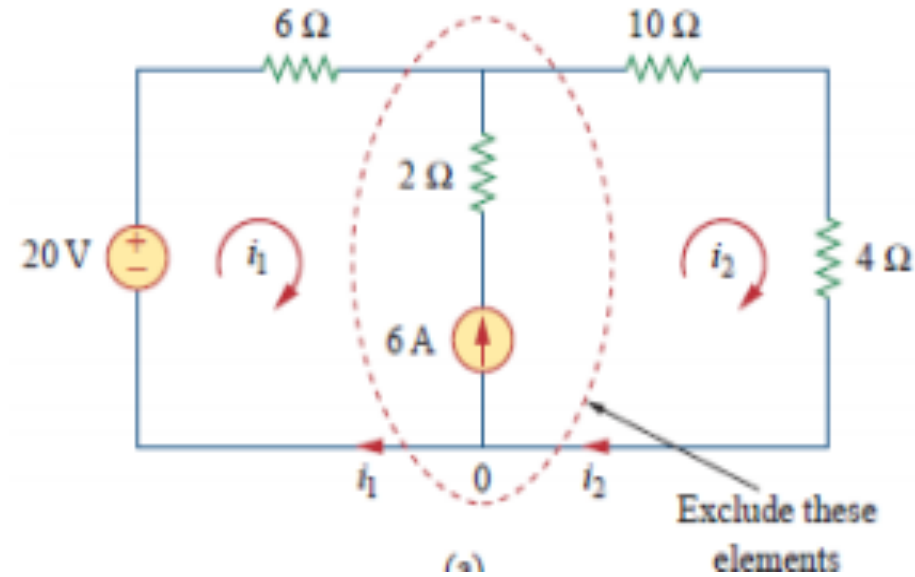

$$i_2 - i_1 = 6 \quad (1)$$

$$-20 + 6 i_1 + 10 i_2 + 4 i_2 = 0 \quad (2)$$

from (1) and (2)

$$i_1 = -3.2 \text{ A}, \quad i_2 = 2.8 \text{ A}$$

# Superposition Method


## □ Superposition

➤ The superposition principle states that the voltage across (or current through) an element in a linear circuit **is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.** With these in mind, **we apply the superposition principle in three steps:**

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.
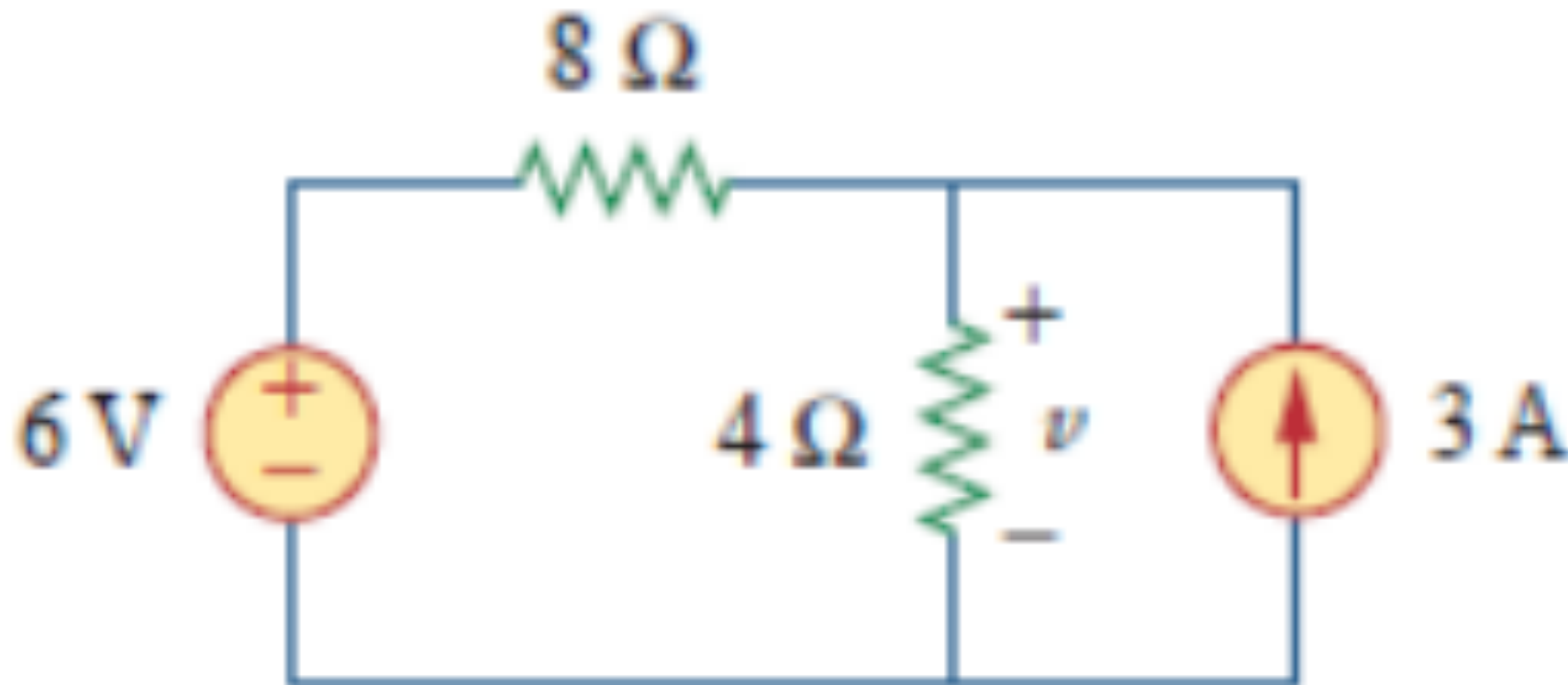
## □ Example5:


- Use the superposition theorem to find  $v$  in the circuit



## □ Example5:



(a)

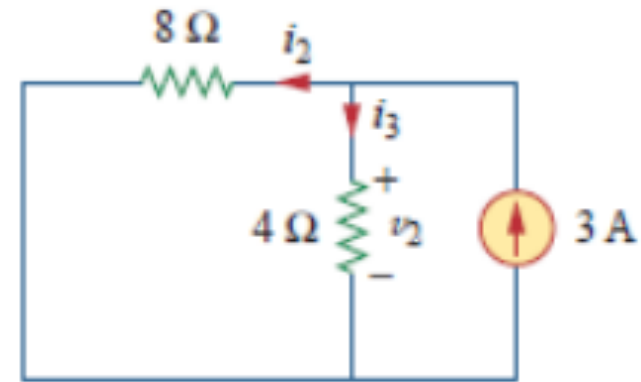

(b)

**Answer:**  $v = v_1 + v_2$

from figure a by voltage divider

$$v_1 = 4i_1 = \frac{4}{4 + 8} * 6 = 2V$$


from figure b by current divider

$$v_2 = 4i_3 = 4 * \frac{8}{4 + 8} * 3 = 8V$$

$$v = v_1 + v_2 = 2 + 8 = 10V$$
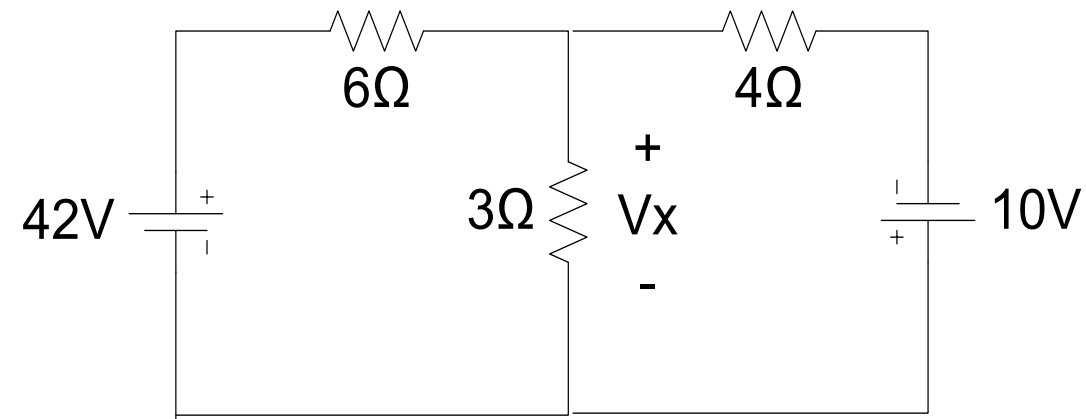
## □ Example 6


- Find voltage  $V_x$  using superposition theorem




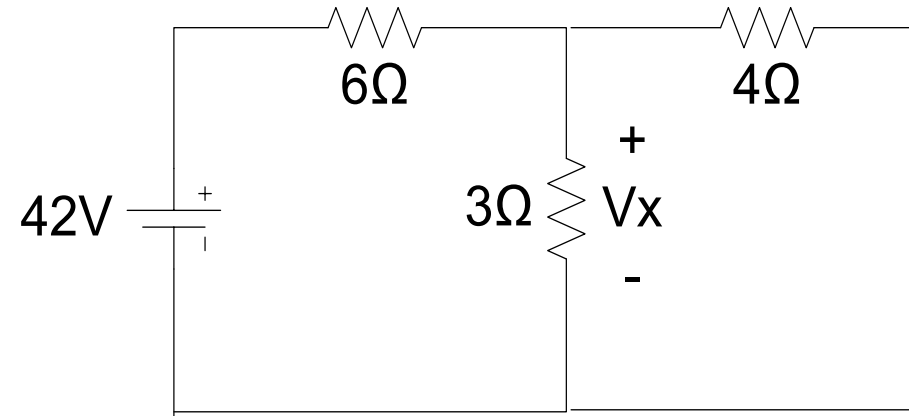
## □ Example 6

- Find voltage  $V_x$  using superposition theorem




*Considering 42V source only (10V source SC)*

$$V_{x(42V)} = \frac{(3 \parallel 4)}{6 + (3 \parallel 4)} \times 42 = \frac{(12/7)}{6 + (12/7)} \times 42$$
$$= 9.333V$$
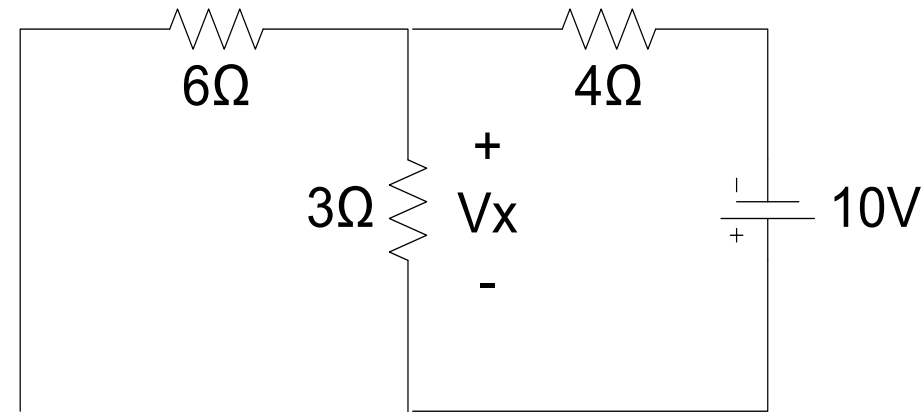
## □ Example 6

- Find voltage  $V_x$  using superposition theorem




*Only 10V source connected (42V source replaced by SC)*

$$V_{x(10V)} = -\frac{(6 \parallel 3)}{(6 \parallel 3) + 4} \times 10 = -\frac{2}{2 + 4} \times 10$$
$$= -3.333V$$
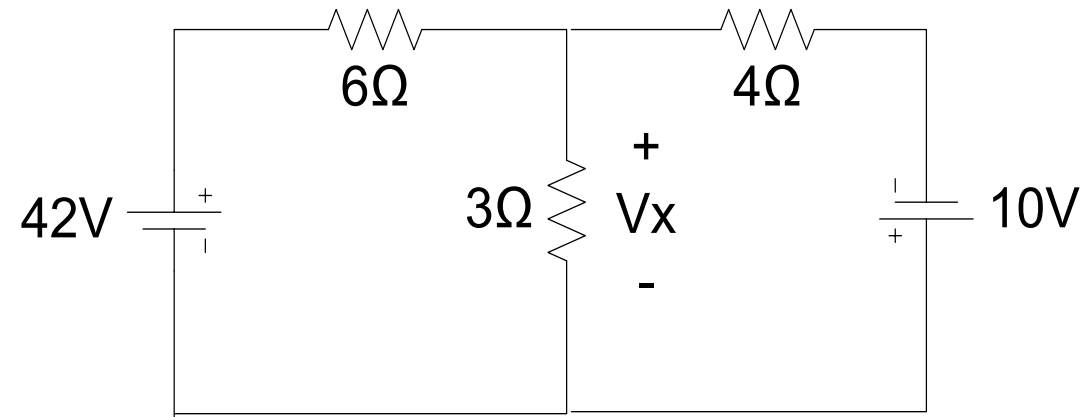
## □ Example 6

- Find voltage  $V_x$  using superposition theorem




*Total Voltage =*

$$V_x = V_{x(42V)} + V_{x(10V)}$$


$$= 9.333 - 3.333 = 6V$$

## □ Example 7

- Use superposition to find  $i_x$

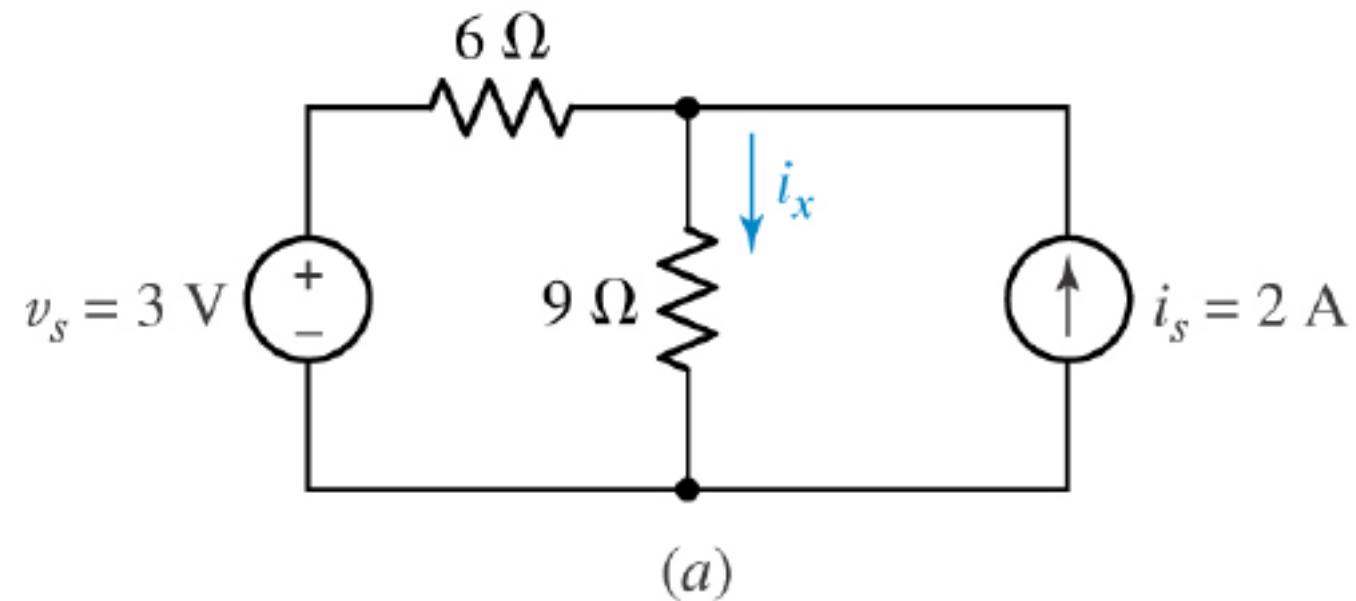

## □ Example 7

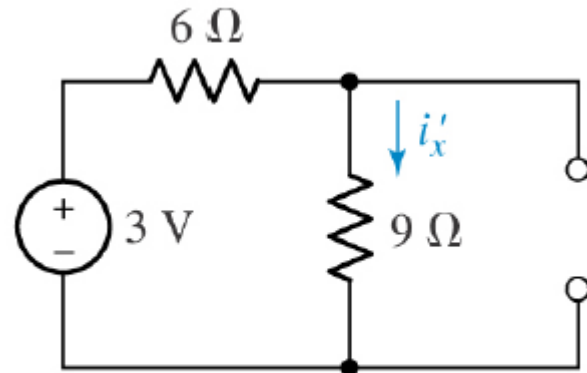


(b)

**Step 1:**

**Only 3V source connected (2A source is OC)**

$$i'_x = 3/15 = 0.2 \text{ A}$$

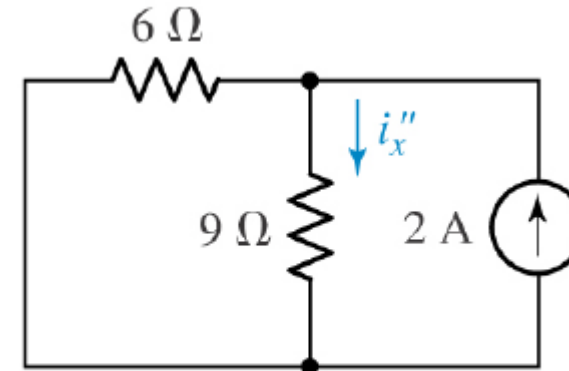

(c)

**Step 2:**

**Only 2A source connected (3V source is SC)**


$$i''_x = 2 \times 6 / (6 + 9) = 0.8 \text{ A}$$

**Step 3: Total current = 0.2 + 0.8 = 1A**

$$i_x = 1.0 \text{ A}$$
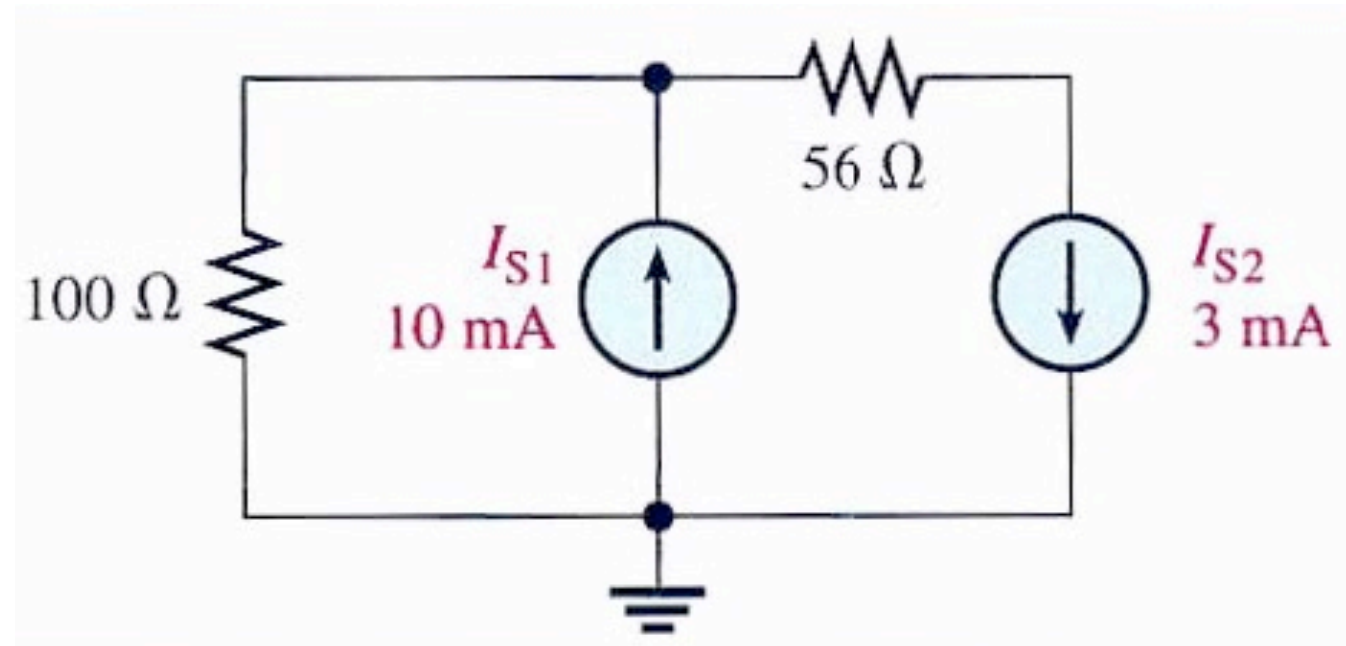
## □ Example 8

- Find the current through 100-ohm resistor





## □ Example 8

- Find the current through 100-ohm resistor

Step 1:

Only 10mA source connected in circuit(3mA source OC)

$I=10\text{mA}$

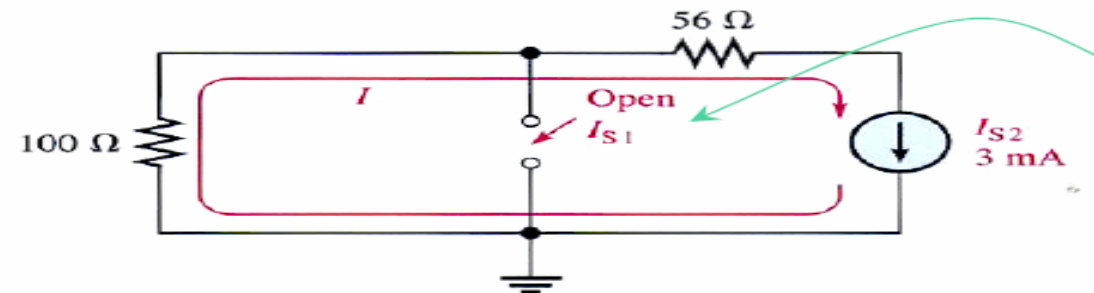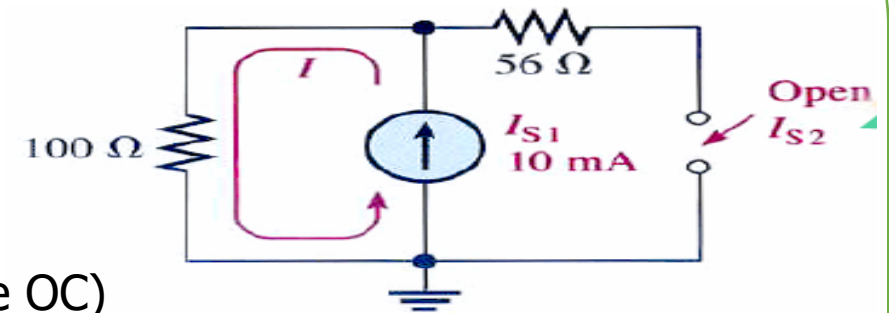

Step2: Only 3mA source connected(10mA source OC)

$I'=3\text{mA}$


Total Current:  $10\text{mA}-3\text{mA}=7\text{mA}$

# Thevenin's theorem


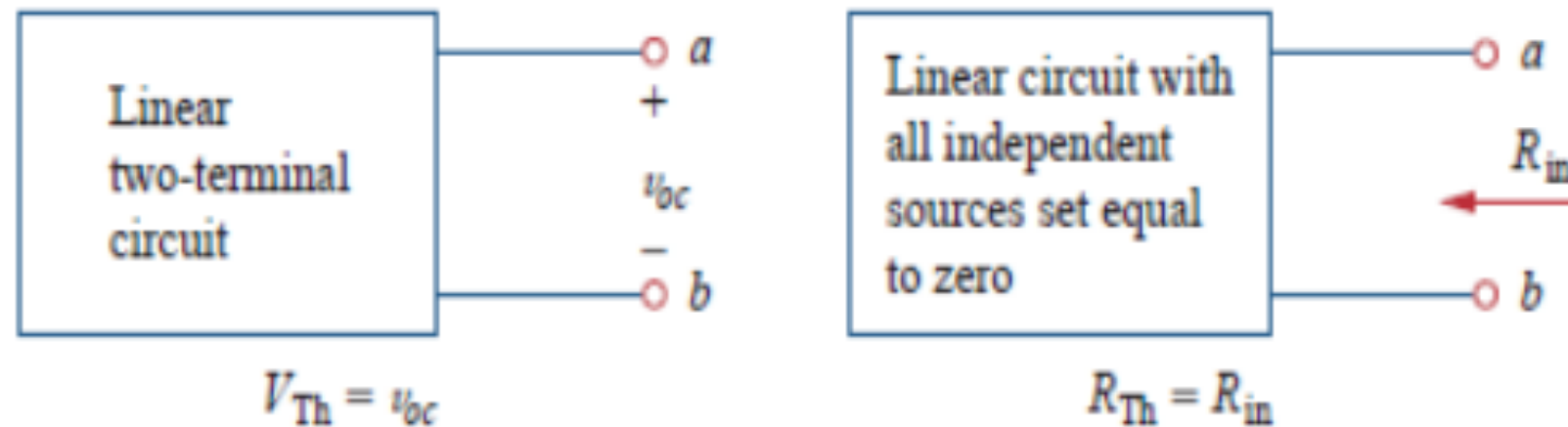
## □ Thevenin's theorem


- Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$ , where  $V_{Th}$  is the open-circuit voltage at the terminals and  $R_{Th}$  is the input or equivalent resistance at the terminals when the independent sources are turned off as shown in figure



# THEVENIN & NORTON

## THEVENIN'S THEOREM:

**Consider the following:**

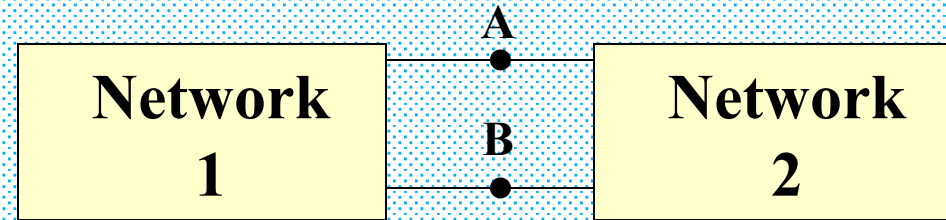


**Figure: Coupled networks.**

**For purposes of discussion, at this point, we consider that both networks are composed of resistors and independent voltage and current sources**

# THEVENIN & NORTON

## THEVENIN'S THEOREM:

**Suppose Network 2 is detached from Network 1 and we focus temporarily only on Network 1.**

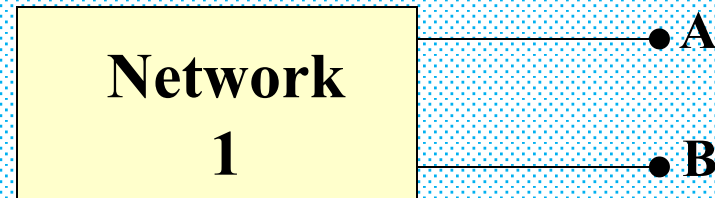


**Figure: Network 1, open-circuited.**

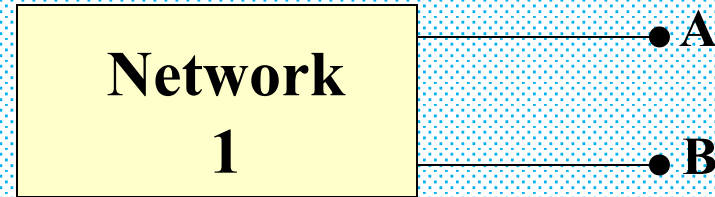**Network 1 can be as complicated in structure as one can imagine. Maybe 45 meshes, 387 resistors, 91 voltage sources and 39 current sources.**

# THEVENIN & NORTON

## THEVENIN'S THEOREM:



**Now place a voltmeter across terminals A-B and read the voltage. We call this the open-circuit voltage.**

**No matter how complicated Network 1 is, we read one voltage. It is either positive at A, (with respect to B) or negative at A.**

**We call this voltage  $V_{os}$  and we also call it  $V_{\text{THEVENIN}} = V_{\text{TH}}$**


# THEVENIN & NORTON

## THEVENIN'S THEOREM:

- We now deactivate all sources of Network 1.
- To deactivate a voltage source, we remove the source and replace it with a short circuit.
- To deactivate a current source, we remove the source.
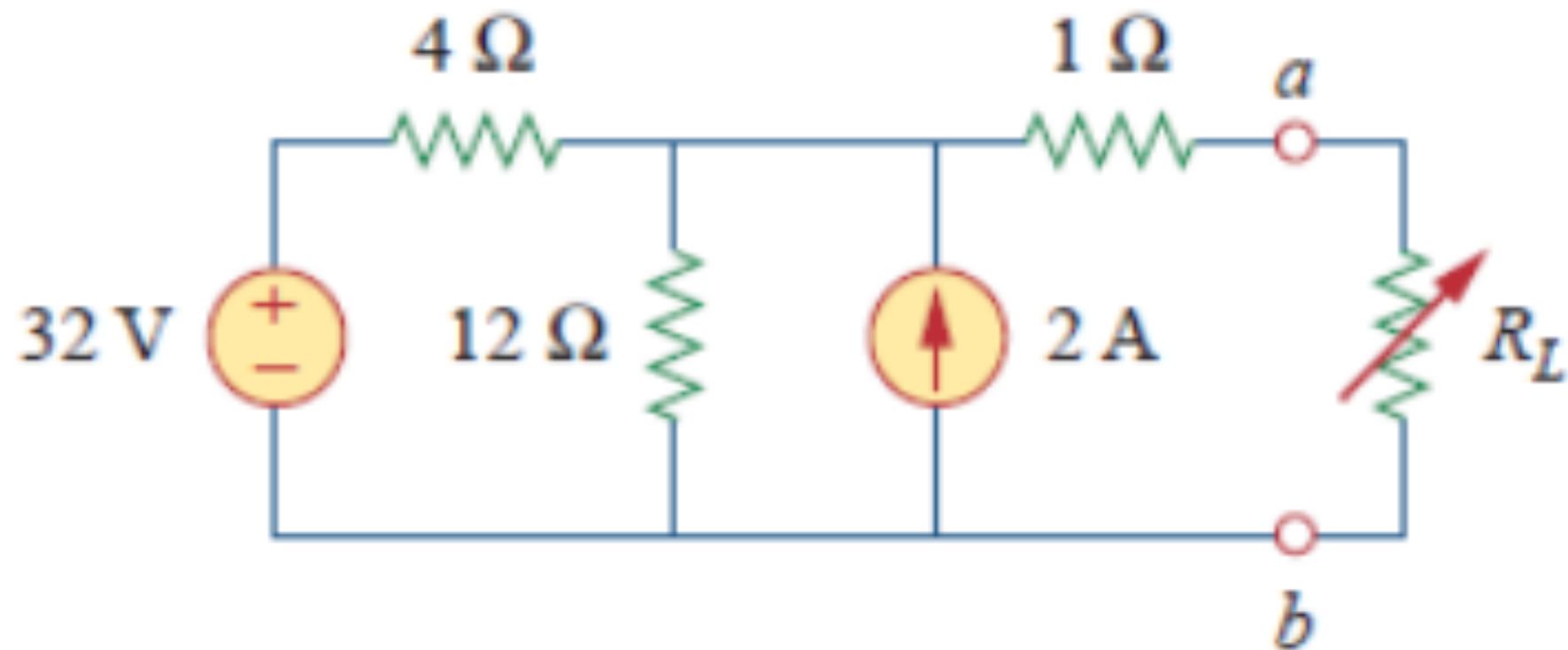
## □ Example 1

- Find the Thevenin equivalent circuit of the circuit shown, to the left of the terminals a - b.



## □ Example 1

- Find the Thevenin equivalent circuit of the circuit shown, to the left of the terminals a - b.

Answer:



$$R_{th} = (4//12) + 1 = 4\Omega$$

$$i_2 = -2A$$

$$-32 + 16i_1 - 12i_2 = 0$$

$$i_1 = 0.5A$$

$$V_{Th} = 12(i_1 - i_2) = 30V$$

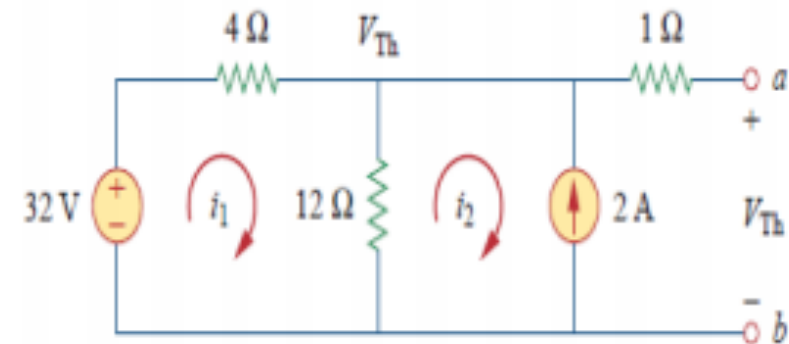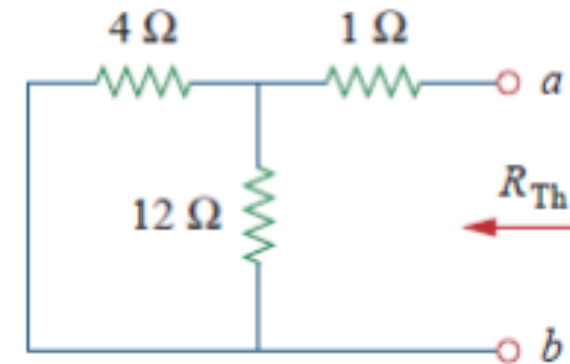

# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2.

Find  $V_X$  by first finding  $V_{TH}$  and  $R_{TH}$  to the left of A-B.

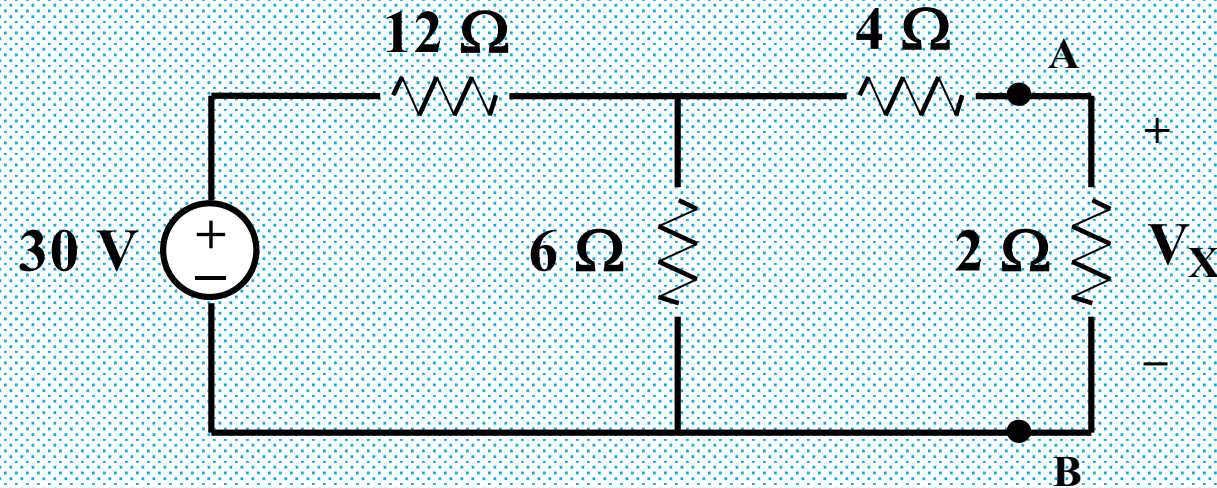


Figure: Circuit for Example 2.

First remove everything to the right of A-B.



# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2. continued

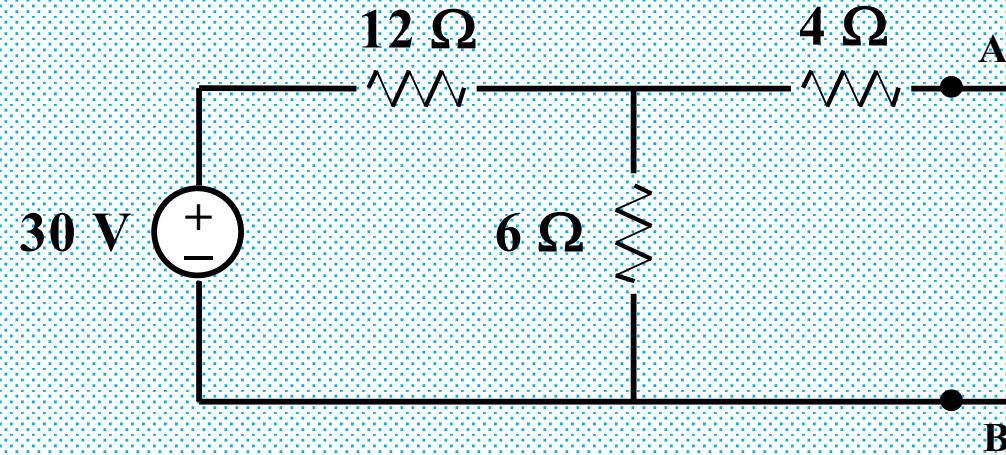


Figure: Circuit for finding  $V_{TH}$  for Example 2.

$$V_{AB} = \frac{(30)(6)}{6+12} = 10V$$

Notice that there is no current flowing in the 4 Ω resistor (A-B) is open. Thus, there can be no voltage across the resistor.

# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2. continued

We now deactivate the sources to the left of A-B and find the resistance seen looking in these terminals.

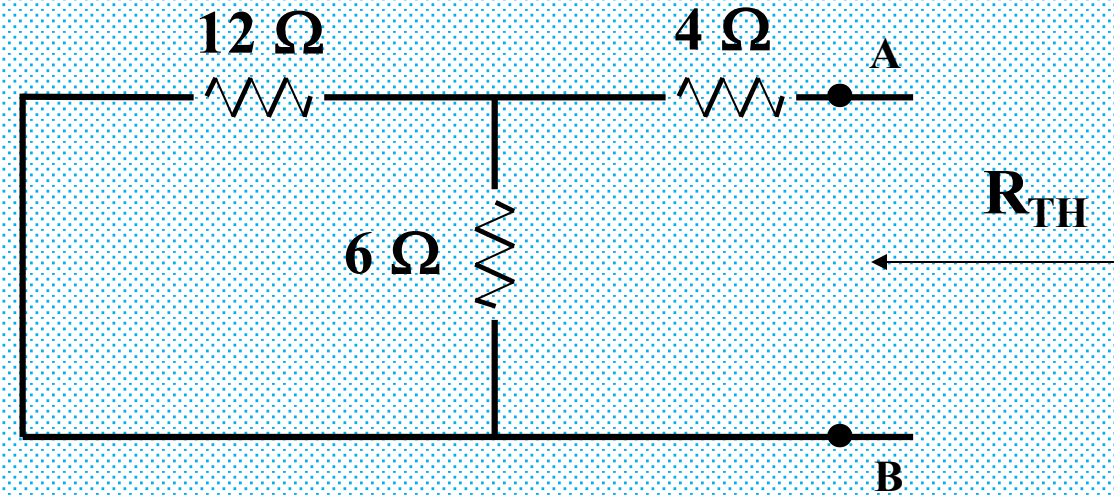


Figure: Circuit for find  $R_{TH}$  for Example 2.

We see,

$$R_{TH} = 12 || 6 + 4 = 8 \Omega$$

# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2. continued

After having found the Thevenin circuit, we connect this to the load in order to find  $V_X$ .

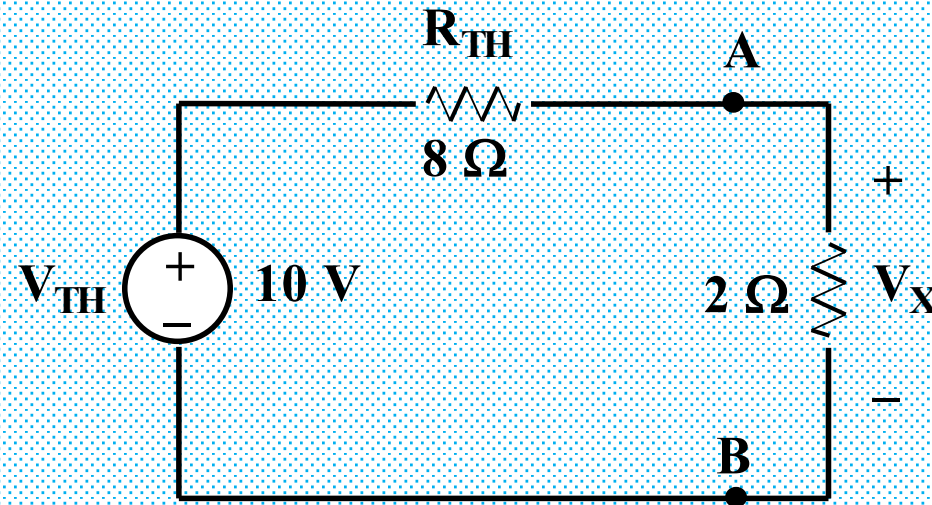


Figure: Circuit of Ex 2 after connecting Thevenin circuit.

$$V_X = \frac{(10)(2)}{2+8} = 2V$$

# Norton theorem


## □ Norton theorem


- Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_N = V_{Th}/R_{Th}$  in parallel with a resistor  $R_N = R_{Th}$ , where  $I_N$  is the short-circuit current through the terminals and  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.


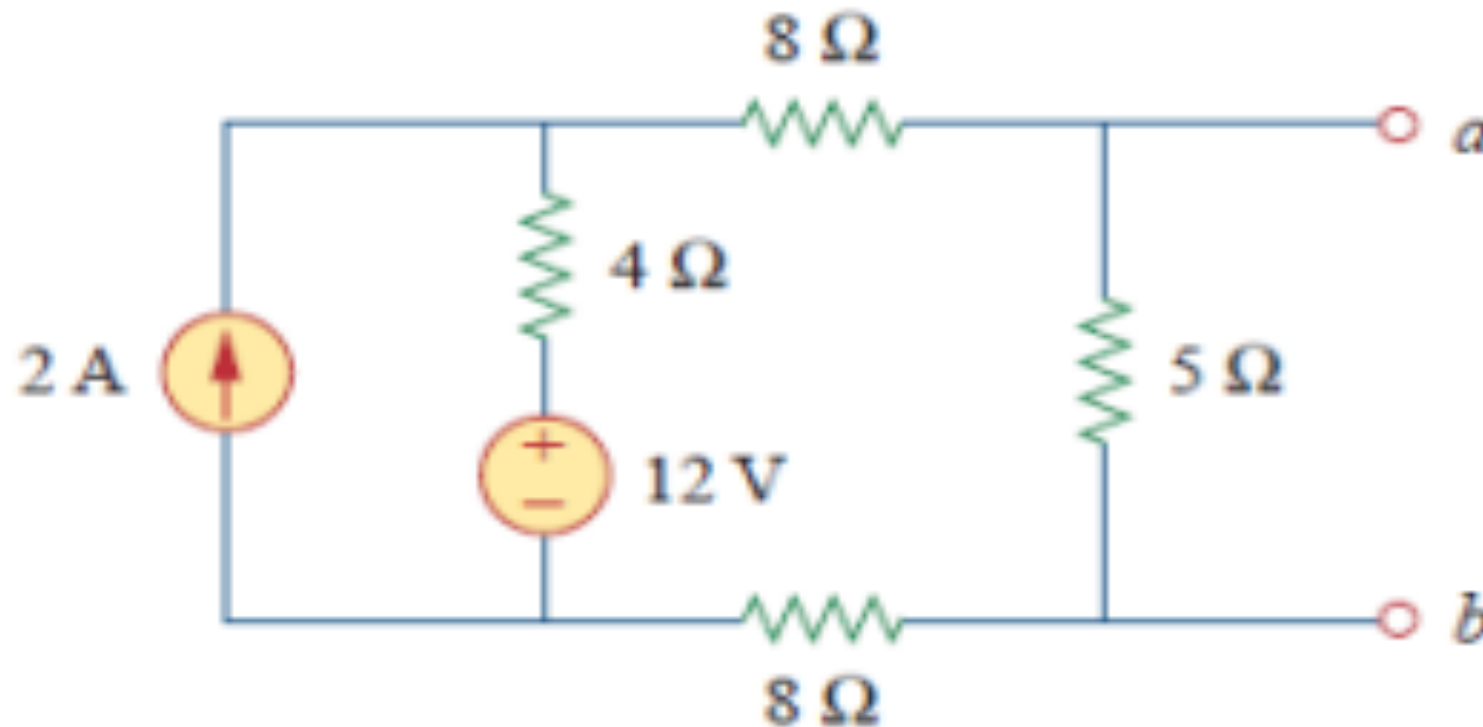
## □ Example

- Find the Norton equivalent circuit of the circuit shown, to the left of the terminals a - b.



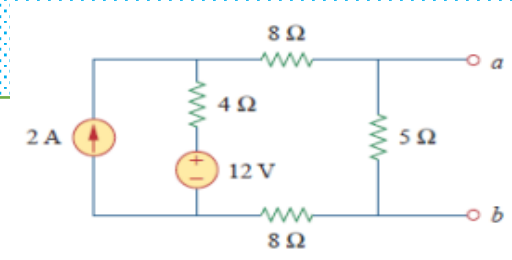


## Example


- Find the Norton equivalent circuit of the circuit shown, to the left of the terminals a - b.

Answer:

$$R_N = 5 // (8 + 4 + 8) = 4\Omega$$

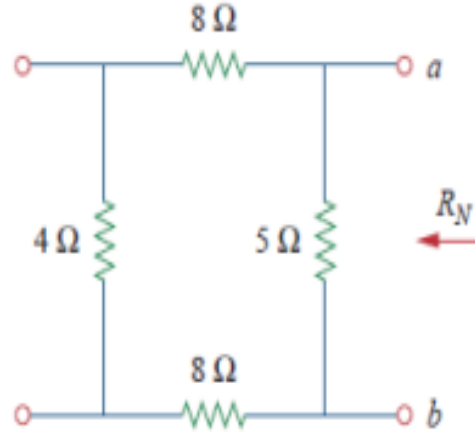
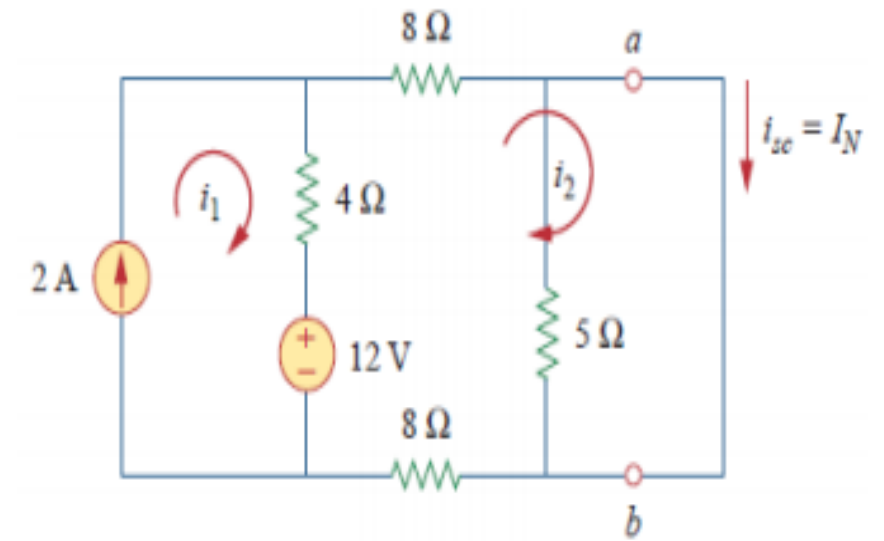
$$\begin{aligned}
 i_1 &= 2A \\
 20i_2 - 4i_1 - 12 &= 0 \\
 i_2 &= 1A = i_{sc} \\
 &= I_N
 \end{aligned}$$



*Thank  
you*

