




# Electronics 1

BSC 113

Fall 2022-2023

Lecture 6

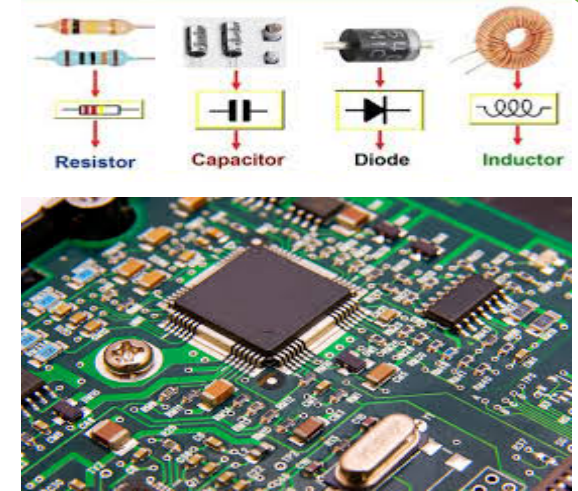

# Thevenin's & Norton theorems & Maximum Power Transfer and Source Transformation

**INSTRUCTOR**

DR / AYMAN SOLIMAN


## ➤ Contents

- 1) Thevenin's theorem
- 2) Norton theorem
- 3) Maximum Power Transfer
- 4) Source Transformation


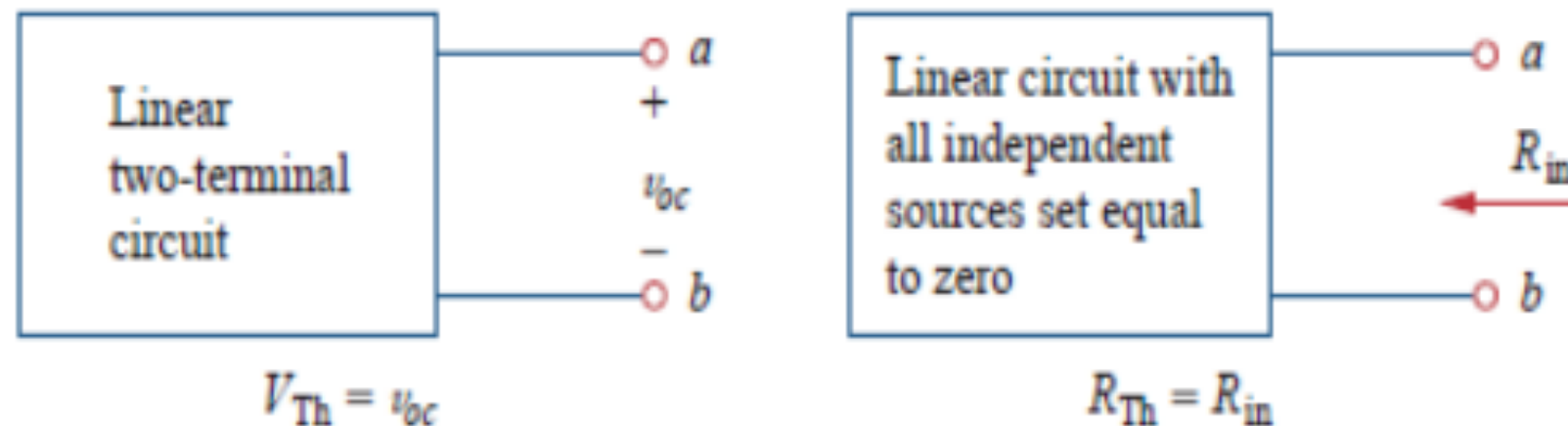
## □ Thevenin's theorem

- Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$ , where  $V_{Th}$  is the **open-circuit voltage at the terminals** and  $R_{Th}$  is the **input or equivalent resistance at the terminals** when the independent sources are turned off as shown in figure



# THEVENIN

## THEVENIN'S THEOREM:

Consider the following:

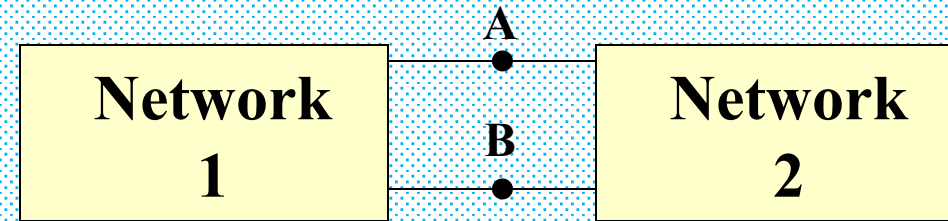


Figure: Coupled networks.

For purposes of discussion, at this point, we consider that both networks are composed of resistors and independent voltage and current sources

# THEVENIN

## THEVENIN'S THEOREM:

Suppose Network 2 is detached from Network 1 and we focus temporarily only on Network 1.


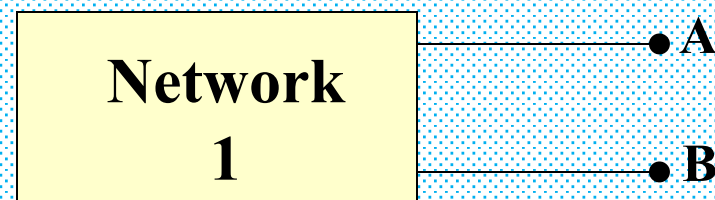


Figure: Network 1, open-circuited.

- Network 1 can be as complicated in structure as one can imagine.
  - ✓ Maybe 45 meshes
  - ✓ 387 resistors
  - ✓ 91 voltage sources
  - ✓ 39 current sources.

# THEVENIN

## THEVENIN'S THEOREM:

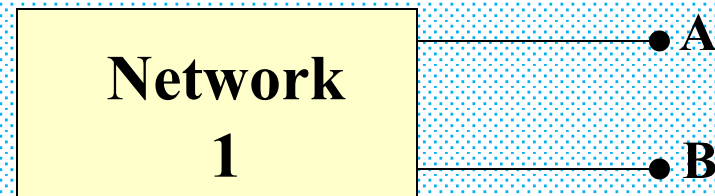

**Now place a voltmeter across terminals A-B and read the voltage. We call this the open-circuit voltage.**

**No matter how complicated Network 1 is, we read one voltage. It is either positive at A, (with respect to B) or negative at A.**



**We call this voltage  $V_{os}$  and we also call it  $V_{THEVENIN} = V_{TH}$**

# THEVENIN

## THEVENIN'S THEOREM:


- We now deactivate all sources of Network 1.
- To deactivate a voltage source, we remove the source and replace it with a short circuit.
- To deactivate a current source, we remove the source.

To set sources to zero

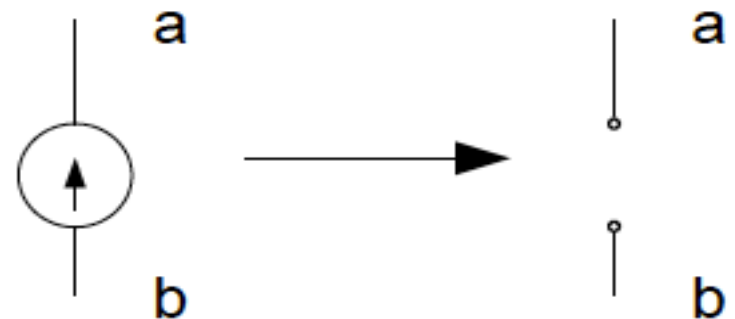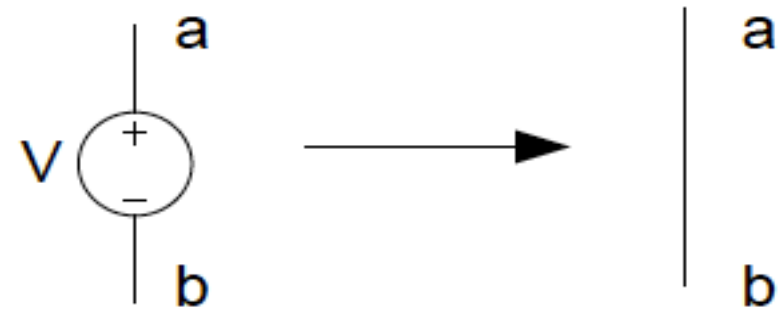
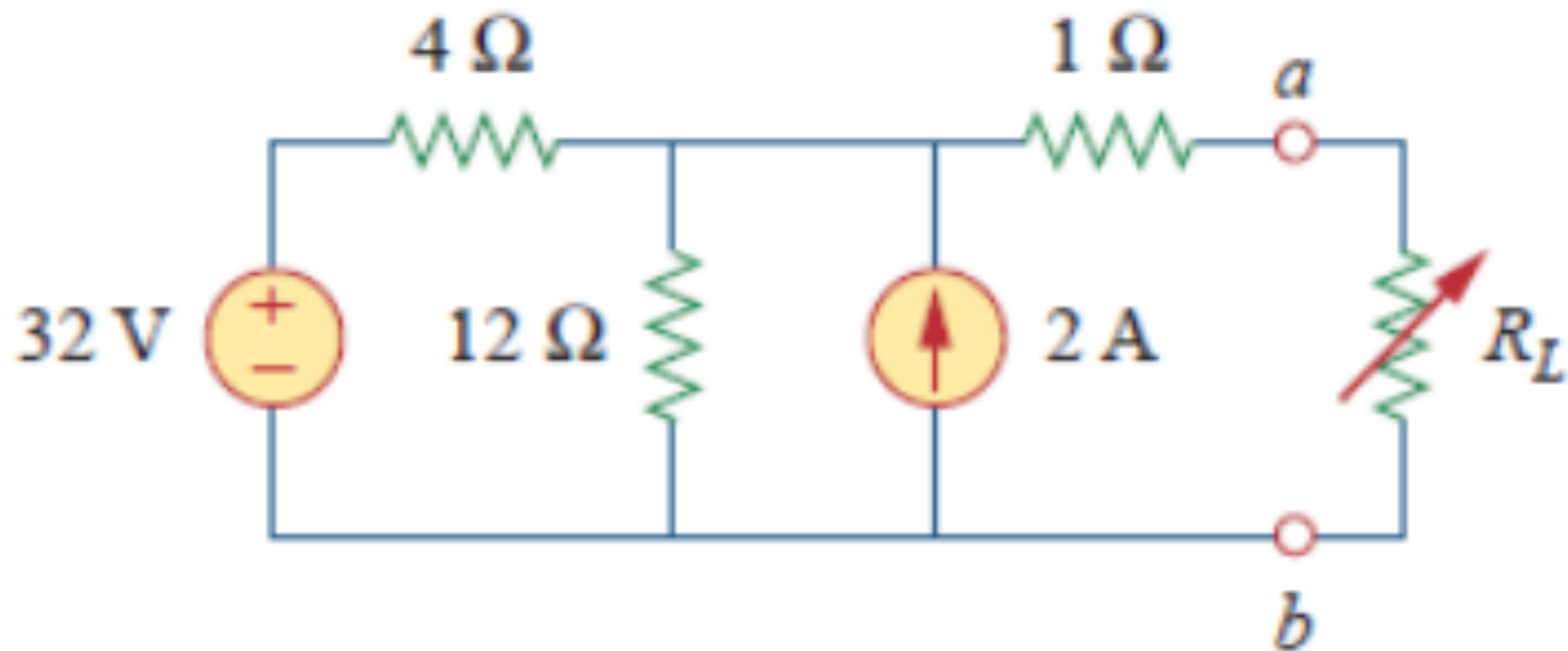
## □ Example 1

- Find the Thevenin equivalent circuit of the circuit shown, to the left of the terminals a - b.





## □ Example 1

- Find the Thevenin equivalent circuit of the circuit shown, to the left of the terminals a - b.

Answer:



$$R_{th} = (4//12) + 1 = 4\Omega$$

$$i_2 = -2A$$

$$-32 + 16i_1 - 12i_2 = 0$$

$$i_1 = 0.5A$$

$$V_{Th} = 12(i_1 - i_2) = 30V$$

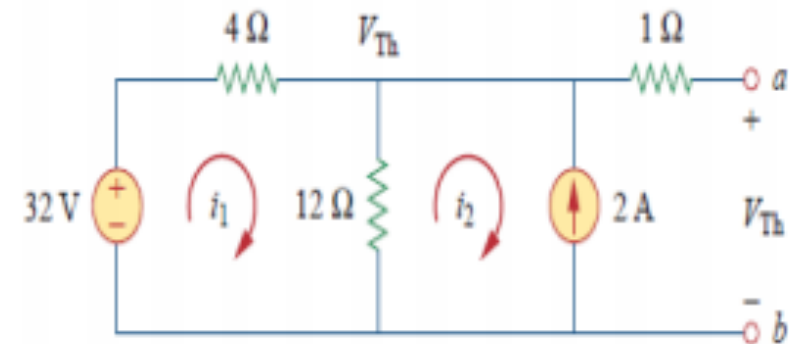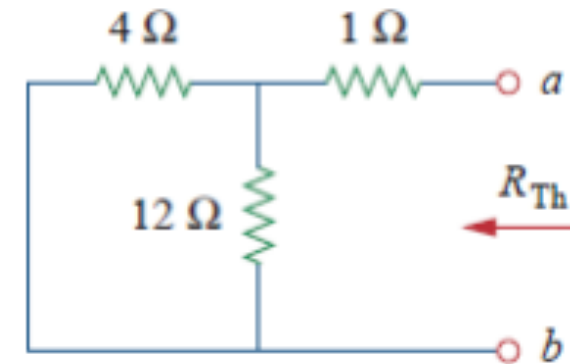

# THEVENIN

## THEVENIN'S THEOREM: Example 2.

Find  $V_X$  by first finding  $V_{TH}$  and  $R_{TH}$  to the left of A-B.

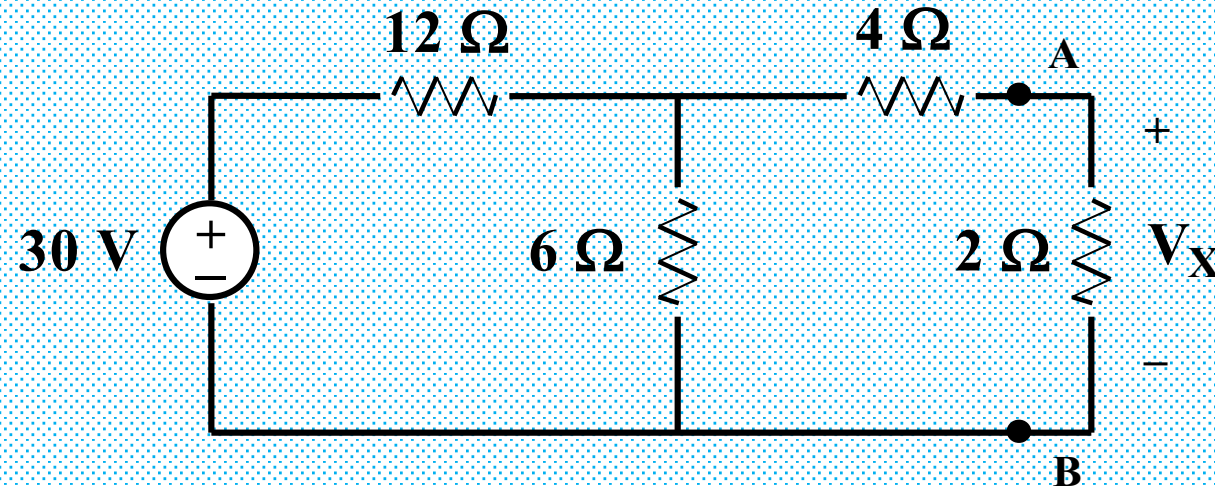


Figure: Circuit for Example 2.

First remove everything to the right of A-B.

# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2. continued

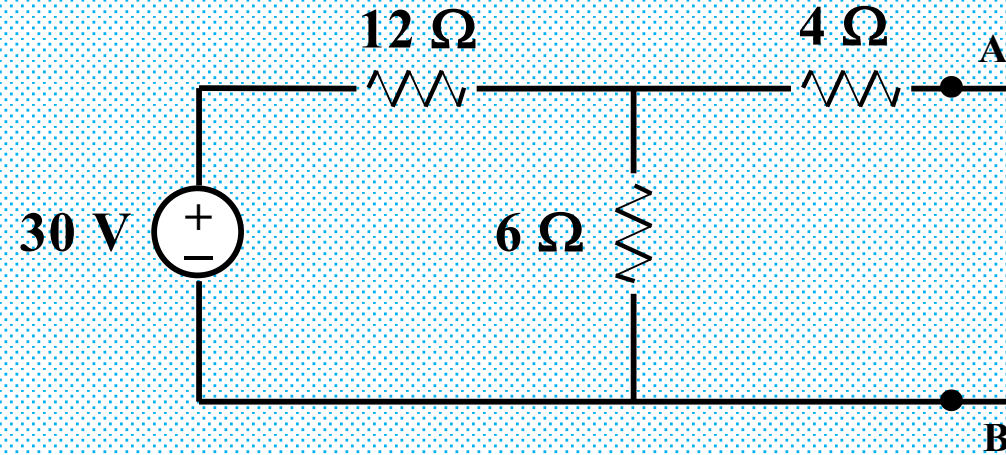


Figure: Circuit for finding  $V_{TH}$  for Example 2.

$$V_{AB} = \frac{(30)(6)}{6+12} = 10V$$

Notice that there is no current flowing in the 4 Ω resistor (A-B) is open. Thus, there can be no voltage across the resistor.

# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2. continued

We now deactivate the sources to the left of A-B and find the resistance seen looking in these terminals.

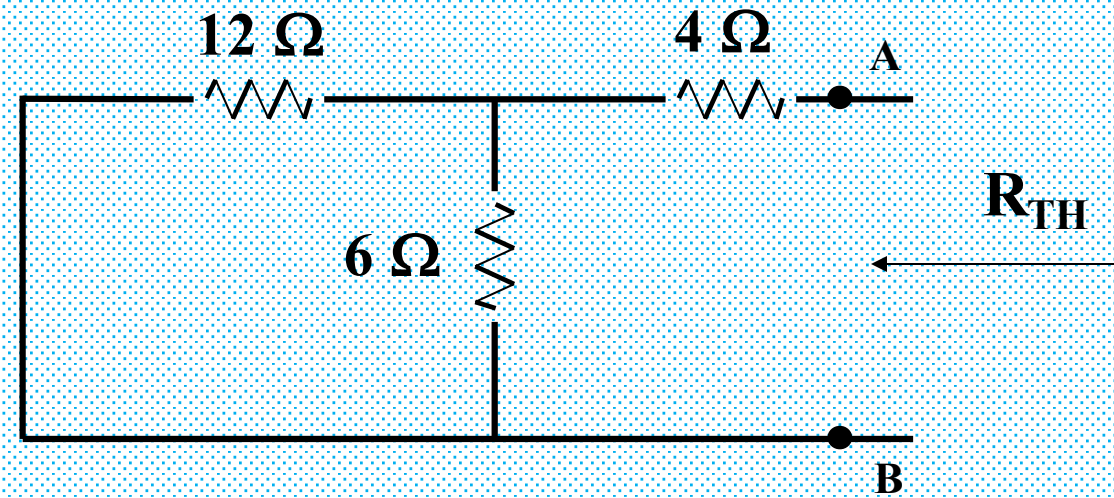


Figure: Circuit for find  $R_{TH}$  for Example 2.

We see,

$$R_{TH} = 12 || 6 + 4 = 8 \Omega$$

# THEVENIN & NORTON

## THEVENIN'S THEOREM: Example 2. continued

After having found the Thevenin circuit, we connect this to the load in order to find  $V_X$ .

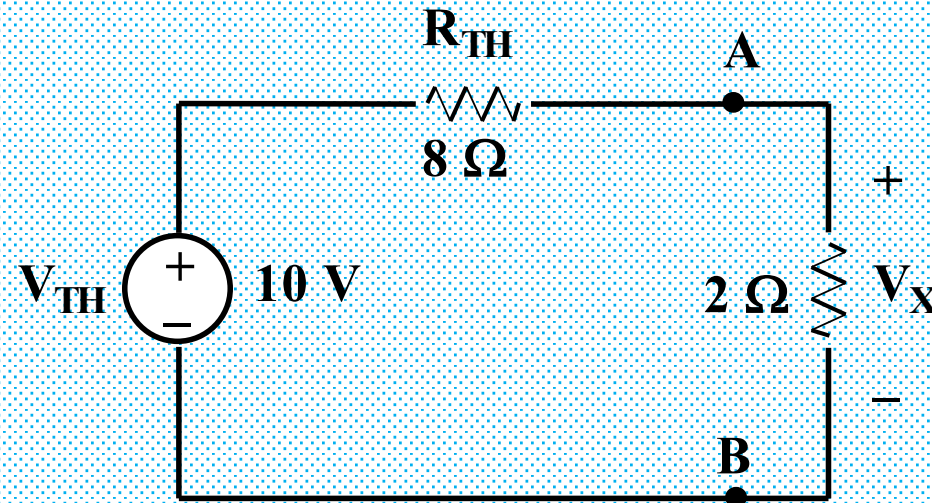


Figure: Circuit of Ex 2 after connecting Thevenin circuit.

$$V_X = \frac{(10)(2)}{2+8} = 2V$$

# Norton theorem


## □ Norton theorem

- Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_N = V_{Th}/R_{Th}$  in parallel with a resistor  $R_N = R_{Th}$ , where  $I_N$  is the **short-circuit current through the terminals** and  $R_N$  is the **input or equivalent resistance at the terminals when the independent sources are turned off**.



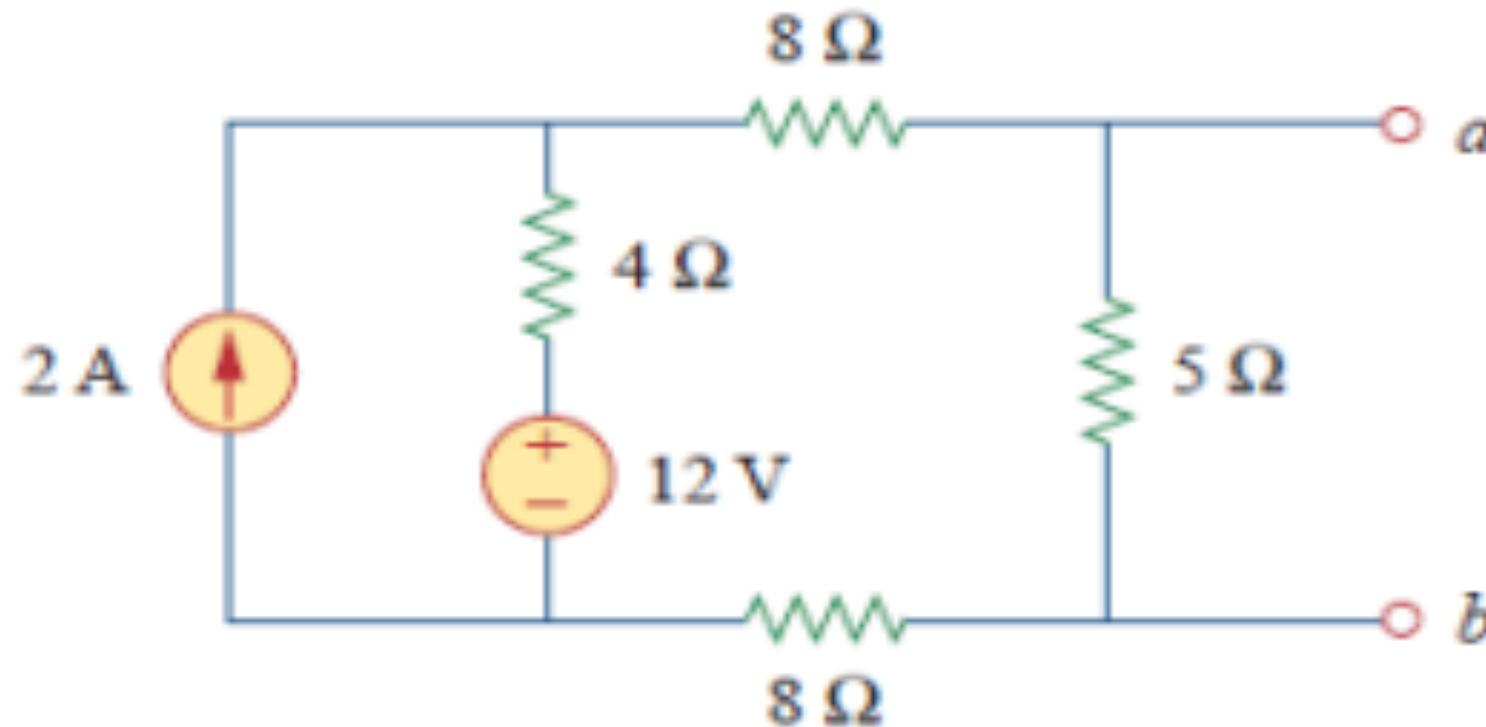
## □ Example

- Find the Norton equivalent circuit of the circuit shown, to the left of the terminals a - b.





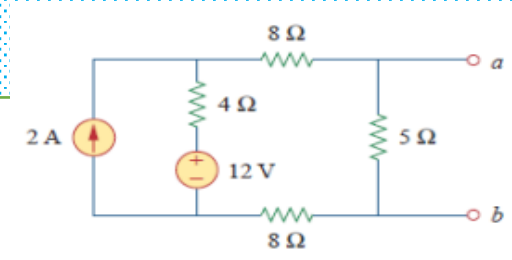


## Example

- Find the Norton equivalent circuit of the circuit shown, to the left of the terminals a - b.

Answer:


$$R_N = 5 // (8 + 4 + 8) = 4\Omega$$

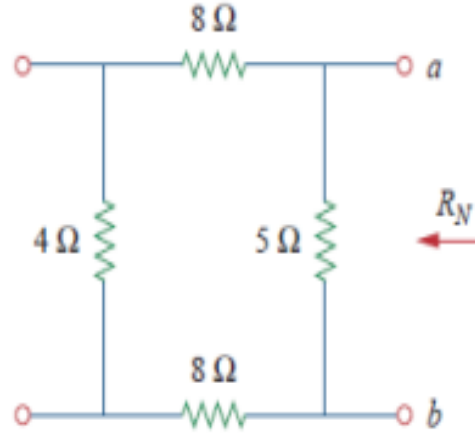

$$i_1 = 2A$$


$$20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1A = i_{sc} = I_N$$

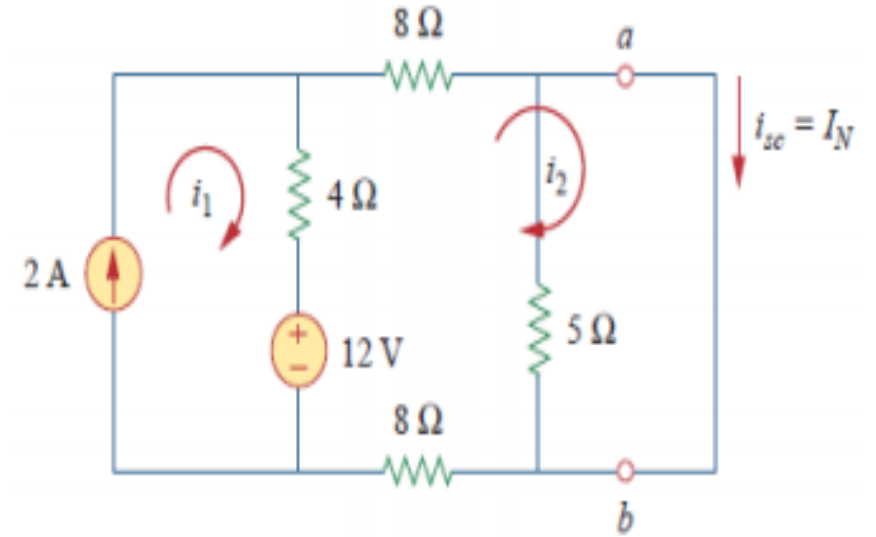


# Maximum Power Transfer

## □ Maximum Power Transfer

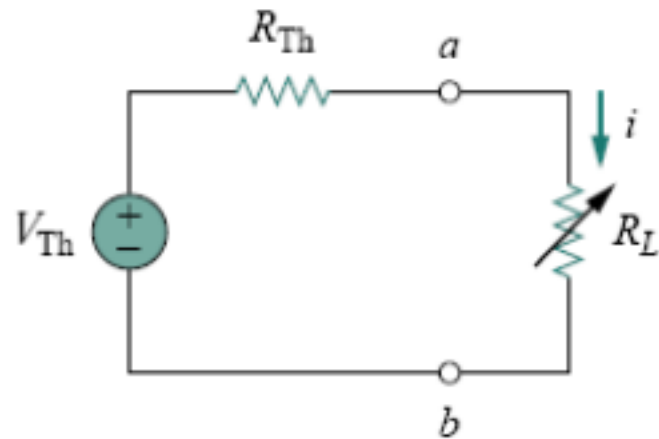
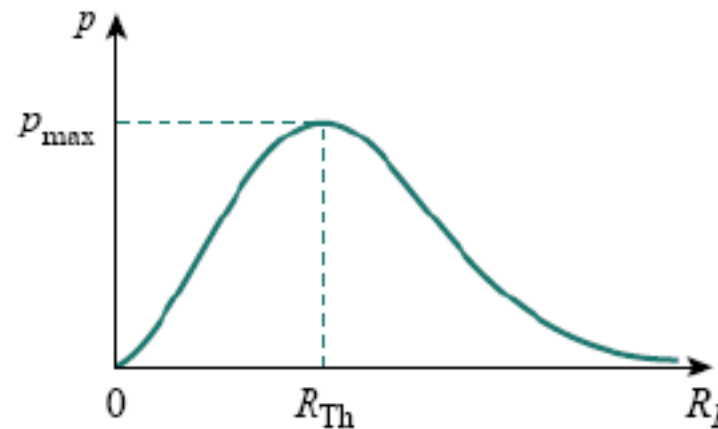
$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$



## □ Maximum Power Transfer

$$\begin{aligned}\frac{dp}{dR_L} &= V_{Th}^2 \left[ \frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] \\ &= V_{Th}^2 \left[ \frac{(R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} \right] = 0\end{aligned}$$

$$0 = (R_{Th} + R_L - 2R_L) = (R_{Th} - R_L)$$


$$R_L = R_{Th}$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

Maximum power is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ( $R_L = R_{Th}$ ).



applies only when  $R_L = R_{Th}$ .

## □ Example

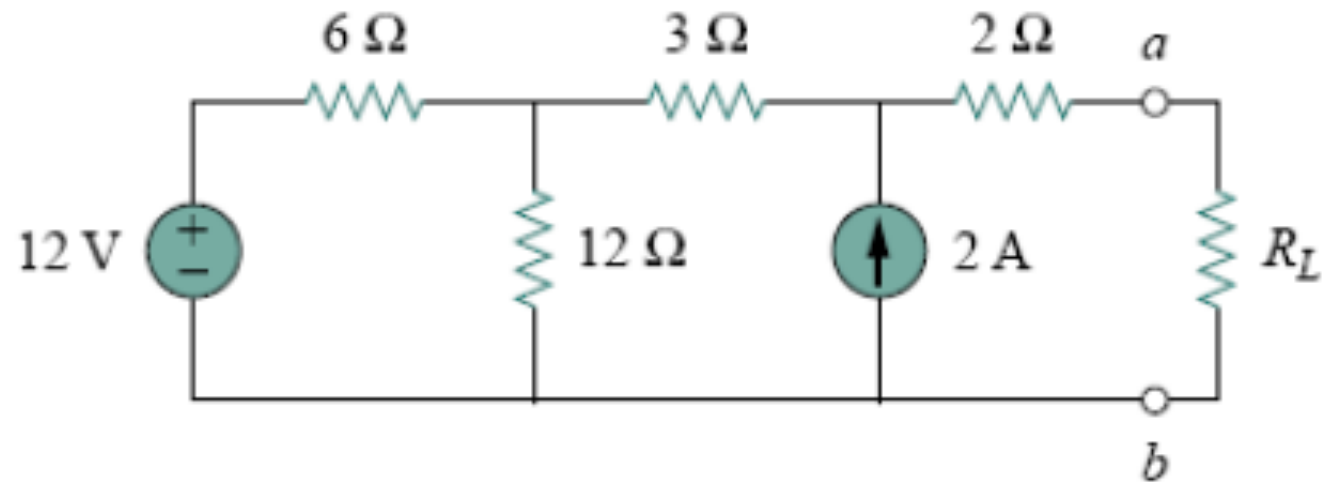


Find the value of  $R_L$  for maximum power transfer in the circuit of Fig.  
Find the maximum power.

## □ Example

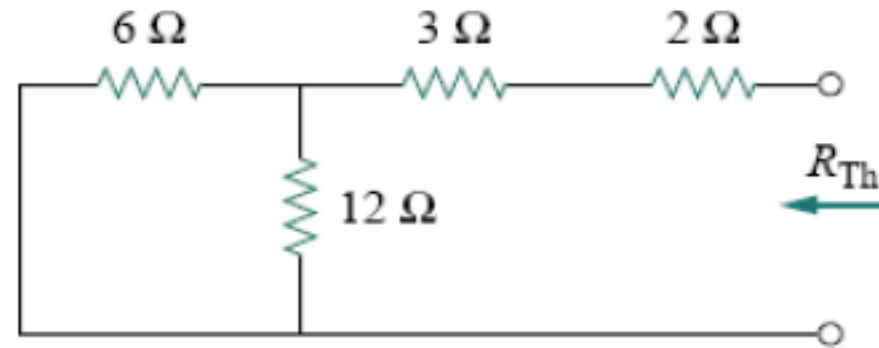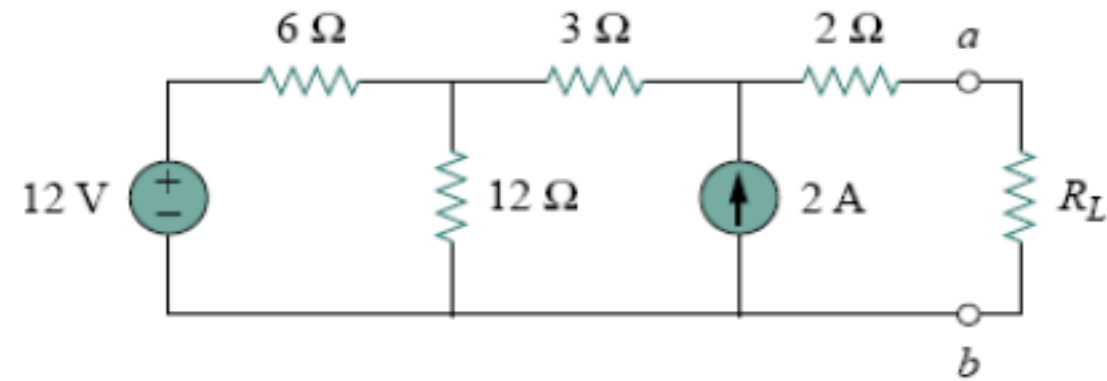

$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$

## □ Example

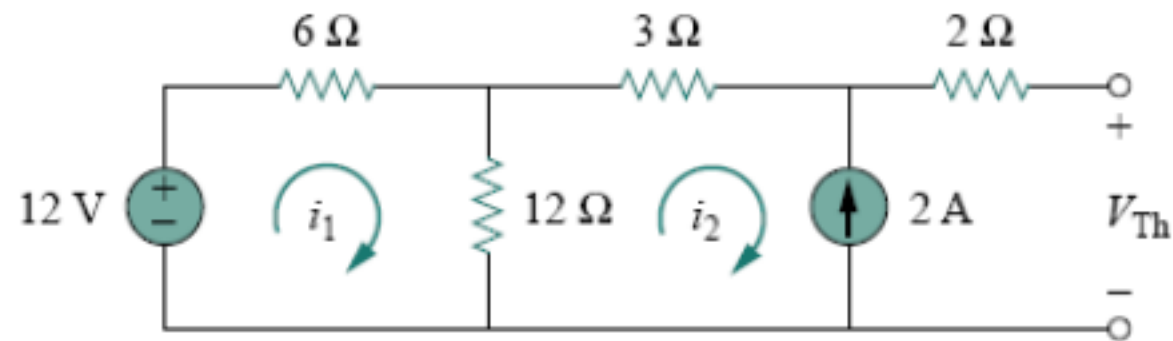

$$-12 + 18i_1 - 12i_2 = 0, \quad i_2 = -2 \text{ A}$$

$$i_1 = -2/3$$

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0$$

$$V_{Th} = 22 \text{ V}$$

## □ Example

For maximum power transfer,

$$R_L = R_{Th} = 9 \Omega$$


and the maximum power is

$$P_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$



# Source Transformation


## □ Source Transformation

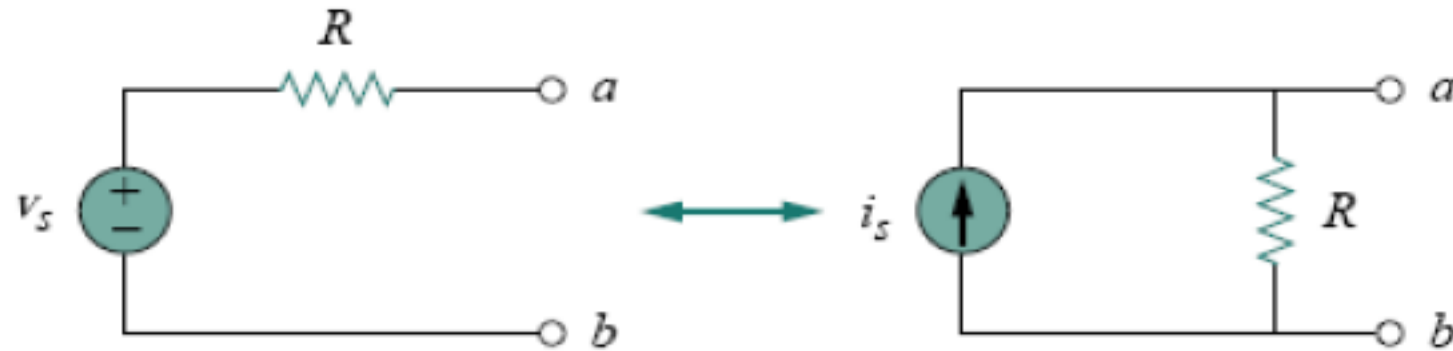

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$



A **source transformation** is the process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.

## □ Example



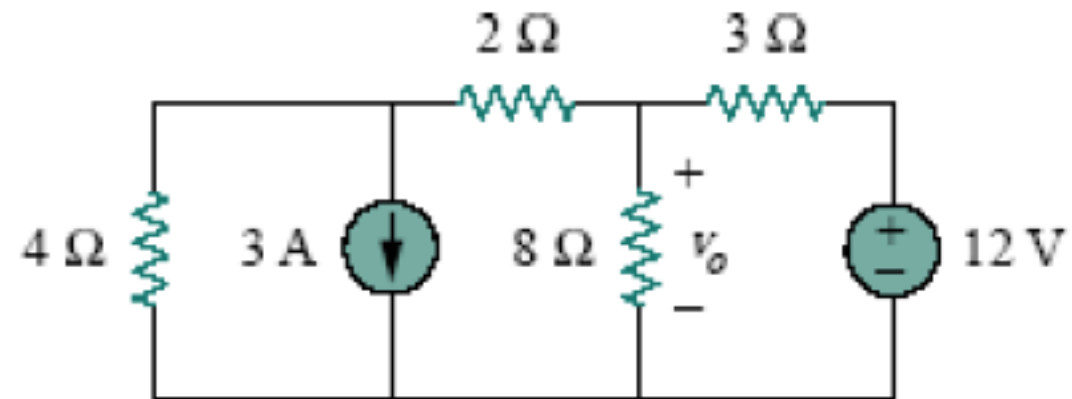


Use source transformation to find  $v_o$  in the circuit in Fig.

## □ Example

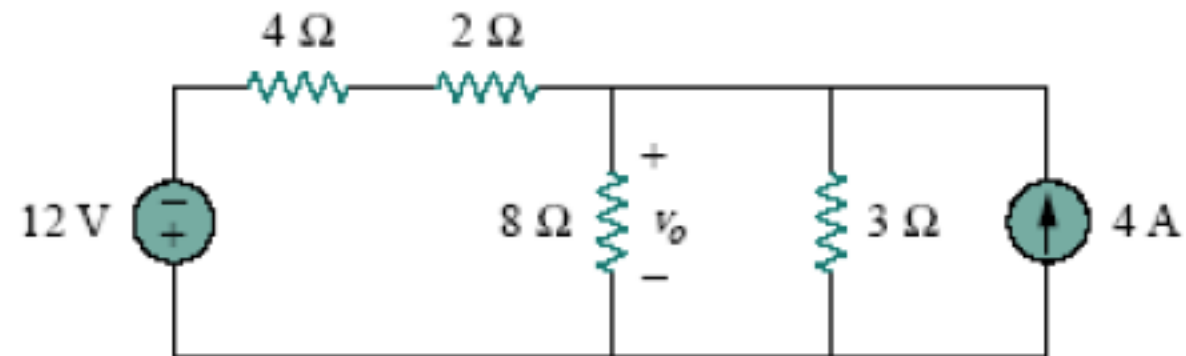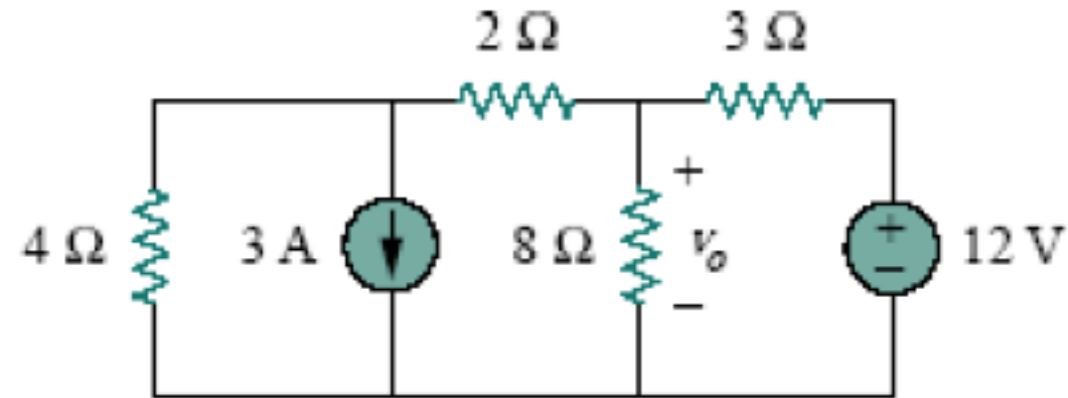

## □ Example

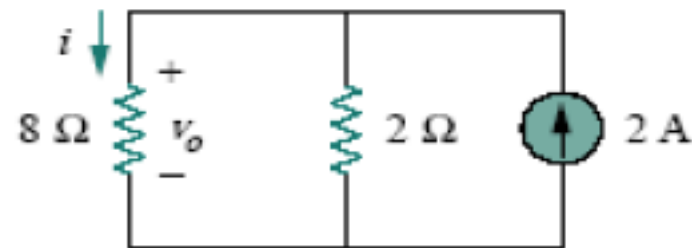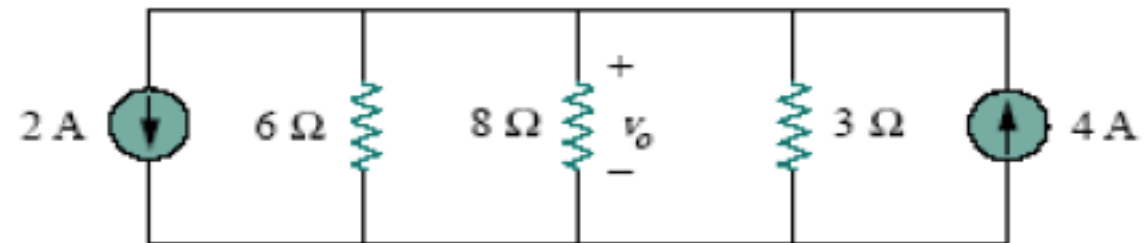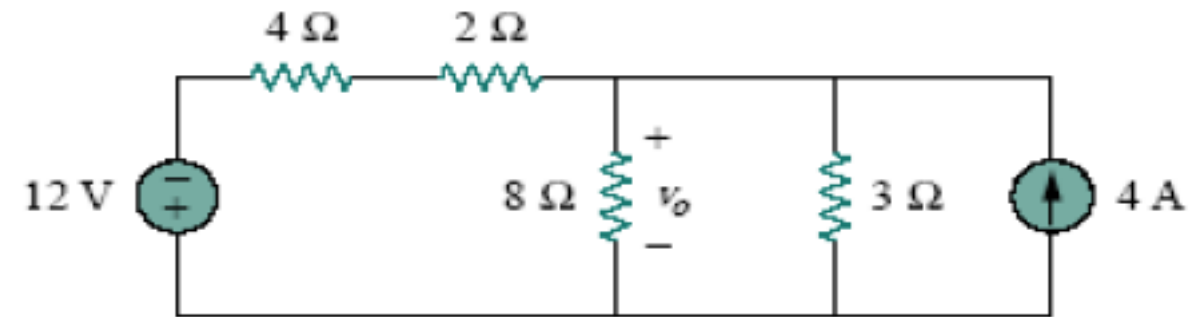

$$i = \frac{2}{2 + 8}(2) = 0.4$$

$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$

*Thank  
you*

