




Electronics 1

BSC 113

Fall 2022-2023

Lecture 7

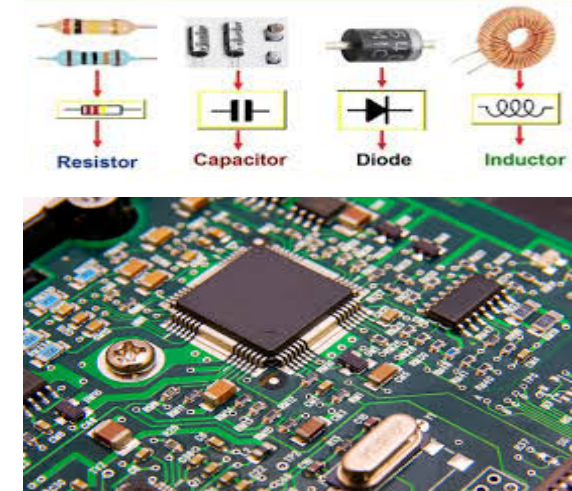

Delta-to-Wye (Pi-to-Tee) Equivalent Circuits Inductor & Capacitor

INSTRUCTOR



DR / AYMAN SOLIMAN

➤ Contents

- 1) Delta-to-Wye Equivalent Circuits
- 2) The Delta-to-Y transformation
- 3) Delta-to-Y Equations
- 4) Y-to-Delta Equations
- 5) Example
- 6) Inductor
- 7) Capacitor
- 8) Revision





Delta-to-Wye Equivalent Circuits

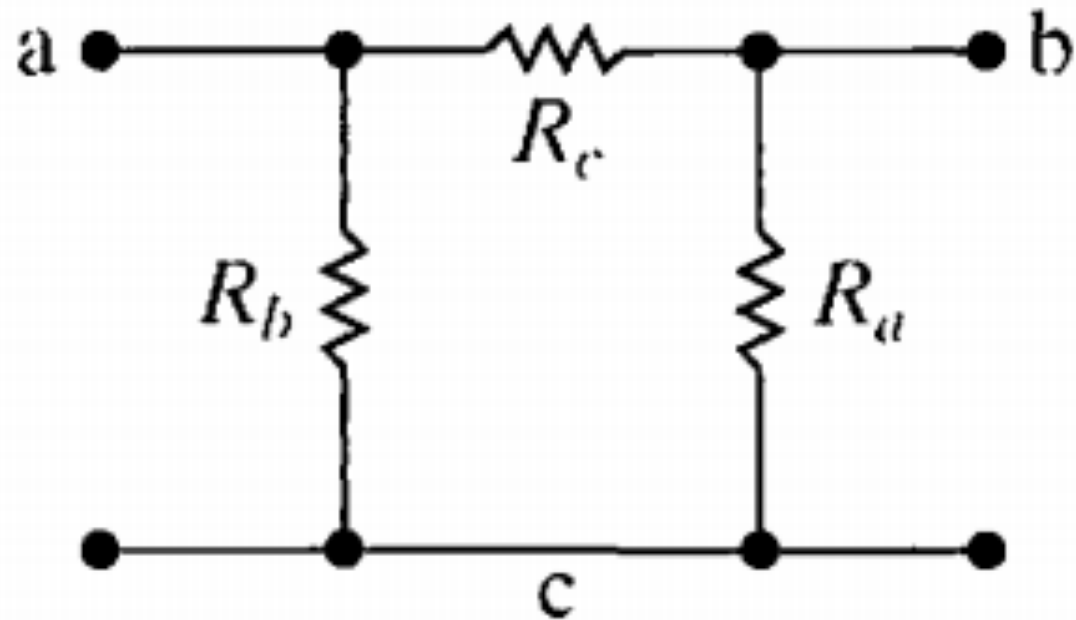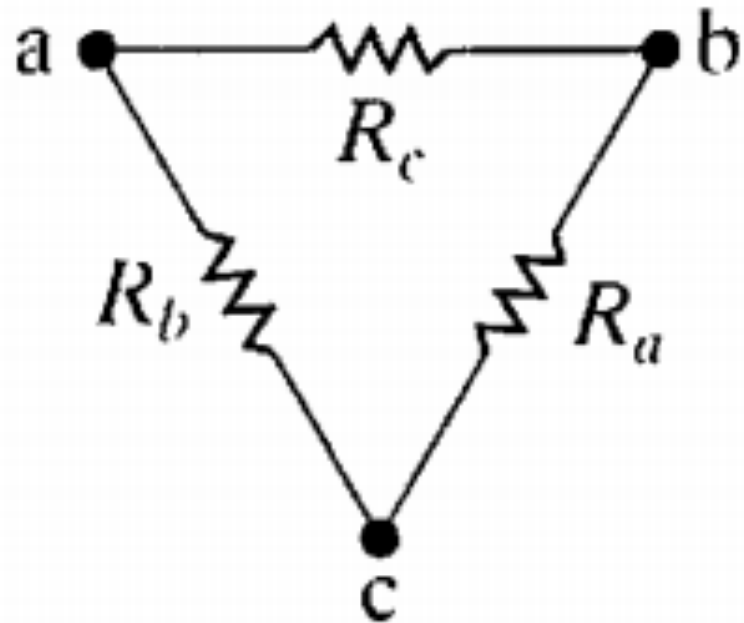


▲ A Δ configuration viewed as a π configuration.

Delta-to-Wye Equivalent Circuits

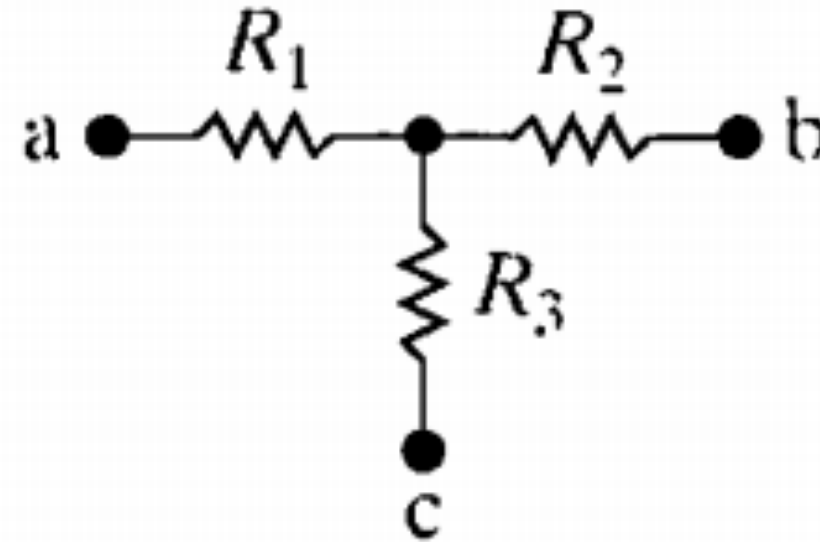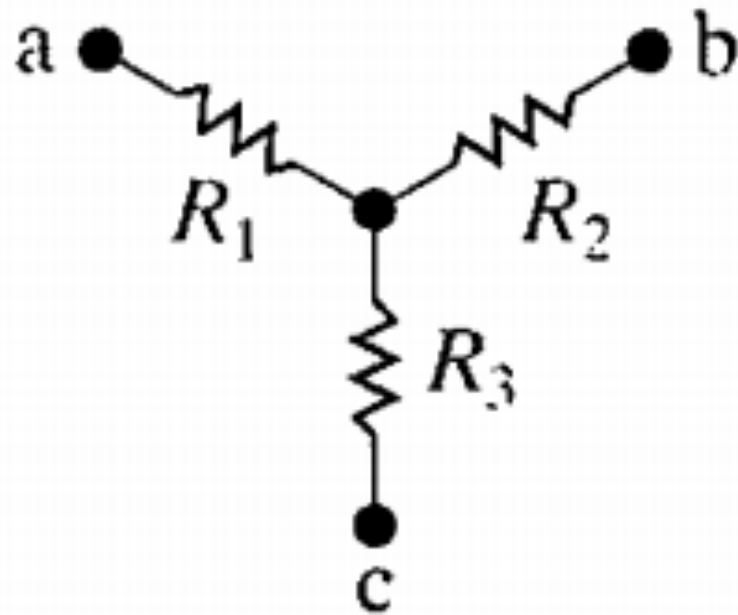

▲ A Y structure viewed as a T structure.

The Delta-to-Y transformation

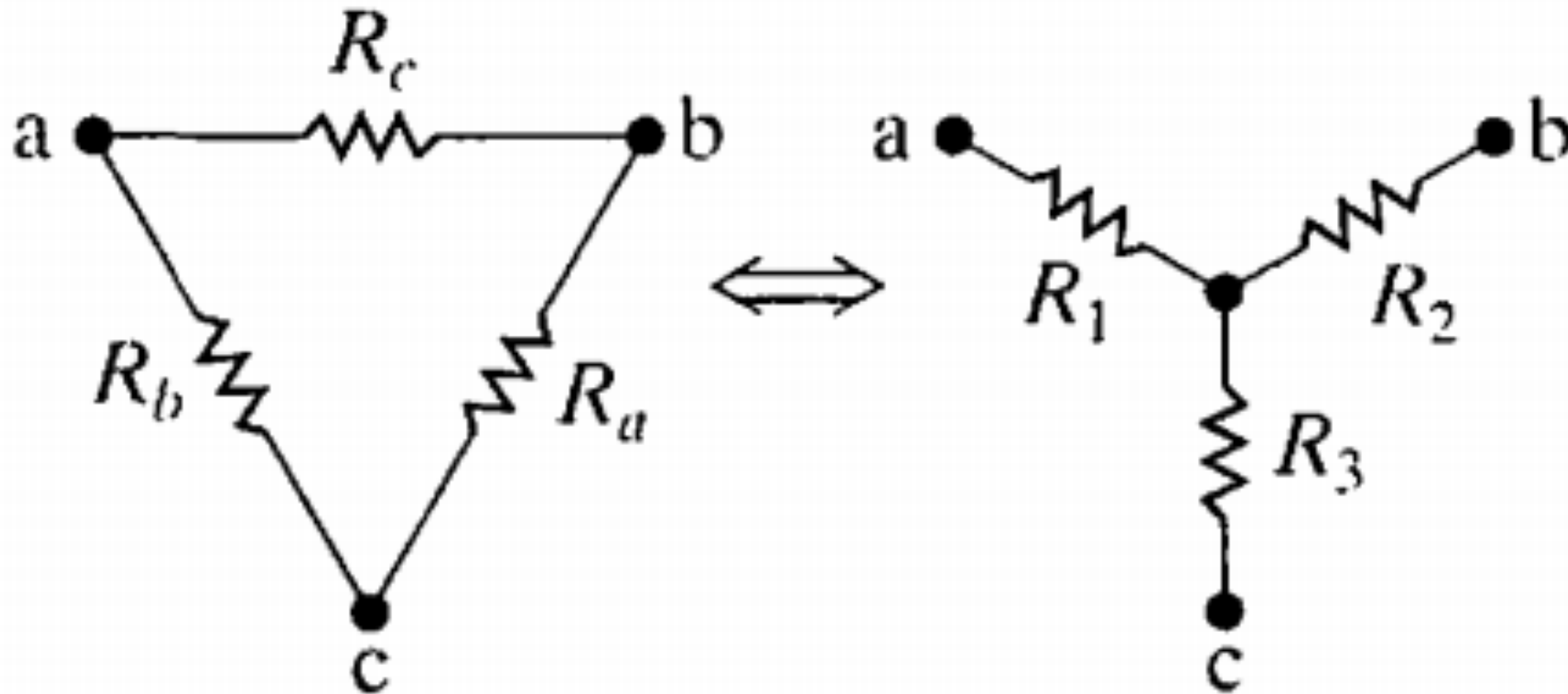


Delta-to-Y Equations

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c},$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c},$$
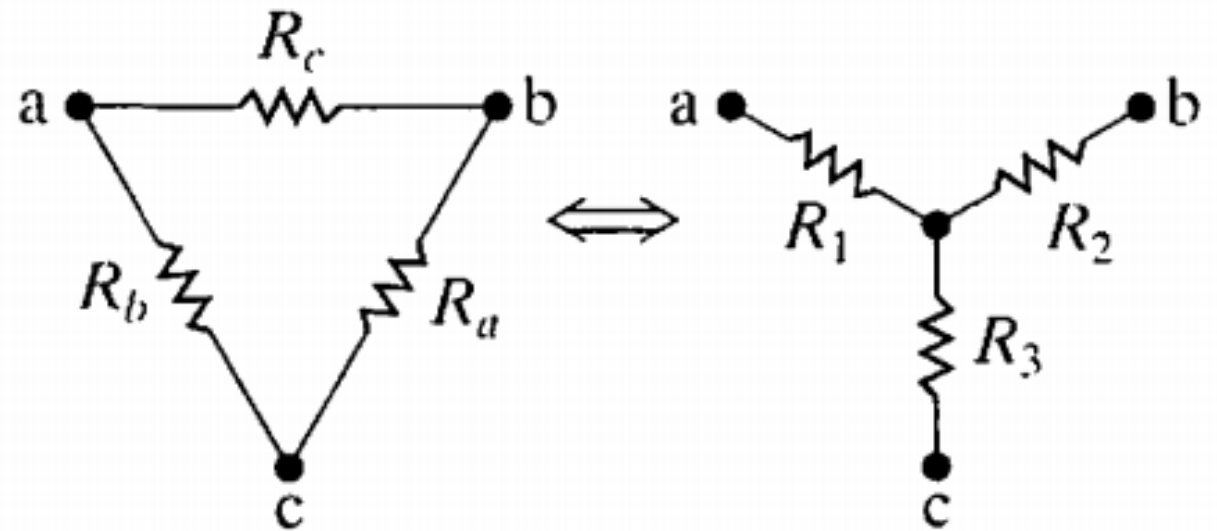
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}.$$




Y-to-Delta Equations


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1},$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2},$$
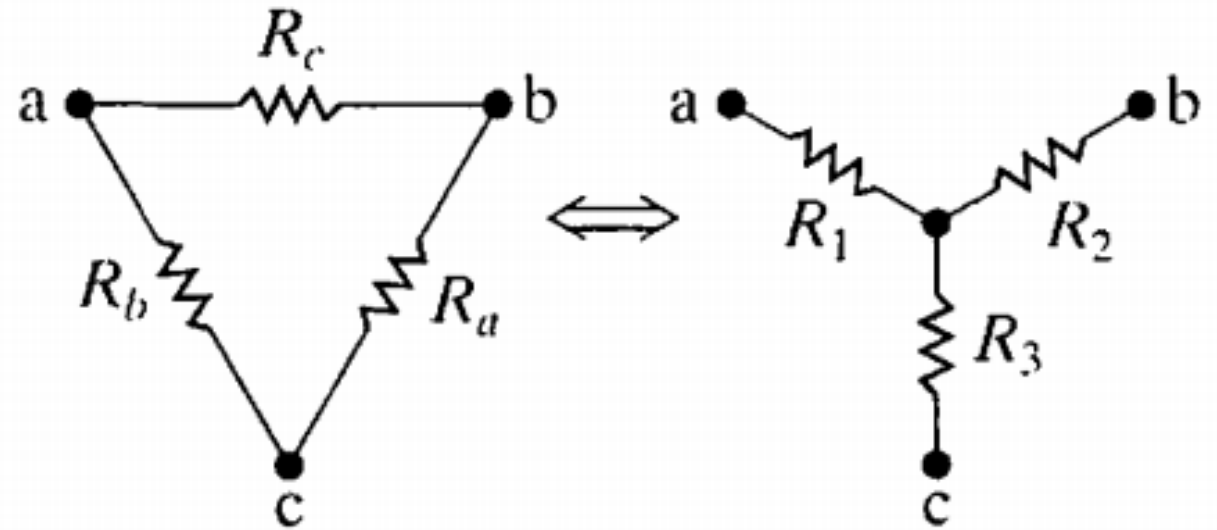
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}.$$



Y-to-Delta Equations and vice-versa

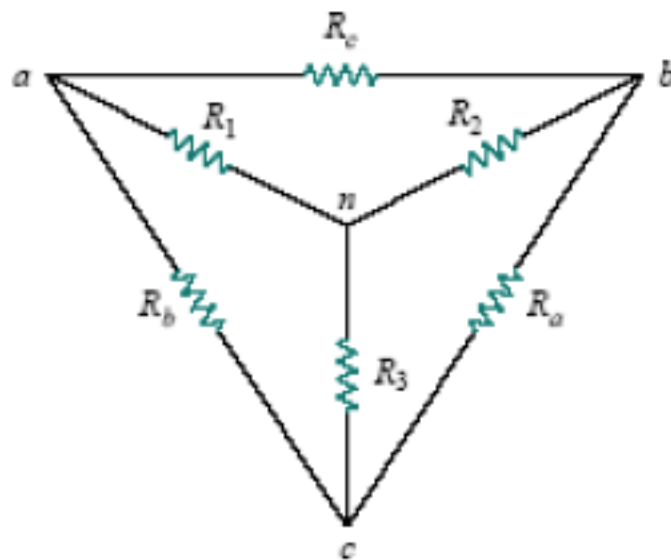

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Example

Find the current and power supplied by the 40 V source in the circuit shown

$$R_1 = \frac{100 \times 125}{250} = 50 \Omega,$$



$$R_2 = \frac{125 \times 25}{250} = 12.5 \Omega,$$

$$R_3 = \frac{100 \times 25}{250} = 10 \Omega.$$

Substituting the Y-resistors into the circuit shown in Fig. 3.32 produces the circuit shown in Fig. 3.34. From Fig. 3.34, we can easily calculate the resistance across the terminals of the 40 V source by series-parallel simplifications:

$$R_{eq} = 55 + \frac{(50)(50)}{100} = 80 \Omega.$$

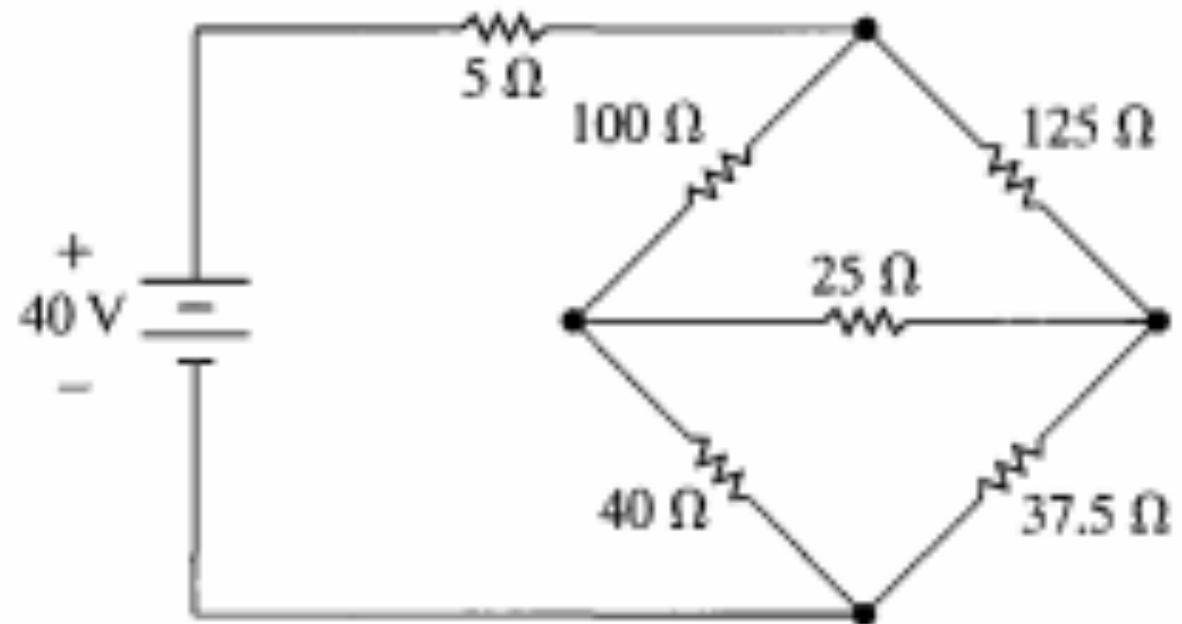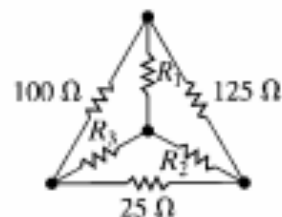The final step is to note that the circuit reduces to an 80 Ω resistor across a 40 V source, as shown in Fig. 3.35, from which it is apparent that the 40 V source delivers 0.5 A and 20 W to the circuit.



Example

Find the current and power supplied by the 40 V source in the circuit shown

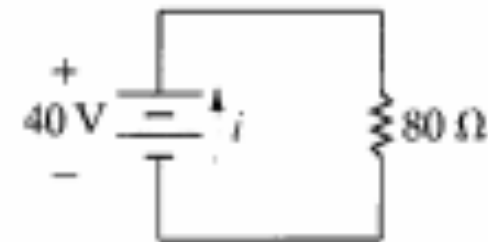
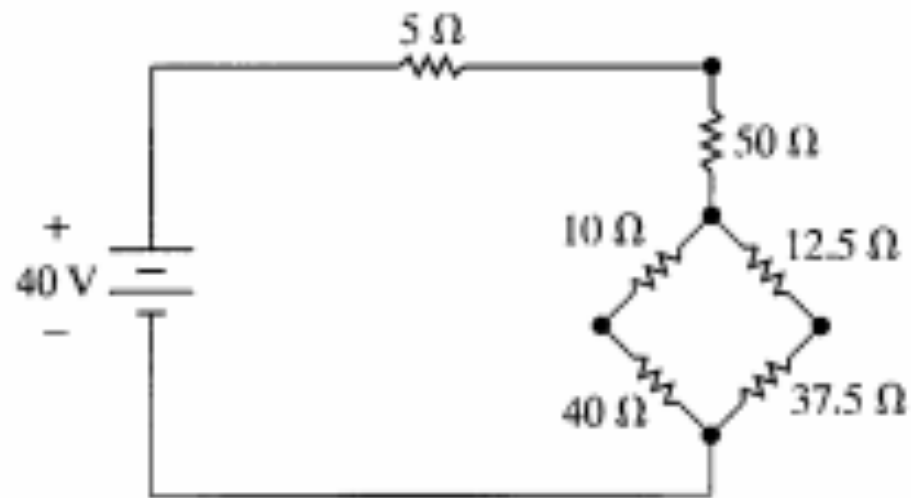


Figure 3.35 ▲ The final step in the simplification of the circuit shown in Fig. 3.32.

Special cases

The Y and Δ networks are said to be *balanced* when

$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta$$

Under these conditions, conversion formulas become

$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y$$

Example

Obtain the equivalent resistance R_{ab} for the circuit in Fig. and use it to find current i .

Solution:

In this circuit, there are two Y networks and one Δ network. Transforming just one of these will simplify the circuit. If we convert the Y network comprising the 5- Ω , 10- Ω , and 20- Ω resistors, we may select


$$R_1 = 10 \Omega, \quad R_2 = 20 \Omega, \quad R_3 = 5 \Omega$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10}$$

$$= \frac{350}{10} = 35 \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5 \Omega$$
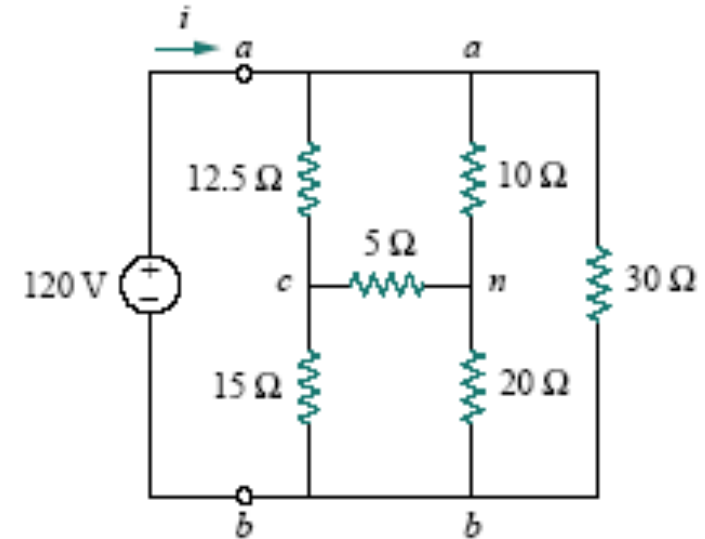
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70 \Omega$$



Example

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.2917 \Omega$$


$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$

so that the equivalent circuit is shown in Fig. 2.53(b). Hence, we find

$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \Omega$$


Then
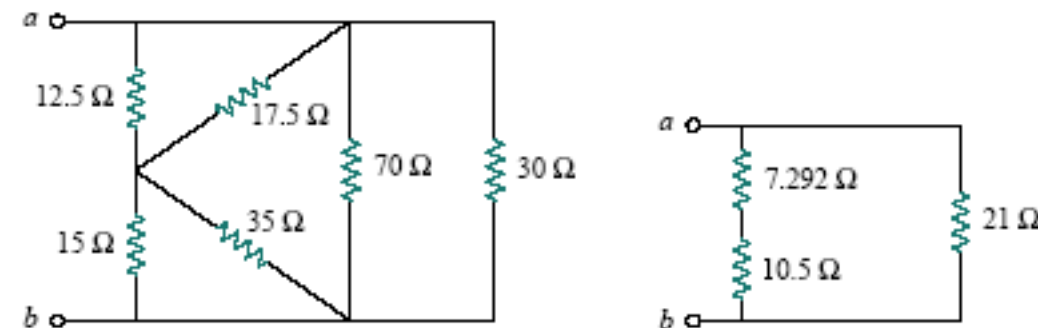
$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 \text{ A}$$



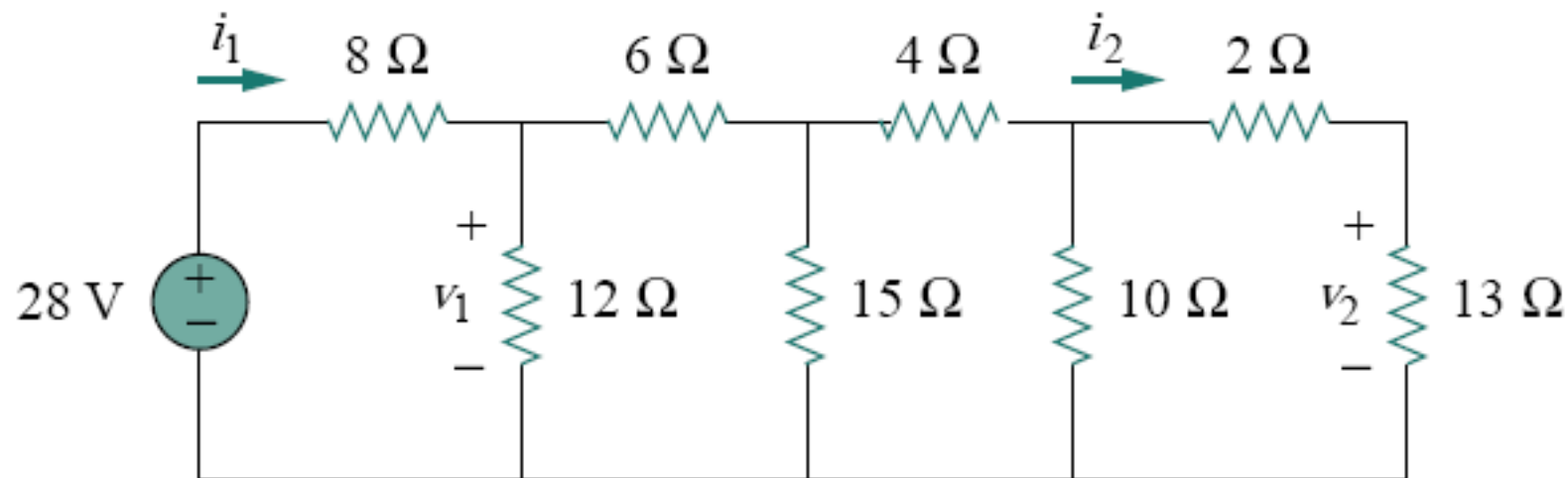
Example

Determine i_1 , i_2 , v_1 , and v_2 in the ladder network in Fig. Calculate the power dissipated in the $2\text{-}\Omega$ resistor.



Example

Calculate I_o in the circuit of Fig.

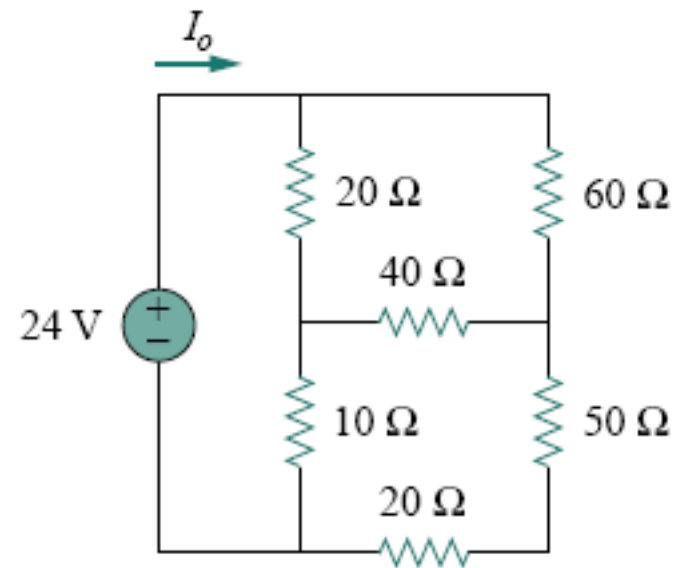


Inductors

Inductors

- An inductor is a passive element designed to **store energy** in its magnetic field. Inductors find numerous applications in electronic and power systems.
- They are used in **power supplies, transformers, radios, TVs, radars, and electric motors.**
- Any conductor of electric current has inductive properties and may be regarded as an inductor. But in order to enhance the inductive effect, a practical inductor is usually formed into a **cylindrical coil** with **many turns** of conducting wire



Inductors

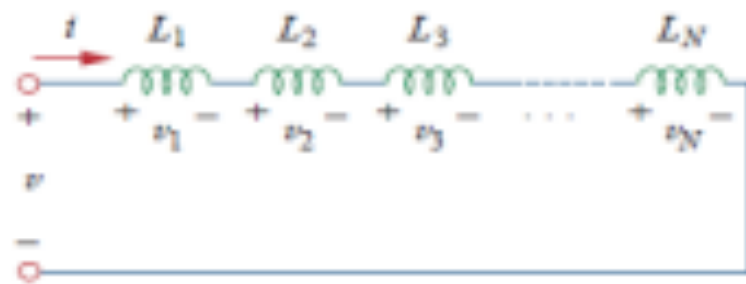



$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt}$$

$$= \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$
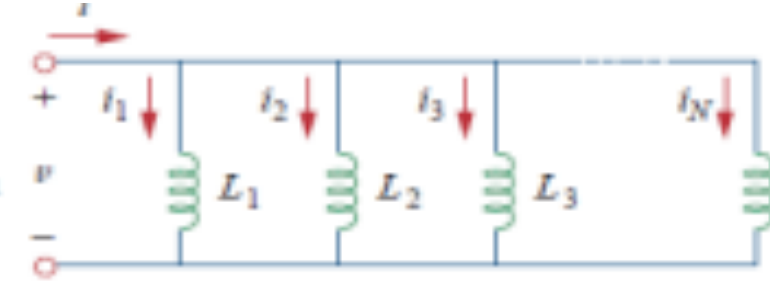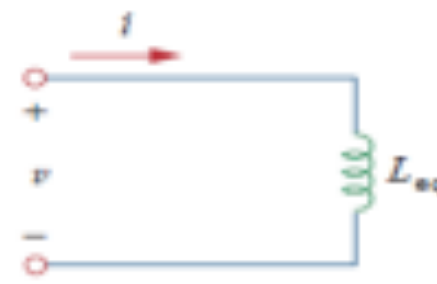
$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$

$$= \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

Capacitors

Capacitors

- A capacitor is a passive element designed to **store energy** in its electric field. Besides resistors, capacitors are the most common electrical components. Capacitors are used extensively in **electronics, communications, computers, and power systems.**

$$1F = 1C/1V$$

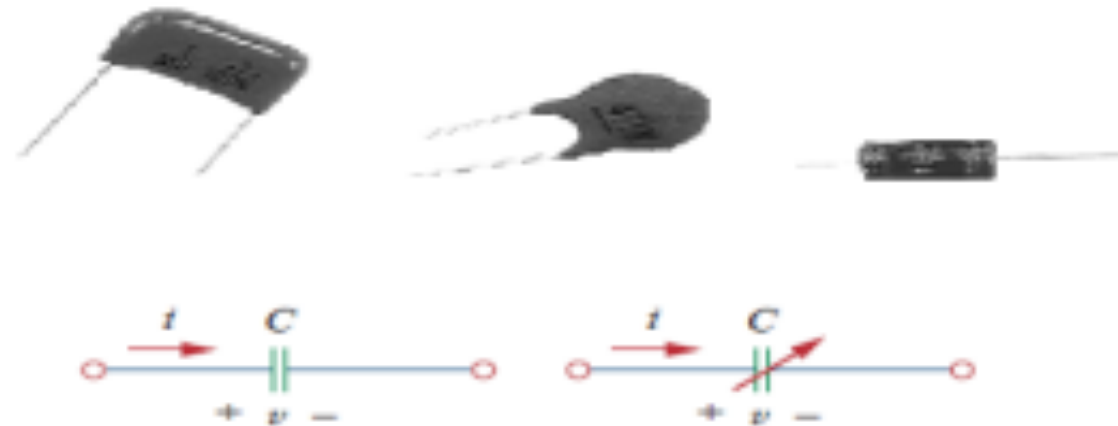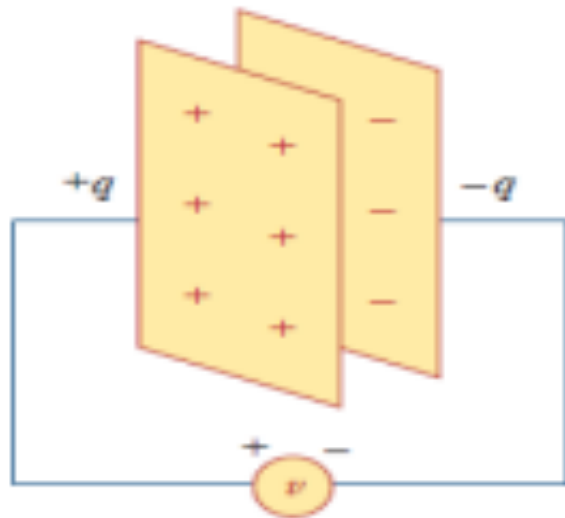

Capacitors




$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$
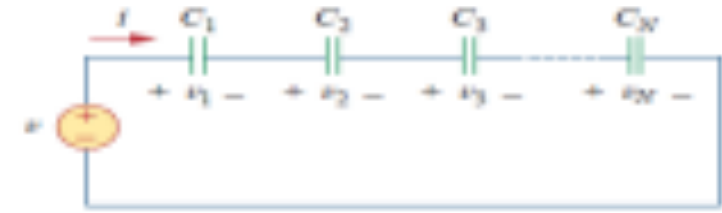
$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$



$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = \frac{1}{C_1} \int_{t_0}^t i(t) dt + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(t) dt + v_2(t_0)$$

$$+ \dots + \frac{1}{C_N} \int_{t_0}^t i(t) dt + v_N(t_0)$$

$$= \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(t) dt + v_1(t_0) + v_2(t_0)$$

$$+ \dots + v_N(t_0)$$

$$= \frac{1}{C_{eq}} \int_{t_0}^t i(t) dt + v(t_0)$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

Important characteristics of basic elements

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
$v-i$:	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit

Revision

*Thank
you*

