
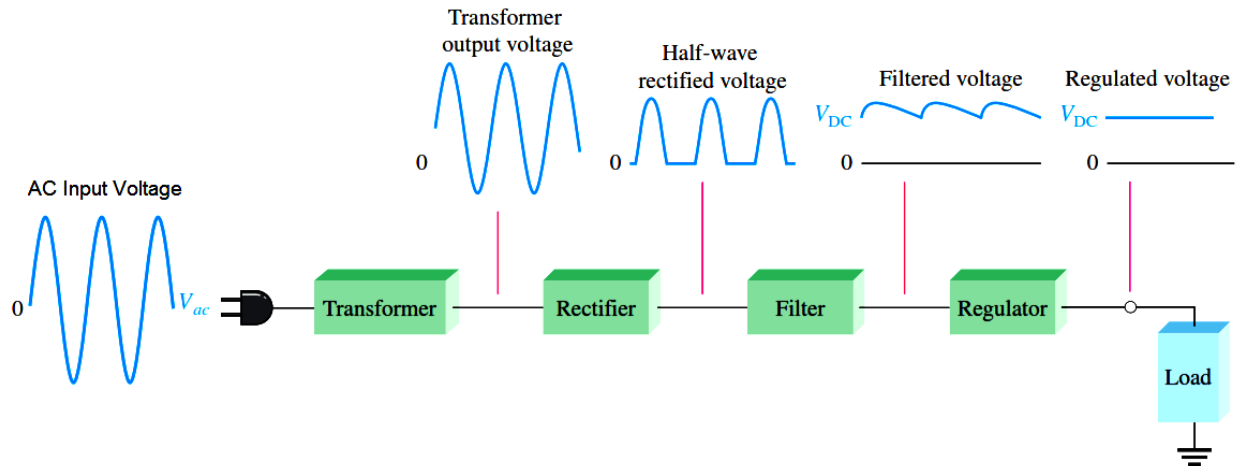


Project

Regulated Power Supply Circuit Diagram

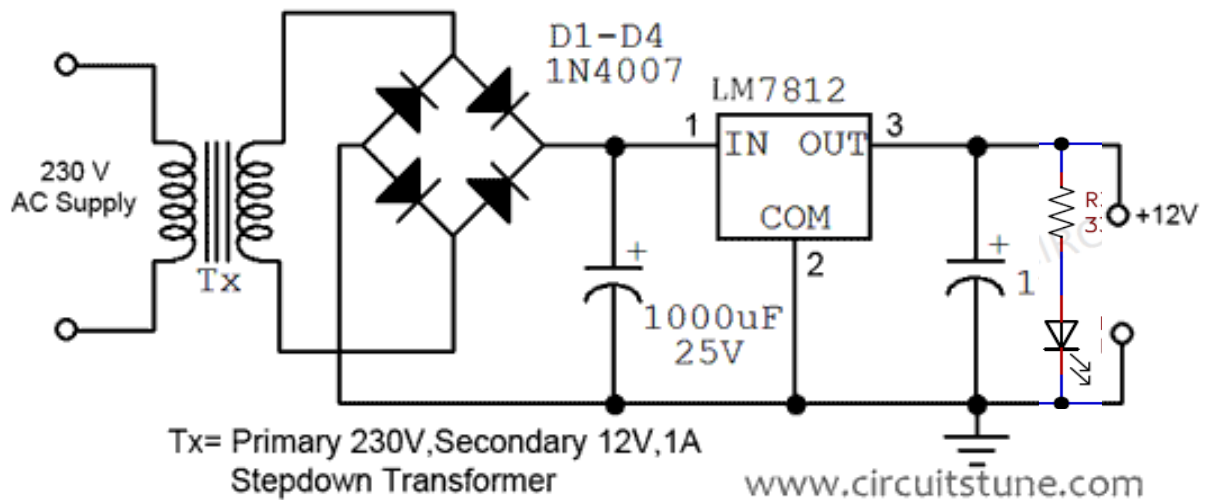

Here this circuit diagram is for **+12V regulated (fixed voltage) DC power supply**. This **power supply circuit diagram** is ideal for an average current requirement of 1Amp. This circuit is based on IC **LM7812**. It is a 3-terminal (+ve) voltage regulator IC. It has short circuit protection, thermal overload protection. LM7812 IC is from LM78XX series. The LM78XX series IC is positive voltage regulator IC for different voltage requirements, for example [LM7805](#) IC is made for [5 volt fixed output voltage](#). There is LM79XX IC series for negative voltage.



A transformer (Tx=Primary 230 Volt, Secondary 12 Volt , 1Amp step down transformer) is used to convert 230V to 12V from mains. Here used a bridge rectifier made by four 1N4007 or 1N4003 diode to [convert AC to DC](#) . The filtering capacitor 1000uF,25V is used to reduce the ripple and get a smooth DC voltage. This circuit is very easy to build. For good performance input voltage should be greater than 12V in pin-1 of IC LM7812. Use a heat sink to IC LM7812 for safeguarding it from overheating.