

* SEC 3 *

* Medical Power electronics *


* Desired Characteristics In Controllable Switches

In Ideal:

M-han

- (1) Block arbitrarily large forward & reverse voltages with zero current flow when off
- (2) Conduct arbitrarily large currents with zero voltage drop when on.
- (3) Switch from on to off or vice versa ~~instantaneously~~ when triggered
- (4) Small power required from control source to trigger the switch.

⇒ In Practical:

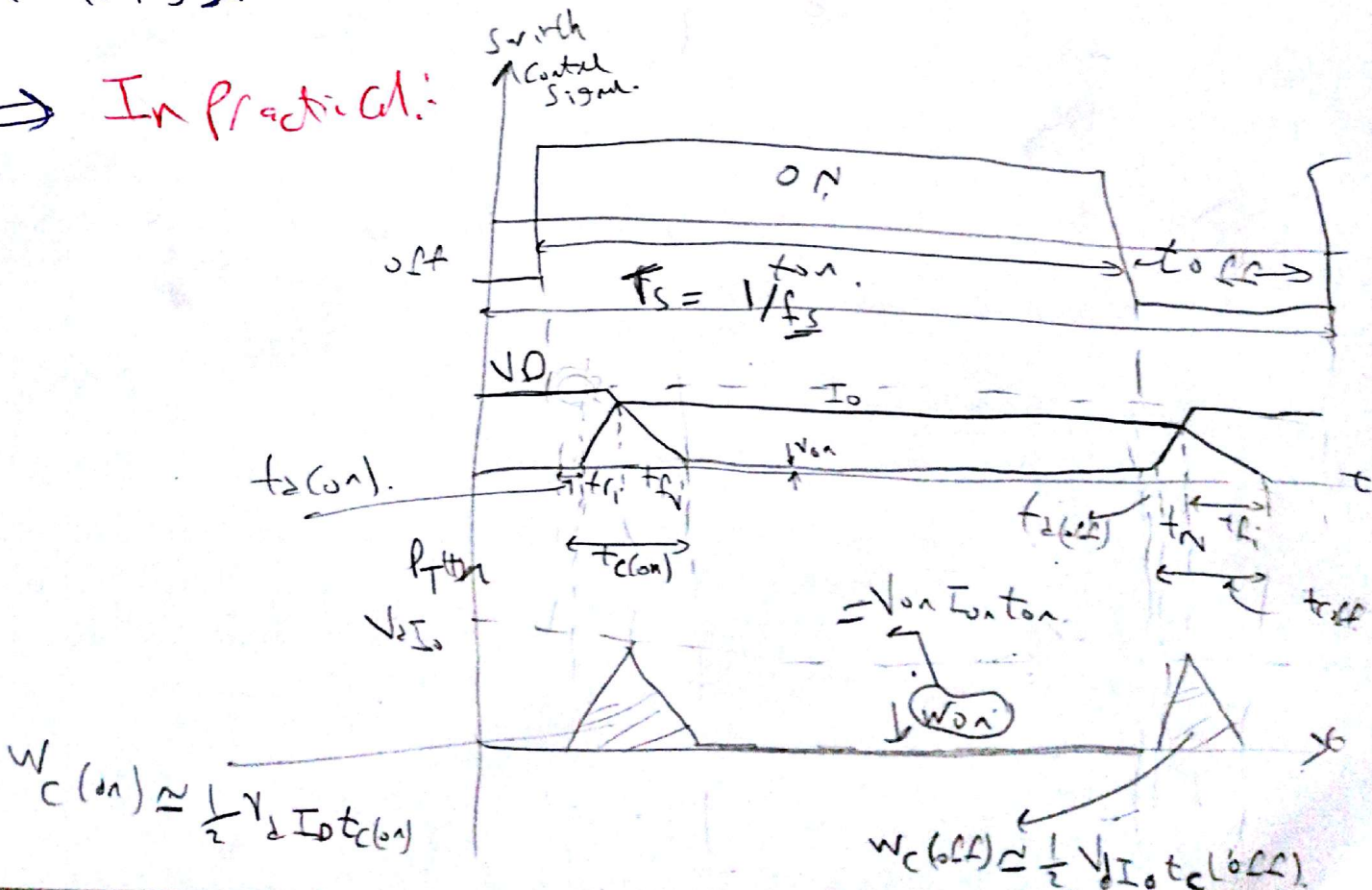

⇒ Average power losses during transition:

$$P_s = \frac{1}{2} V_d I_o f_s (t_{(on)} + t_{(off)})$$

↪ $P_T(t) = V_T C_T$

$$P = \int_0^T V_T C_T dt \approx \frac{1}{2} V_d I_o f_s (t_{(on)} + t_{(off)})$$

$\propto f_s$

⇒ In Green s.f.f-state, leakage current can be neglected.

Sheet (1)

(1)


$$P_s \approx \frac{1}{2} V_d I_o f_s \left(\overset{t_{r_i} + t_{r_v}}{t_c(\text{on})} + \overset{t_{f_i} + t_{f_v}}{t_c(\text{off})} \right)$$

$$= \frac{1}{2} \times 300 \times 4 \times \frac{1}{10 \times 10^{-6}} \times (100 \times 10^{-9} + 50 \times 10^{-9} + 200 \times 10^{-8} + 190 \times 10^{-9})$$

$$P_s = 27 \text{ W}$$

(2)

$$P_s \propto f_s$$

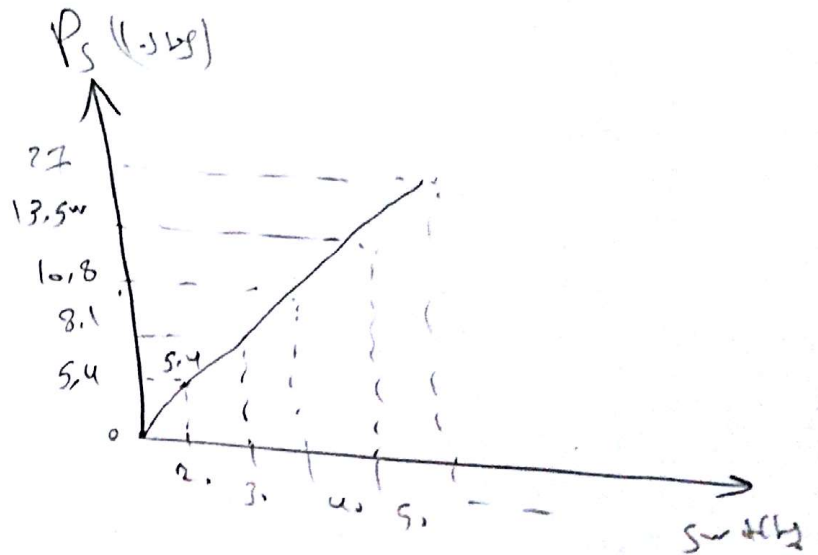

$$\textcircled{3} V_{BD} = 2500 \text{ V}$$

Req: $w_d = ?$ $N_d = ??$

drift region

↳ doping density.

Solution:

$$\textcircled{*} w_d = 10^{-5} * V_{BD} \Rightarrow 10^{-5} * 2500 = 25 \text{ mm}$$

for Non-Bunch Through = $\frac{1}{2} * 25 = 12.5 \text{ mm}$


$$\textcircled{*} N_d \approx \frac{1.3 * 10^{17}}{2500} = 5.2 * 10^{13} \text{ cm}^{-3}$$

④ Given:

$$V_s = 120 \text{ V}_{\text{rms}}, f = 60 \text{ Hz}, R = 5 \Omega$$

Req:
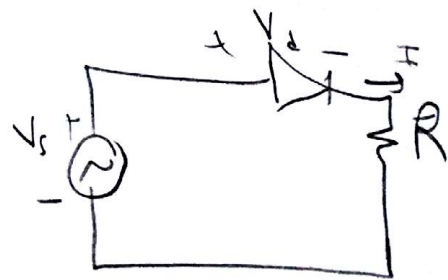
$$V_{\text{avg}} = ?, I_{\text{avg}} = ?, P_{\text{avg}} = ?, \text{P.f.} = ?$$



Solution:

$$\textcircled{1} V_{\text{avg}} = \frac{V_m}{\pi} = \frac{120\sqrt{2}}{\pi} = 54.01 \text{ V}$$

$$\textcircled{2} I_{\text{avg}} = \frac{V_{\text{avg}}}{R} = \frac{54}{5} = 10.8 \text{ A}$$

$$\textcircled{3} P_{\text{avg}} = I_{\text{avg}} * V_{\text{avg}} = 54 * 10.8 = 583.4 \text{ W}$$

$$\textcircled{4} \text{P.f.} = \frac{V_{\text{rms}} I_{\text{rms}}}{V_{\text{avg}} I_{\text{avg}}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{V_m}{\pi}} = \frac{\sqrt{2}}{2} = 0.707$$


5) Given:

$$V_s = 220 \text{ V (R.M.S)}, R = 20 \Omega$$

Req: a) V_{avg} b) V_{rms} c) V_{avc} d) Diode rating f) draw waveform


Solution:
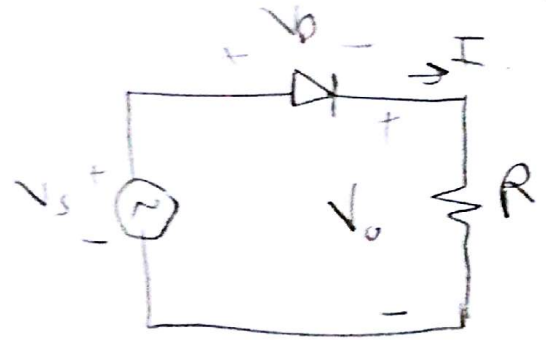
$$\begin{aligned} \text{a) } V_{avg} &= \frac{V_m}{\pi} = \frac{\sqrt{2} V_{rms}}{\pi} \\ &= \frac{\sqrt{2} \times 220}{\pi} = 99.33 \text{ V} \end{aligned}$$



$$\text{b) } V_{rms} = \frac{V_{max}}{2} = \frac{\sqrt{2} \times 220}{2} = 155.56 \text{ V}$$
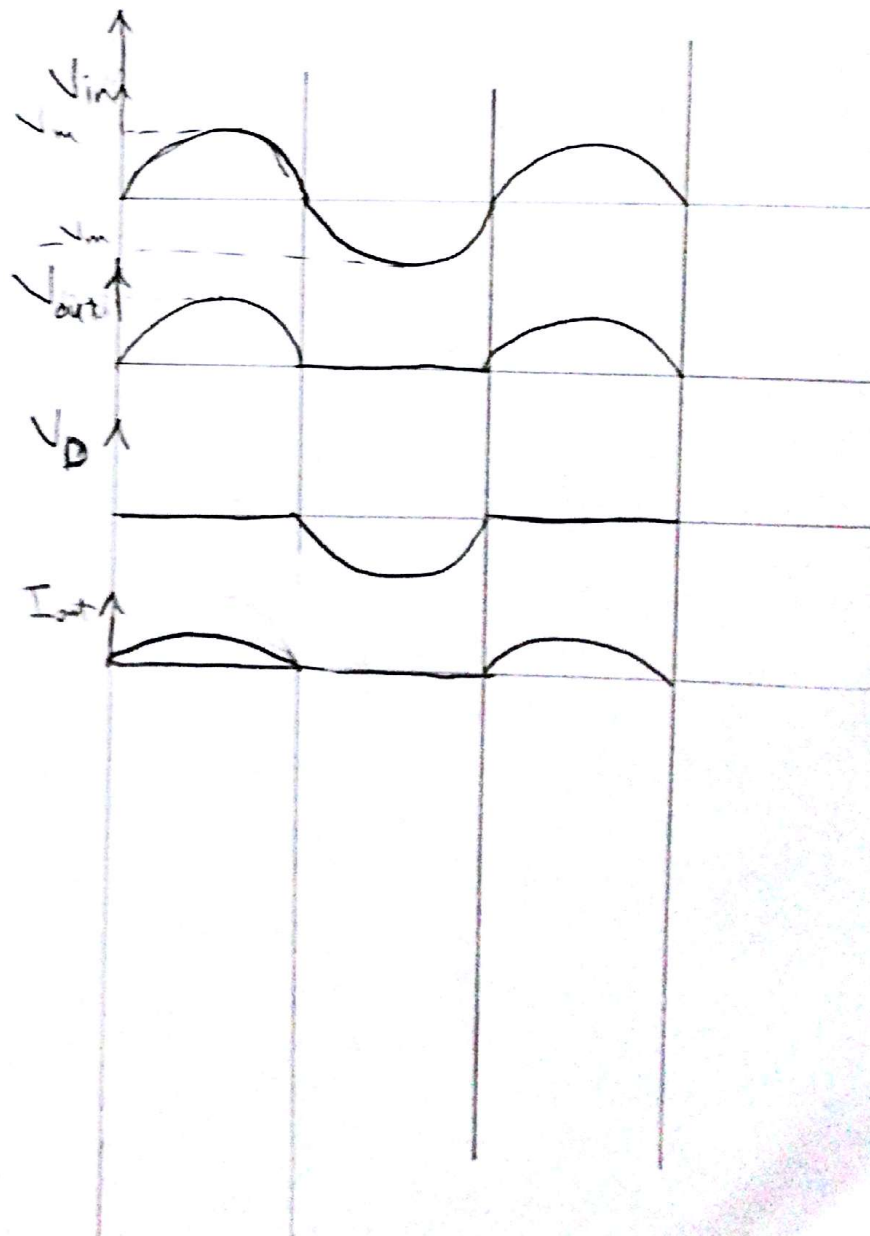
$$\begin{aligned} \text{c) } V_{avc} &= \sqrt{V_{rms}^2 - V_{avg}^2} \\ &= \sqrt{(155.56)^2 - (99.33)^2} \\ &= 119.96 \text{ V} \end{aligned}$$



d)

The Peak reverse voltage

In diode = V_m .

→ To be In safe IT must be greater ($1.5 \times V_m$).

$$\begin{aligned} I &= \frac{V_{rms}}{R} = \frac{V_{max}}{2R} \\ &= \frac{220\sqrt{2}}{2 \times 20} = 7.77 \text{ A} \end{aligned}$$



Sheet (1)

1- For the circuit shown in Fig.(1), calculate the switching power loss if the switching time from the data sheet of the switching device are:

$$t_{ri}=100 \text{ ns} \quad t_{ff}=200 \text{ ns} \quad t_{rv}=100 \text{ ns} \quad t_{fv}=50 \text{ ns}$$

and the $V_d=300\text{V}$, $I_d=4 \text{ A}$, the switching period time is 10 μs .

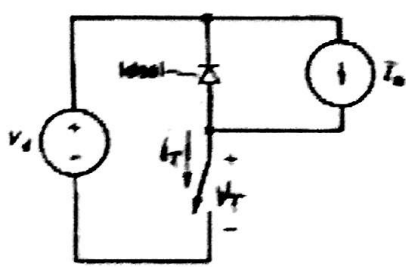


Fig. (1)

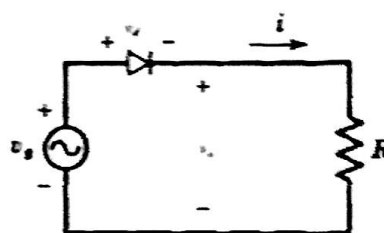


Fig.(2)

2- Plot the switching power loss as function of switching frequency from 20-100 KHz for the switching device in problem (1).

3- A power diode is designed to have a breakdown voltage of 2500 V, estimate the minimum width of the drift region (W_d), and the doping density of the drift region (N_d). Assuming that the diode is non-punch through type.

4- For the half-wave rectifier of Fig.(2), the source is a sinusoid of 120 V rms at a frequency of 60 Hz. The load resistor is 5 Ω . Determine (a) the average load current, (b) the average power absorbed by the load and (c) the power factor of the circuit.

5- If the voltage of problem (4) is 220 V and the load resistance is 20 Ω , find the a) average output voltage , (b) the r.m.s of output voltage , (c) the r.m.s of ac components of the output voltage (d) the rating values of the diode , and (f) draw the different waveforms